SEPT 1977

practical WIRELESS

85

THE PW 'jubilee'

ELECTRONIC ORGAN
Part-1

Australia 85c
New Zealand 85c
South Africa 80c
Malaysia $2·25

Also:

C CAR VOLTAGE REGULATOR

GP SHORT-WAVE RECEIVER-1

New eries { DESIGN YOUR OWN PROJECTS
PASSING THE RADIO AMATEURS EXAM.

T.T.L. 74 I.C's By TEXAS, NATIONAL, I.T.T., FAIRCHILD Etc

7400	14p	7413	35p	7432	25p	7454	15p	7490	35p	74121	25p	74139	100p	74156	70p
7401	16p	7414	80p	7437	55p	7460	15p	7491	75p	74122	45p	74140	60p	74157	70p
7402	16p	7416	39p	7438	25p	7470	39p	7492	45p	74123	60p	74141	270p	74160	90p
7403	16p	7417	39p	7440	15p	7472	25p	7493	40p	74125	50p	74142	270p	74161	90p
7404	16p	7420	15p	7441	65p	7473	30p	7495	60p	74126	59p	74144	270p	74162	90p
7405	16p	7422	39p	7442	65p	7474	38p	7496	70p	74130	130p	74147	230p	74163	90p
7406	40p	7423	25p	7445	80p	7475	39p	74100	95p	74131	100p	74148	155p	74164	125p
7407	40p	7425	25p	7447	75p	7476	39p	74101	45p	74132	70p	74150	120p	74165	125p
7408	20p	7426	25p	7448	75p	7483	85p	74105	40p	74135	100p	74151	65p	74166	125p
7409	20p	7427	25p	7450	15p	7485	100p	74106	50p	74136	70p	74153	65p	74167	150p
7410	15p	7428	45p	7451	15p	7486	30p	74107	35p	74137	140p	74154	120p	74170	200p
7411	20p	7430	15p	7453	15p	7489	250p	74120	90p	74138	125p	74155	70p	74173	150p
7412	20p														

74174	100p	74180	70p	74188	350p	74251	90p	74298	100p	74365	80p	74490	150p	74C151	150p
74175	75p	74181	350p	74189	350p	74253	90p	74299	250p	74366	80p	74491	150p	74C154	350p
74176	100p	74182	90p	74190	140p	74256	90p	74300	250p	74367	80p	74492	150p	74C157	150p
74177	100p	74184	150p	74191	140p	74257	90p	74301	90p	74368	80p	74495	150p	74C160	150p
74178	140p	74185	150p	74192	120p	74259	250p	74302	90p	74369	80p	74496	150p	74C161	150p
74179	140p	74186	350p	74193	120p	74260	90p	74303	90p	74370	80p	74500	150p	74C162	150p
74180	100p	74187	350p	74194	140p	74265	90p	74304	90p	74371	80p	74501	150p	74C163	150p
74181	125p	74188	350p	74195	120p	74266	90p	74305	90p	74372	80p	74502	150p	74C164	150p
74182	75p	74189	350p	74196	140p	74267	90p	74306	90p	74373	80p	74503	150p	74C165	150p
74183	150p	74190	140p	74197	100p	74268	90p	74307	90p	74374	80p	74504	150p	74C173	150p
74184	150p	74191	140p	74198	185p	74273	90p	74308	90p	74375	80p	74505	150p	74C174	150p
74185	150p	74192	140p	74199	185p	74274	90p	74309	90p	74376	80p	74506	150p	74C175	150p
74186	350p	74193	140p			74276	90p	74310	90p	74377	80p	74507	150p	74C192	150p
74187	350p	74194	140p			74278	90p	74311	90p	74378	80p	74508	150p	74C193	150p
74188	350p	74195	140p			74279	90p	74312	90p	74379	80p	74509	150p	74C195	150p
74189	350p	74196	140p			74283	90p	74313	90p	74380	80p	74510	150p	74C200	150p
74190	140p	74197	140p			74284	90p	74314	90p	74381	80p	74511	150p	74C221	150p
74191	140p	74198	185p			74285	90p	74315	90p	74382	80p	74512	150p	74C240	150p
74192	120p	74199	185p			74286	90p	74316	90p	74383	80p	74513	150p	74C241	150p
74193	140p					74290	90p	74317	90p	74384	80p	74514	150p	74C242	150p
74194	140p					74293	90p	74318	90p	74385	80p	74515	150p	74C243	150p
74195	120p					74294	90p	74319	90p	74386	80p	74516	150p	74C244	150p
74196	140p					74295	90p	74320	90p	74387	80p	74517	150p	74C245	150p
74197	140p					74296	90p	74321	90p	74388	80p	74518	150p	74C247	150p
74198	185p					74297	90p	74322	90p	74389	80p	74519	150p	74C248	150p
74199	185p					74298	100p	74323	90p	74390	80p	74520	150p	74C249	150p
						74299	250p	74324	90p	74391	80p	74521	150p	74C250	150p
						74300	250p	74325	90p	74392	80p	74522	150p	74C251	150p
						74301	90p	74326	90p	74393	80p	74523	150p	74C253	150p
						74302	90p	74327	90p	74394	80p	74524	150p	74C256	150p
						74303	90p	74328	90p	74395	80p	74525	150p	74C257	150p
						74304	90p	74329	90p	74396	80p	74526	150p	74C258	150p
						74305	90p	74330	90p	74397	80p	74527	150p	74C259	150p
						74306	90p	74331	90p	74398	80p	74528	150p	74C260	150p
						74307	90p	74332	90p	74399	80p	74529	150p	74C261	150p
						74308	90p	74333	90p	74400	80p	74530	150p	74C262	150p
						74309	90p	74334	90p	74401	80p	74531	150p	74C263	150p
						74310	90p	74335	90p	74402	80p	74532	150p	74C264	150p
						74311	90p	74336	90p	74403	80p	74533	150p	74C265	150p
						74312	90p	74337	90p	74404	80p	74534	150p	74C266	150p
						74313	90p	74338	90p	74405	80p	74535	150p	74C267	150p
						74314	90p	74339	90p	74406	80p	74536	150p	74C268	150p
						74315	90p	74340	90p	74407	80p	74537	150p	74C269	150p
						74316	90p	74341	90p	74408	80p	74538	150p	74C270	150p
						74317	90p	74342	90p	74409	80p	74539	150p	74C271	150p
						74318	90p	74343	90p	74410	80p	74540	150p	74C272	150p
						74319	90p	74344	90p	74411	80p	74541	150p	74C273	150p
						74320	90p	74345	90p	74412	80p	74542	150p	74C274	150p
						74321	90p	74346	90p	74413	80p	74543	150p	74C275	150p
						74322	90p	74347	90p	74414	80p	74544	150p	74C276	150p
						74323	90p	74348	90p	74415	80p	74545	150p	74C277	150p
						74324	90p	74349	90p	74416	80p	74546	150p	74C278	150p
						74325	90p	74350	90p	74417	80p	74547	150p	74C279	150p
						74326	90p	74351	90p	74418	80p	74548	150p	74C280	150p
						74327	90p	74352	90p	74419	80p	74549	150p	74C281	150p
						74328	90p	74353	90p	74420	80p	74550	150p	74C282	150p
						74329	90p	74354	90p	74421	80p	74551	150p	74C283	150p
						74330	90p	74355	90p	74422	80p	74552	150p	74C284	150p
						74331	90p	74356	90p	74423	80p	74553	150p	74C285	150p
						74332	90p	74357	90p	74424	80p	74554	150p	74C286	150p
						74333	90p	74358	90p	74425	80p	74555	150p	74C287	150p
						74334	90p	74359	90p	74426	80p	74556	150p	74C288	150p
						74335	90p	74360	90p	74427	80p	74557	150p	74C289	150p
						74336	90p	74361	90p	74428	80p	74558	150p	74C290	150p
						74337	90p	74362	90p	74429	80p	74559	150p	74C291	150p
						74338	90p	74363	90p	74430	80p	74560	150p	74C292	150p
						74339	90p	74364	90p	74431	80p	74561	150p	74C293	150p

SEMICONDUCTORS
by MULLARD, TEXAS, MOTOROLA, SIEMENS, I.T.T., R.C.A.

AA113	18p	BA138	16p	BC168B	14p	BC548C	14p	BF123	45p	BF336	35p	BY164	50p	OC140	150p
AA144	18p	BA148	16p	BC168C	14p	BC549B	13p	BF125	45p	BF337	35p	BY404	30p	OC171	60p
AA217	38p	BA154	12p	BC169C	15p	BC549C	14p	BF127	50p	BF353	50p	C1120	38p	OC200	80p
AC125	38p	BA157	15p	BC171	14p	BC557	13p	BF128	50p	BF394	50p	C1124	38p	OC201	80p
AC126	19p	BA173	15p	BC172C	12p	BC558	13p	BF152	50p	BF451	50p	E300	42p	R1039	150p
AC127	19p	BA182	15p	BC182	12p	BC559	13p	BF154	50p	BF459	50p	E304	42p	TIP29	45p
AC127/01	25p	BA218	15p	BC182B	12p	BCY71	28p	BF167	35p	BF833	130p	E310	125p	TIP29A	47p
AC128	18p	BAX13	5p	BC182L	12p	BCY72	15p	BF179C	40p	BFX84	25p	E320	95p	TIP29B	49p
AC128	18p	BAX16	5p	BC183	12p	BD124	85p	BF180	39p	BFX85	30p	MJE340	45p	TIP29C	52p
AC153K	40p	BB105A	35p	BC183L	12p	BD131	85p	BF181	35p	BFX87	25p	MPSA06	35p	TIP30	55p
AC176	28p	BB110	45p	BC184	12p	BD132	85p	BF182	39p	BFX88	25p	OA10	49p	TIP30A	58p
AC177	35p	BC107	16p	BC184L	12p	BD135	49p	BF183	39p	BFY50	25p	OA47	15p	TIP30B	65p
AC191	38p	BC108	14p	BC186	25p	BD136	49p	BF184	35p	BFY51	25p	OA90	6p	TIP30C	70p
AD149	60p	BC108C	15p	BC205	14p	BD137	49p	BF185	35p	BFY52	25p	OA91	6p	TIP31	55p
AD161	48p	BC109	16p	BC212	12p	BD138	49p	BF194	10p	BFY90	125p	OA202	8p	TIP31A	58p
AD162	48p	BC109C	14p	BC212L	12p	BD139	49p	BF195	10p	BFY90	125p	OC23	200p	TIP31B	65p
AD161/2MP	pr	BC113	12p	BC213L	12p	BD140	49p	BF196	10p	BR101		OC25	100p	TIP31C	70p
	90p	BC117	19p	BC214	13p	BD175	40p	BF197	10p	BRY56		OC26	100p	TIP32	60p
AF114	50p	BC125	25p	BC214L	13p	BD176	40p	BF198	25p	BRY56		OC35	75p	TIP32A	65p
AF115	22p	BC126	15p	BC258	13p	BD177	40p	BF199	30p	BSX20		OC42	75p	TIP32B	85p
AF116	22p	BC146	12p	BC294	45p	BD178	40p	BF200	39p	BSY40		OC43	35p	TIP32C	90p
AF117	22p	BC147	10p	BC303	55p	BD182	80p	BF224	25p	BSY51		OC45	35p	TIP33A	90p
AF118	36p	BC148	10p	BC307	10p	BD183	80p	BF225	39p	BT100A		OC71	25p	TIP33B	95p
AF125	25p	BC148C	14p	BC323	60p	BD233	59p	BF244B	35p	BU105		OC72	25p	TIP33C	100p
AF126	25p	BC149	10p	BC328	60p	BD234	65p	BF245	35p	BU133		OC74	30p	TIP34A	95p
AF127	25p	BC157	16p	BC338	12p	BD410	100p	BF256	39p	BU208		OC75	30p	TIP34B	100p
AF239	45p	BC158	16p	BC477	15p	BDY92/01	150p	BF258	39p	BY100		OC81	35p	TIP34C	105p
BA114	18p	BC159	16p	BC478	25p	BF115	45p	BF259	39p	BY126		OC81D	25p	TIP41A	90p
BA121	9p	BC167A	12p	BC548	12p	BF121	45p	BF324	30p	BY133		OC82	35p	TIP41B	95p
												OC84	50p	TIP41C	100p
														TIP42A	95p
														TIP42B	100p
														TIP42C	105p
														TIP55	70p
														TIP120	150p
														TIP121	150p
														TIP122	150p
														TIP125	150p
														TIP2955	150p
														TIP3055	70p
														TIS90	25p
														TIS91	25p
														TIS97	25p
														2N1302	110p
														2N1303	70p
														2N1304	70p
														2N1305	70p
														2N1306	70p
														2N1307	70p
														2N1308	70p
														2N1711	25p
														2N2219A	25p
														2N2222	18p
														2N2222A	20p
														2N2907	35p
														2N3053	25p
														2N3054	50p
														2N3055	60p
														2N3439	90p
														2N3702	11p
														2N3703	12p
														2N3704	11p
														2N3705	12p
														2N3706	11p
														2N3711	12p
														2N3771	230p
														2N3772	175p
														2N3819	45p
														2N3866	95p
														2N4058	11p
														2N4062	14p
														2N4286	14p
														2N5061	35p
														2N5062	35p
														2N5457	58p
														2SD234	56p

BZY88		CA3090AQ	400p	**ELECTROLYTIC CAPACITORS**			330/35	16p	**SPECIAL OFFERS**		**RESISTORS**		**MULLARD POT CORES**		**SKELETON PRE-SET POTENTIOMETERS**
400M.W.				µF/V			330/50	18p			**CARBON FILM** 5%		LA3	100–500 KHz	75p	
Zeners		TAA300	150p	1/16	5p		470/10	12p	25 W				LA4	10–100 KHz	100p	
2V7	10p	TAA350	180p	1/16	5p		470/16	12p	2 Ω 0.4 7M	2p			LA5	30–100KHz	100p	
3V0	10p	TAA550	50p	1/10	5p		470/25	15p			5 W		LA7	455K Hz	60p	
3V3	10p	TAA611B	140p	1/50	5p		470/35	18p	2 Ω 12-4 7M	2.5p	2 Ω 10 MEG	3.5p	LA13 FOR W.W. OSCILLOSCOPE		200p	
3V6	10p	TAA700	280p	2/25	5p		1000/10	25p								
3V9	10p	TAD100	250p	2/35	5p		1000/16	25p	2 Ω 12-4 7M	2.5p						
4V7	10p	TBA120S	125p	4/10	5p		1000/35	30p	2 Ω 10 MEG	3.5p						
5V1	10p	TBA120T	125p	4/25	5p		1000/50	50p								
5V6	10p	TBA540	300p	4/35	5p		2200/10	28p								
6V2	10p	TBA540Q	400p	4/50	5p		2200/35	35p								
6V8	10p	TBA550Q	400p	6.8/25	5p		2200/16	35p								
7V5	10p	TBA560	350p	10/10	5p		2200/50	70p								
8V2	10p	TBA641A12	250p	10/16	5p		2200/100	100p								
9V1	10p	TBA720	250p	10/25	5p		3300/16	35p								
10V	10p	TBA800	100p	10/50	5p		3300/25	42p								
11V	10p	TBA920	150p	22/10	5p		3300/63	85p								
BZY88		TBA990	250p	22/16	5p		4700/25	45p								
12V	10p	TCA270Q	250p	22/25	5p		4700/40	50p								
13V	10p	TCA270S	250p	22/25	5p		4700/63	120p								
15V	10p			47/10	5p											
18V	10p	LM301A	65p	22/50	5p		**POLYTER CAPACITORS**		**RELAYS**							
20V	10p	LM307A	65p	33/16	5p		Mullard or Erie		24V 3 C.O. H.D.							
22V	10p	LM308 D.I.L.	130p	33/16	5p		µF/V		11 Pin Plug 1N							
24V	10p	LM309 K	180p	33/25	5p		.001	5p	**£1·00 Each**							
30V	10p	LM309H	185p	33/40	5p		.0022	5p								
33V	10p	LM340T	280p	47/10	5p		.005	5p	**ASSORTED POLYESTER CAPACITORS**							
100 Mixed		LM380N	110p	47/10	5p		.0033	5p								
Zeners **85p**		LM555	75p	47/25	5p		.0047	5p								
BZY88		LM710 TO5	60p	47/25	5p		.0068	5p	**100 for £5·00**							
Zeners **85p**		LM710 P	45p	47/35	5p		.01	5p								
		LM723 TO5	60p	47/50	7p		.022	5p								
SAD1024	1250p	LM723 14 DIL	70p	100/10	5p		.033	5p	**BYX84 DIODES**							
5N7603ND	125p	LM741	25p	100/16	6p		.047	5p	1250 PIV 1 Amp.							
5N7602ND	125p	LM748	45p	100/25	6p		.1	5p	**100 for £8·00**							
5N7603N	125p	LM833N	155p	100/50	6p		.22	8p								
5N7602TN	150p	LM3900	90p	100/63	8p		.33	8p	**MULLARD**							
5N7602BR	188p			220/16	8p		.47	15p	1P 10V	48p						
5N7666N	160p	NE555	35p	220/16	10p		1·00	25p	4500/64V C.432	48p						
2N414	12p	NE556	100p	220/25	8p		2·2	25p	Screw Terminal	48p						
2N414	12p	NE560B	600p	330/25	15p		4·7	35p		75p						
							6·8	40p	3P 4W	48p						
									4P 3W	48p						
									4P 3W	48p						

SPECIAL OFFERS	
BC147	10p
BC148	10p
BC149	10p
BC157	10p
BC158	10p
BC159	10p
BF194	10p
BF195	10p
BF196	10p
BF197	10p
IN4148	
100 for 150p	
741 Op AMPS	
100 for £20	
555 TIMERS	
100 for £30	
RELAYS	
24V 3 C.O. H.D.	
11 Pin Plug 1N	
£1·00 Each	
ASSORTED POLYESTER CAPACITORS	
100 for £3·00	
BYX84 DIODES	
1250 PIV 1 Amp.	
100 for £8·00	
MULLARD	
4500/64V C.432	
Screw Terminal	75p

ASSOR-TED FOR £7·50p

POTENTIO-METERS

1K Lin	39p
5K Lin	39p
10K Lin	39p
25K Lin	39p
50K Lin	39p
100K Lin	39p
250K Lin	39p
500K Lin	39p
1 Meg Lin	39p
2 Meg Lin	39p
5K Log	39p
10K Log	39p
25K Log	39p
50K Log	39p
100K Log	39p
250K Log	39p
500K Log	39p
1 Meg Log	39p
2 Meg Log	39p

ROTARY SWITCHES BY LORLIN

1P 12W	48p
2P 8W	48p
3P 4W	48p
4P 3W	48p

SPECIAL SOOP OFFERS

SEMICONDUCTORS. ALL BRANDED NAMES E.G. MULLARD, TEXAS, SIEMENS, VALVO. BC107B, BC108B, BC108C, BC109B, BC109C.

£8 · 50 PER 100 CAN BE ASSORTED

WESTINGHOUSE THYRISTORS

300 Volts	16 Amp	250p

CMOS

4000	30p	4023	20p	4055
4001	20p	4024	100p	4056
4002	20p	4025	20p	4060
4006	120p	4026	280p	4066
4007	20p	4027	85p	
4009	75p	4028	155p	4069
4011	20p	4029	180p	4071
4012	20p	4030	60p	4072
4013	60p	4035	150p	4081
4015	90p	4043	220p	4082
4016	55p	4044	220p	4510
4017	110p	4047	150p	4511
4018	140p	4049	70p	4516
4020	140p	4050	50p	4518
4022	180p	4054	130p	4528

70p	74174	100p	74C151	150p	74C221	150p	74C285
70p	74175	75p	74C154	350p	74C240	150p	74C286
90p	74176	100p	74C157	150p	74C241	150p	74C287
90p	74177	100p	74C160	150p	74C242	150p	74C288
90p	74178	140p	74C161	150p	74C243	150p	74C289
90p	74179	140p	74C162	150p	74C244	150p	74C290
125p	74180	100p	74C163	150p	74C245	150p	74C291
125p	74181	350p	74C164	150p	74C247	150p	74C292
125p	74182	75p	74C165	150p	74C248	150p	74C293
150p	74185	150p	74C173	150p	74C249	150p	74C294
200p	74188	350p	74C174	150p	74C250	150p	74C295

BRIDGE RECTIFIERS

1A 50V	25p	V/REG.		
1A 100V	30p	7805	140p	
1A 200V	35p	7808	140p	
1A 400V	35p	7812	140p	
1A 600V	45p	7815	140p	
2A 50V	35p	7818	140p	
2A 100V	38p	7824	150p	
2A 200V	55p	7824	150p	

SKELETON PRE-SET POTENTIOMETERS

0·1W 50N–5M mini vert & horiz 70p
·25W 100N–3·3M horiz. 7p
·25W 200N–4·7M vert. 8p

TANTALUM BEAD CAPACITORS

35V: 0·1uF, 0·22, 0·33, 0·47, 0·68, 1·0, 2·2, 3·3, 4·7, 6·8, 22uF 10, 15, 16V: 4·7, 10, 22, 47, 10V 4·7, 15, 25, 33 Price 14p each.

LEDS

RED .125 15p
Green .125 25p
YELLOW .125 25p
RED .2 15p
GREEN .2 25p
YELLOW .2 25p
DL747 Display 200p

DIL SOCKETS

8 Pin 13p
14 Pin 14p
16 Pin 19p

BZX81 Zeners

1·3W

6V8	15p
9V1	15p
11V	15p
13V	15p
15V	15p
22V	15p
30V	15p
33V	15p
47V	15p
68V	15p
75V	15p
160V	15p

XEROZA RADIO

306 ST. PAUL'S ROAD, HIGHBURY CORNER, LONDON, N.1

TELEPHONE 01-226 1489

Easy access to Highbury via Victoria Line (London Transport) British Rail

PLEASE NOTE ALL PRICES INCLUDE POSTAGE AND V.A.T. AT 8 OR 12½% AS APPROPRIATE

LARGE STOCKS OF NEONS, NUMICATOR TUBES, SINGLE AND MULTIPHASE HIGH CURRENT RECTIFIER STACKS, CAPACITORS OF ALL TYPES INCLUDING PHOTO-FLASH AND MOTOR START, TV TUNERS ALSO SOME HIGHLY TECHNICAL EQUIPMENT AND PARTS FOR INDUSTRIAL USERS AND SCHOOLS FOR PERSONAL CALLERS

Manufacturers (Large and Small) we welcome your enquiries. Overseas Buyers/Agents etc. let us know your requirements.

ISSUE 847

practical WIRELESS

SEPTEMBER 1977 · VOLUME 53 · NUMBER 5

BRITAIN'S LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD
Telephone: 01-634 4444

News and Views

332 **EDITORIAL**—'Our Face-lift'

333 **NEWS . . . NEWS . . . NEWS**

346 **TELEVISION**—Details of the September issue

349 **PRODUCTION LINES**—Information on the latest products.....*Bill Tull*

351 **PRACTICAL WIRELESS**—Pre-view of our next issue

362 **PW READERS' PCB SERVICE**—Prices and details of the PCBs available

367 **HOTLINES**—Recent developments in electronics.....*Ginsberg*

368 **ON THE AIR**—Amateur Bands.....*Eric Dowdeswell G4AR*
SW Broadcast Bands.....*Derek Bell*
MW Broadcast Bands.....*Charles Molloy G8BUS*
VHF Bands.....*Ron Ham BRS15744*

For our Constructors

337 **GENERAL PURPOSE SW RECEIVER—1**
Complete constructional information for a general coverage receiver for AM, CW and SSB.A preselector follows next month.....*Frank Rayer G3OGR*

345 **S-DeCNOLOGY Project No. 10**
This month we present a simple **Record Player Amplifier**.....*David Gibson*

352 **THE PW 'JUBILEE' ELECTRONIC ORGAN—1**
This project uses the latest devices, is extremely versatile, and is built entirely on one printed circuit board
M. J. Hughes MA, C.Eng., MIERE

358 **DESIGN YOUR OWN PROJECTS—1**
In this series the authors show how the values of components are derived. This month, a **'Light Trigger'**
Toby Bailey and Bob Whitaker

363 **ELECTRONIC CAR VOLTAGE REGULATOR**
Replace your car's mechanical regulator with a fully electronic circuit.....*C. Grayson B.Sc.*

General Interest

334 **SO YOU WANT TO PASS THE R.A.E.?—1**
Our new series won't teach you all about electronics but you can learn enough to pass the Radio Amateurs' Examination.....*John Thornton Lawrence GW3JGA and Ken McCoy GW8CMY*

COPYRIGHT
© IPC Magazines Limited 1977. Copyright in all drawings, photographs and articles published in 'Practical Wireless' is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by 'Practical Wireless' to ensure that the advice and data give n to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

EXPANDING OFFER!

To celebrate the increased size of P.W. we are giving you a:— PAPERMATE CHROME PLATED PEN WORTH £3·95 with any watch under £20. PAPERMATE GOLD PLATED PEN WORTH £5·70 if you spend over £20. CHROME PEN & PENCIL SET (or two pens) WORTH £7·90 if you spend over £28. GOLD PLATED SET (one pen & pencil) WORTH £11·40 if you spend over £50. Items may be combined. Offer closes 30th Sept. 1977. Subject to availability.

SPECIAL PURCHASE. CASIO CASIOTRON **S15B.** Now you can afford probably the best watch in the world! Multifunction LCD with backlight. STOPWATCH, DUAL TIME ZONES. All stainless steel. Mineral glass Battery hatch. Water resistant to 130 feet. **£49·95 (R.R.P. £89·95) Black or blue face.**

R16B (Not illust) **£34·95** Bk or Bl.

ST-1. Hand-held ELECTRONIC STOPWATCH Calculator. Four stopwatch functions: Standard, Time Out, Two kinds of Lap time. TOTAL Time button. Rollover after 9 hrs, 59 mins, 59·9 secs. Converts Time to Decimal Hours & back again. Full seconds memory, constants, eg. roots, ⅟x etc. **£27·50 (£24·95 without pen).**

MQ-1. Miniature pocket version of CQ-1, 12 or 24 hour clock, stopwatch and basic calculator **£37 95** (£34·95 without pen & pencil set).

TC410
TC411

TC440
TC441

TC412
TC413

FAIRCHILD TIMEBAND LCD Watches. Latest models with BATTERY HATCH & VOUCHER FOR FREE REPLACEMENT BATTERY. Continual display of Hours & minutes. Push button once for Month & Date, twice for Seconds. Backlight, automatic calendar, AM/PM setting indicator, easily selected alternative time/date display. Beautifully styled Swiss/W. German cases. **TC441 chrome £19·95, TC440 Gold Plated £21·95, TC411 chrome £24·95, TC410 Gold Plated £27·95, TC413 Si(St bracelet £30·95, TC412 Gold Pl. £31·95.**

C5110

C500

C590

TIMEBAND MAINS DIGITAL ALARM CLOCKS. Wake up to Timeband. Precise timekeeping, can be synchronised to the exact second. Alarm accuracy to the exact minute. Wide display last minute digit and seconds. Solid state reliability, silent running. 9 minute snooze. Alarm on, Mains Failure Indicators. **C500** (left) 3½" × 3½" × 2¾". Black or white **£16·95.** C5110 (centre). As C500 but more sophisticated controls **£19·95. C590** (right). With built-in High/Low intensity elevating reading lamp **£23·33.**

402 ES

405 ILB

700

From **NATIONAL SEMICONDUCTOR** 5+3 functions. As Timeband but without alternating Time/Date facility. DAC3 series (left).

DAC3 WS Chrome on Strap **£22·90**
DAC3 YS Gold Plate Strap **£25·90**
DAC3 WB Chrome Bracelet **£24·90**
DAC3 YS G.P. Bracelet **£28·50**
DAB5 Series (Right)
DAB5 WB All stainless **£33·50**
DAB5 YB Heavy G.P. **£39·50**

IBICO. Traditional Swiss craftsmanship. 5+4 functions LCD. Mineral Glass face. **405 ILB** strap **£33·95, 405 ILB** Si/St bracelet **£35·50. 402 ELB** Stainless steel on strap **£30·90. 402 ES** All stainless **£29·90. 700** "1000 day" Quartz Analogue. Stepping Motor. High speed adjustment. Seconds synchronisation. **£25·90.** Not illustrated **400 RIB £39·75. 403 RIB £42·50.** IBICO watches are water resistant to 100 feet or more. (Waterproof straps).

W/T 6F. 6+3 function LCD. Metal case, S/S bracelet. Superb styling **£11·95. INSTAL** 2½ function LCD. Gold plated & matching bracelet **£9·95.**

CALCULATORS. FX-25 £19·95. FX-29 £14·95. FX-105 £19·95. FX-115 £17·95 (Rechargeable batteries £3 pair. AC adaptor/charger £3). **FX-2000 £24·95, FX-201P £44·95, FX-3900P £58·95, PRC-FX1 £134·95.**

Send 15p for our illustrated mail order catalogue of over 50 watches (Accurist, Timex etc) clocks, car clocks. The BEST T.V. games at LOWEST prices. Prices include VAT P & P. Credit cards welcome or send cheque, P.O. to:—

TEMPUS Dept P.W.
19-21 Fitzroy Street
Cambridge CB1 1EH
Telephone (0223) 312866

Wilmslow Audio

THE firm for speakers!

SEND 10P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

ATC ● AUDAX ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GAUSS ● GOODMANS ● HELME ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER MCKENZIE ● MONITOR AUDIO ● PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● TANNOY ● VIDEOTONE ● WHARFEDALE

WILMSLOW AUDIO (Dept. P.W.)
SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF
Discount HiFi Etc. at 5 Swan Street and 10 Swan Street
TEL: WILMSLOW 29599 FOR SPEAKERS
WILMSLOW 26213 FOR HIFI

TRAMPUS ELECTRONICS LTD

BARCLAYCARD

Buy it with Access

A SEMICONDUCTOR POWERHOUSE (Trade & Export Welcome). **TRAMPUS ELECTRONICS LTD., 58-60 GROVE RD., WINDSOR, BERKS. SL4 1HS. Tel: Windsor (07535) 54585. Callers welcome Mon-Sat 9am-5pm** Fast service. Same day despatch on ex stock product. Quality devices, all full spec. Same Trampus low prices. Barclaycard and Access by post or telephone £5 minimum. VAT: Add 8% to prices marked *. Add 12½% VAT to all other prices. Post and packing 20p U.K. Send C.W.O. except Gov Depts etc. Free catalogue list with sale bargains & micro processors (send S.A.E.).

IC's. All price each
555 DIL 8 pin timer 38p*
723 TO99 regulator 45p*
723 DIL 14 pin reg. 45p*
741 DIL 8 pin op amp 28p*
741 DIL 14 or TO99 39p*
747 Dual 74l 88p*
748 DIL 14 pin 33p*
748 DIL 8 pin 45p*
7805 TO3 5V reg. £1·00*
7805 Plastic 5V Reg. £1·33*
7812 or 7815 £1·50*
78015 or 7809 AF £1·60
8038 Signal Gen. £1·90*
LM300 £1·00*
LM301 DIL 14 pin OPA 38p*
LM301 DIL 8 pin OPA 38p*
LM309K TO3 5V Reg. £1·00*
LM319 70V US OPA £2·25*
LM380N 2W AF 1V £1·00*
LM381 2 × Pre amp £2·00*
LM3900 Quad op amp 75p*
NE536 FET OPA £4·90*
NE555 Timer 39p*
NE556 2 × 555 timer £1·00*
SN76 110 1 & 00 IF £1·25
TBA 810 7W AF £1·60

LEDS ⅛" & 2" DIA.
Red no clip 12p*
TIL209 & clip 26p*
2" Red & LEDs 17p*
Coloured LEDS 11p

DISPLAYS (Red Led)
0·3" DL704/ DL707 £1·69*
0·6" DL747 Jumbo £1·69*
Data PCB Pen. £5·95*
2 Tips 74p*
Decoon Desolder Braid Reel 74p*
SRBP 6" × 4" 6DP. FEC Tub £1·00*

TRANSISTORS
AD161, 162 os 98p*
SC107 18p*
SC107B 18p*
SC108 18p*
SC108 B or C 18p*
SC109 18p*
SC109 B or C 18p*
SC147/8/9 18p
SC167/8/9 18p
SC177/8/9 30p*
SC182/3/4 A or L 18p
SC212/3/4 A or L 18p
SC167/177/8 30p*
BD131 or 132 es 59p*
BFY90 or 51 £1·00*
MJ2955 (PNP 3055) £1·65*
MJE2955 £1·45*
MJE3055 65p*
ORP12 60p*
OCP71 or 42A 60p*
TIP2955 65p*
TIP3055 80p*
TIS43 38p*
2TX107/8/9 18p*
2N3646 59p*
2N3646/9 39p*
2N3906 rbo 15p
2N3926Y/G 15p

2N3053 35p*
2N3055 49p*
2N3702/3/06 19p*
2N3704 9p*
2N3818 & FET 18p
2N3820 FET 69p*
2N3904/5/6 39p
2N5457 FET 59p*
2N5777 OPTO 99p*

SILICON GREASE
Mini satchet 25p*
Ins. Bush sets 10p*
Matching 20p*

TTL
7400 14p*
7401 14p*
7402 18p*
7403 18p*
7410 29p*
7413 39p*
7430 29p*
7437 39p*
7440 29p*
7441 89p*
141 79p*
7442 89p*
7470, 72, 73, 74, 76 29p*
7472, 74 35p*
74 35p*
7475 65p*
7476 39p*
7483 89p*
7485 89p*
7490 89p*
7491 89p*
92 79p*
74121 33p*
74123 89p*
74190/1 89p*

CMOS
4001/2 29p*
4006/10
4011 35p*
4013
16 99p*
4017
20 £1·29*
4024 89p*
4026 £2·49*
4029 £1·25*
4040 89p*
4042 89p*
4047 £1·49*
4049 59p*
4050 59p*
4066 £3·29*
4067 £3·99*
4071 or 4Ø2A 49p*
4511 £1·75*
4528 £1·62*
4553 £5·99*
CMOS data book £2·50

DISCO TRIAC 10A
400v £1·99*

RSC 100 WATT DISCO SYSTEM

AT A FANTASTIC LOW PRICE

Consisting of
(1) TWIN T/TABLE CONSOLE with PRE-AMP, and POWER OUTPUT STAGES
(2) & (3) PAIR 100 WATT LOUD-SPEAKERS including 12" UNITS

Rec. Mic. UD 150 Cardioid **£9·95** extra with system only

- ★ DISCOMAJOR 200 POWER DISCO CONSOLE with integral Power Amplifier.
- ★ TWIN FULL SIZE GARRARD turntable with cueing device.
- ★ CARTRIDGES with Diamond Stylí
- ★ 3 SEPARATE VOLUME CONTROLS for each turntable and Mic.
- FULL HEADPHONE MONITORING FACILITIES
- CONSOLE COMPLETE WITH LID

Terms: Deposit £40·00 and 12 monthly payments £15·60 (Total £327·20) Carr. £7·50.

Also available **100 WATT SYSTEM** with Dynamic Stick MICROPHONE **£169·95**

£199·95

ALL RSC PRICES INCLUDE VAT

TD1 DISCO CONSOLE

Incorporating twin BSR type turntables and Sonotone or Acos Cartridges with diamond styli. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate Input for 'mike' with vol. control. Black Vynide covered

Cabinet with lid **£109·95**

Dep £16·49 & 18 f'tnly pymts. £6·11 (Total £126·47) Carr. £3.

TD2 STEREO VERSION OP ABOVE £129·00

Terms DEPOSIT £20 and 18 fortnightly payments £6·89 Total £144·02) Carr. £3

40W SYSTEM £169·95. 100W SYSTEM £199·95

OTHERS UP TO 300 WATTS AT UNBEATABLE PRICES

WRITE OR PHONE for Free Catalogue

DISCOMAJOR/100 TWIN TURNTABLE POWER CONSOLE £129·95

Twin Full size BSR turntables. Sonotone or Acos Carr. £3·00 Cartridges with Diamond Stylí. Facilities as TD1 Console but with built-in 100 watt Power Amplifier complete with lid. Terms: Deposit £19·95 and 18 fortnightly payments £7·03 (Total £146·49).

DISCOMAJOR/200 £149·95

200 watt version of above. Terms: Dep. £29·95 and 18 fortnightly payments £7·87 (Total £171·61)

RSC PHANTOM 50 COMBO AMP. £69·95

Rating 50 watts. 3 inputs, 2 vol controls—Bass, Treble Presence. Suitable for Lead or Rhythm Guitar, mic., Radio, Tape, etc. Inc. High Flux 12" 50w Speaker. Dep. £10·95 & 8 mthly payments £8·71 (Total £80·63). Carr. £1·50.

100W POWER (SLAVE) AMPLIFIER

Suitable for use with DISCO-Consoles. Also for increasing output of lower-powered Amp. Dep. £9·00 and 8 mthly pyts of £6·05 (Total £57·40) Carr. £1·50

100 + 100W MODEL £69·95 **£49·95**

Carr. £1·50

TITAN TA/50A 50W AMPLIFIER

Solid state, 3 sep. controlled inputs plus Master control. Bass, Treble & Presence Controls. Vynide covered cab. with corner protectives. List price £60. Terms: Dep. £9 & 8 monthly payments £6·05. (Total £57·40) Carr. £1.

£49·95

Matching Cabinets 1 × 12" £29·95 2 × 12" £49·95

TITAN TA/100A 100W AMPLIFIER

TWIN CHANNEL—4 INPUTS (NORMAL OR BRIGHT) A De-luxe professional unit with many facilities. R.M.S. Rating. Matching 1 × 12" 120w Cabinet speaker £49·95 with above only. Carr.£1·50

£69.95

Carr. £1·50

INTEREST REFUNDED on Credit Purchases settled in 3 mths

TITAN 'ADD-ON' HIGH FREQUENCY HORN UNITS

MODEL TS2H

Inc. Pair of highly sensitive Horns. Range 3-15 kHz Imp 16Ω. Use with 8 or 15Ω 2 × 12" or 1 × 15" or 18" Drive Unit for increased sound clarity and projection. Rating 100 watts.

Either model **£27·95** Carr. 75p

Terms: Dep £6·95 & 8 mthly pyts £3·12 (Total £31·91)

MODEL TH With single super efficient Horn. Range 3-15 kHz. Imp 8Ω. Use with max 8Ω 2 × 12" or single 15" or 18" 8Ω Drive Units. Maximum amplifier power output to be 100 watts.

Compatible with units at twice 250-350v. 80w. £9·90: 150w. £8·90; 200w £8·07: 300w £9·04. the cost.

RSC MAINS TRANSFORMERS

TYPES FOR VALVE RADIOS & AMPLIFIERS (Inc. L.P. CHOKES & OUTPUT TRANSFORMERS. As previously advertised still available.

FILAMENT OR TRANSFORMER POWER PACK TRANSFORMERS 0-110/150v 200-

AUTO (STEP UP/STEP DOWN)

10v. 1a. £2·10, 6·3v. 1·5a £1·66, 6·3v. 2a £2·10, 6·3v. 3a £2·50, 6·3v. 4a £3·00, 10v. 3a or 5a £3·50, 12-0-12v. 1a. £2·95, 0-10-12-20v. 2a £3·19, 0-10-12-20v. 3a £3·50, 0-10-12-20v. 4a £3·90; 2a £2·95; 5a £3·84. 6a. £3·19; 8a £3·49.

200-250v. 80w. £9·90: 150w. £8·90; 200w £8·07: 300w £9·04.

FANE HIGH POWER SPEAKERS

Power ratings R.M.S. Cont. 2 YRS GUARANTEE *Gauss 14000 imp 8–16 ohms. CARR. FREE.

POP 33T 12" 33w £13·95 Dual cone.

***POP 50/2 12" 50w £15·99** Dep for Pair £8·00 and 8 monthly pyms £3·54 (Total £36·32)

***POP 75 12" 70w £19·99** Gauss 17,000 lines. Dep £9·00 and 8 mthly pyms £3·98 (Total £40·94)

***POP 60 15" 60w £25·95** Dep £7·00 & 8 monthly pymts £2·67 (Total £29·96)

***POP 100 18" 100w £44·95** Dep £10·00 & 8 monthly pymts £5·17 (Total £51·36)

TITAN GROUP/DISCO SPEAKERS

Carr. £1, under £18, over this add 5p per £1.

	List	RSC Price
T12/45 12" 45w	£15·80	£11·95
T12/60A 12" 60w	£21·00	£13·95
T12/100 12" 100w	£36·00	£24·95
T15/60 15" 60w	£26·00	£18·99
T15/75 15" 70w	£28·00	£19·95
T15/100 15" 100w	£41·00	£29·95
T18/100 18" 100w	£47·00	£35·95

GUARANTEED FOR 5 YEARS

Rating RMS Imp 8-15 ohms

CABINETS FOR ABOVE SPEAKERS Heavy duty. Beautifully finished in black Vynide with Vynair fronts fitted protective corner pieces. Various sizes and cut-outs. TE1 1 × 12" £10·95. Low Deposit Terms on orders over £20 TE2 2 × 12" £16·95

Stockist of Lighting by PULSAR Equipment by CARLSBRO Full range of speakers by FANE

TITAN TA/100C COMBO

100w R.M.S. Amp. incorporating a fabulous Fane Crescendo 12" 100 watt spkr for really superlative results with Lead Guitar

Carr. £5 **£119·95**

Or Dep £17·95 & 18 f'tnly payts £6·69 (Total £138·37)

FANE HIGH FREQUENCY HORNS 'J' SERIES

All Carr Free

MODEL J44 Imp 8Ω Size approx. 3¼" × 3¼" × 3¼" Rating 30-50 watts Range 3-15 kHz **£7·95**

MODEL J73 Imp 8Ω Size approx 7¼" × 3" × 6¼" Rating 50 watts Range 2-20 kHz **£11·75**

MODEL J104 Imp 8Ω Size approx 10½" × 3½" × 7¼" Rating 50-70 watts Range 2-15 kHz **£15·50**

FAL DISCO LIGHTING SYSTEMS from £58.95

Incl 2 Spotbanks and bulbs

JINGLE MACHINES from £37·95

ECHO CHAMBERS from £53·95

COLUMN SPEAKERS from £29·95

GROUP DISCO SPKRS in CABINETS from £11·95

FREE FANE HIGH POWER 'CROSS-OVER' WITH ANY OF ABOVE.

Impedance or total impedance of 12", 15" or 18" Drive units must not exceed impedance of single horn or pair in series. Pair J44, Single J73 or J104 suitable for amplifier power up to 100 watts subject to above and with HPX2 'Cross-over'

Barclaycard & Access PHONE ORDERS quoting CARD NUMBER accepted

BARCLAYCARD VISA

MAIL ORDERS & EXPORT ENQUIRIES TO:— AUDIO HOUSE, HERCOMBE LANE, LEEDS, 13. Tel: 0532 579565.

MAIL ORDERS MUST NOT BE SENT TO SHOPS

TERMS C.W.O. or C.O.D. No C.O.D. under £5. POSTAGE for ITEMS ORDER OR AS QUOTED. Phone or Write for FREE CATALOGUE.

New Branches at HANLEY WOLVERHAMPTON and LIVERPOOL

OPEN ALL DAY SATURDAYS (6 Day Week)

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349

BOLTON 23 Deansgate, (Closed Wed.). Tel. 33512

BIRMINGHAM 6/8 Great Western Arcade, Tel. 021-236 1279 (Closed Wed.)

CARLISLE 8 English Street (Closed Thurs.). Tel. 28744

COVENTRY 17 Shelton Sq., The Precint. Tel. 25983

DERBY 97 St. Peter's Street (Closed Wed.). Tel. 41361

DARLINGTON 19 Northgate (Cl. Wed.). Tel. 68043

DEWSBURY 11 Crownest Chambers (Closed Wed.). Tel. 469610

DONCASTER 3 Queensgate, Waterdale Centre, (Closed Thurs). Tel. 63069

EDINBURGH 101 Lothian Rd. (Cl. Wed.). Tel. 229 9501

GLASGOW 326 Argyle St. (Cl. Thurs.). Tel. 248 4179

All items subject to availability. Prices correct at 18.7.77 E. & O.E.

HANLEY Stoke-on-Trent, 44 Piccadilly

HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505

LEICESTER 28 High Street (Closed Thurs.). Tel. 56420

LEEDS 5-7 County (Mezzo) Arcade, Briggate (Closed Wed.). Tel. 458282.

LIVERPOOL 33 Dawson's Way, St. John's Shopping Centre. Tel. 709 6780 (Cl. Wed.).

LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1569

MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2778

MIDDLESBROUGH 103 Linthorpe Rd. Tel. 247095 (Closed Wed.)

NEWCASTLE UPON TYNE 59 Grainger St. (Closed Wed.). Tel. 21469

NOTTINGHAM 19/19A Market Street

PRESTON (Closed Thurs.). Tel. 49088

41 Friargate Walk, St. Georges Shopp Prec. Tel. 51979

SHEFFIELD 17 Exchange Street (Castle Mkt. Side.) (Closed Thurs.). Tel. 20716

STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-5777

SUNDERLAND 5 Market Sc. (Closed Wed.). Tel. 70573

WOLVERHAMPTON 6, Waifrun Way (Cl'd Thurs.) Tel. 25812

INVERTORS

KIT FORM or BUILT UP.

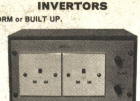

240v-50Hz from your 12v car battery.

O/P Powers available. 25W–40W–75W–150W–300W–400W–500W–1kW–1 5kW. Various battery I/P voltages available.

AUTOMATIC INVERTORS

These units have built-in battery charger which functions whilst mains are healthy. Upon mains failure unit automatically switches to invertor operation ensuring no interruption of supply. Send S.A.E. for price lists.

RHYTHM GENERATOR

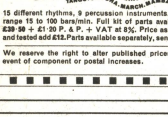

15 different rhythms, 9 percussion instruments. Tempo range 15 to 100 bars/min. Full kit of parts available at £39·90 + £1·20 P. & P. + VAT at 8%. Price assembled and tested add £12. Parts available separately, send S.A.E.

We reserve the right to alter published prices in the event of component or postal increases.

P.E. ORION STEREO AMPLIFIER & TUNER

May be mounted slim line or stacked as above. Parts available separately for both units.

20 + 20 Watts r.m.s. into 2 ohm load. Distortion less than 0·1% 100Hz–10kHz. Frequency response ± 1dB 20 Hz to 25kHz. Hum level virtually nil with volume full on. This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.

TUNER UNIT

May be purchased separately in matching slim line case. As full kit or individual parts.

Send S.A.E. for price list and specification sheets.

LOUDSPEAKERS

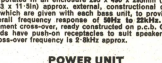

8 inch system

This system is designed for use with above amplifiers rated up to 25W r.m.s. per channel at 8 Ω. May be incorporated in an enclosure 295 x 490 x 295mm (11·5 x 19·3 x 11·8in) approx. external, constructional details of which are given with each bass unit, to provide an overall frequency response of 50Hz to 25kHz. Four-element cross-over, ready constructed on p.c.b. Output leads have push-on receptacles to suit speaker tags. Cross-over frequency is 2·8kHz approx.

POWER UNIT

Regulated

Voltage adjustable from 1–35v at 2 amps. Short circuit protected. Voltage and current meters incorporated. Full Kit of parts £48 + 8% VAT or assembled and tested £58 + 8% VAT.

ASTRO IGNITION

SAVE FUEL

Complete kit of parts for this proven and tested system. (£51·90 + 60p P. & P.) + 8% VAT or ready built with only two connections to alter.

(£64·90 + 60p P. & P.) + 8% VAT.

Consider the advantages:

Fuel economy. Faster acceleration. More power. Excellent cold starting. Smoother running. No contact breaker burning. Less exhaust gases.

TRANSFORMERS

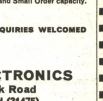

SPECIAL OFFER

Miniature Mains Trans.

6-0-6v-4VA.

12-0-12v-4VA.

(£1·29 + 25p P. & P.) + 8% VAT

Transformer and coils manufactured to customer specifications both in High Volume and Small Order capacity.

TRADE AND EXPORT ENQUIRIES WELCOMED ON ALL PRODUCTS:

ASTRO ELECTRONICS
Springbank Road
Chesterfield (31475)
Derbyshire

N.B.—DELIVERIES ON ALL ITEMS MAY TAKE UP TO 28 DAYS, DEPENDING ON AVAILABILITY AND DEMAND. CASH IN REGISTERED ENVELOPE OR POSTAL ORDERS CAN REDUCE TIME by NOT HAVING TO CLEAR CHEQUES

LEKTROPAKS

17 TURNHAM GREEN TERRACE, CHISWICK, LONDON W.4. Tel. 01-994 2784

★ LARGE RANGE OF COMPONENTS NOW STOCKED. SEND LARGE S.A.E. FOR FREE LISTS.

******* SPECIAL OFFERS *******

QTY.		
12	4.7μF, 25V, BEAD TANT	£1·00
50	·01μF, 50V, MIN DISC CERAMIC	£1·00
1	TGS 105 GAS SENSOR	£2·25
Any 10	BC 107, 147, 148, 182, 183	£1·00
Any 10	BCY 70, 71, 72	£1·50
8	SN 7400	£1·00
15	1μF, 250V, C280 CAPACITOR	£1·00

ALL PRICES INC. VAT. PLEASE ADD 20p P.P.

****

★ WALK-ROUND SELF-SERVICE SHOP NOW OPEN MON-SAT 9.30–5.30.

★ MANY SURPLUS COMPONENT BARGAINS FOR PERSONAL CALLERS.

★ RESISTORS, CAPACITORS, TRANSISTORS, DIODES, TRIACS, DIACS. IC's, POTS, ALI BOXES, VERO, COPPER CLAD BOARD, CABLE, AUDIO CONNECTORS, SPEAKERS, MICROPHONES, P.A. TRANSFORMERS, KNOBS, ETC, ETC.

Random FLASHER UNIT

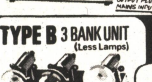

Wired ready for use
Complete with three 100 watt coloured lamps that flash independently at random
£18·95

TWIN BANK 6 LIGHT UNIT

(less lamps) LENGTH 14½ inches

B.C. Fitting £9·55 EACH
E.S. Fitting £10·35 EACH

Sound to Light MASTER UNIT

600 WATTS PER CHANNEL

£30·95
INCLUDING CHANNEL OPTPUT PLUGS AND MAINS INPUT SOCKET

TYPE A SPOT

(less lamp)

B.C. Fitting £1·95 EACH | E.S. Fitting £2·12 EACH

TYPE B 3 BANK UNIT

(Less Lamps)

B.C. Fitting £6·90 EACH | E.S. Fitting £7·26 EACH

TWIN BANK 12 LIGHT UNIT

Length 31¾"

(less lamps)

B.C. Fitting £15·60 EACH | E.S. Fitting £17·00 EACH

100 WATT SPOT LAMPS RED, YELLOW, GREEN BLUE, CLEAR £1 · 40 each B.C. or E.S. Fitting

Minimum 3 lamps £4·20

ALL PRICES INCLUDE VAT and POST & PACKING (Terms strictly C.W.O. to the United Kingdom only)

Send 20p for illustrated leaflet & price list.

ALBEN ENGINEERING CO LTD.,
DEPT. P.W. THE CRESCENT, WORSTHORNE, BURNLEY, LANCS. Tel. Burnley 20940

DIY SPEAKER KITS

15-WATT KIT IN CHASSIS FORM

When you are looking for a good speaker, why not build your own from this kit.

It's the unit which we supply with the enclosures illustrated below Size 13" × 8" (approx.) woofer (EMI),tweeter, and matching crossover components. Power handling capacity 15 watts rms. 30 watts peak.

£17.00 PER STEREO PAIR + P & P £3.40

EASY-TO-BUILD WITH ENCLOSURE

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two task-simulate enclosures, two EMI 13" × 8" (approx.) woofers, two tweeters and a pair of matching crossovers. Easily constructed, using a few basic tools. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms. 30 watts peak. unit. Cabinet size 20" × 11" × 8½" (approx.).

£25.00 PER STEREO PAIR + p & p £5.50

COMPACT' FOR TOP VALUE

How about this for incredible bookshelf value from RT-VC! A pair of high efficiency units for only £7.50 – just what you need for low-power amplifiers. These infinite baffle enclosures come in ready mitred and professionally finished. Each cabinet measures 12" × 9" × 5" (approx.) deep, and is in wood simulate. Complete with two 8" (approx.) speakers for max. power handling of 7 watts.

per stereo pair **£7.50** + p & p £1.70

SPEAKERS Two models – Duo Ilb. task veneer, 12 watts rms, 24 watts peak, 18½" × 13½" × 7½" (approx.).

£34 PER PAIR + p & p £6.50

Duo Ilb. 30 watts rms, 40 watts peak, 27" × 13" × 11½" (approx.)

£52 PER PAIR + p & p £7.50

EASY TO BUILD RECORD PLAYER KIT

Ideally suited for the constructor who requires a complete stereo unit at a budget price, comprising ready assembled stereo amp. module, Garrard auto/manual deck with cueing device, pre-cut and finished cabinet work. Output 4 watts per channel, phones socket and record / replay socket

£26.95 + p & p £4.05

CAR RADIO KIT

Complete with speaker, baffle and fixing strip. The Tourist IV for the experienced constructor only. The Tourist IV has five push buttons, four medium band and one for long wave band. The tuning scale is illuminated and attractive small aluminium control knobs are used for manual tuning and volume control. The modern style fascia has been designed to blend with most car interiors and the finished radio will slot into a standard car radio aperture.

Size approx. 7" × 2" × 4½". MOTOR TOP 10 AWARD

Power Supply Nominal 12 volts positive or negative earth (altered internally) Power Output 4 watts into 4 ohms.

£12.50 + p & p £1.50

PERSONAL SHOPPERS ONLY

Viscount IV 20 x 20 Amplifier as illustrated, plus 1 pair of speakers finished in teak with melamine panels 8" drive unit and 3½" square tweeter. 22" × 13" × 10½" size approx.

£45.00

SPECIAL OFFER

illustrated **20 x 20 WATT STEREO AMPLIFIER**

Superb Viscount IV unit in teak-finished cabinet. Silver fascia with aluminium, rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic. magnetic and crystal pick-ups, tape, tuner, and auxiliary Rear panel features two mains outlets. DIN speaker and input sockets, plus fuse. 20 + 20 watts rms, 40 + 40 watts peak.

£29.00 + p & p £2.10

FREE "Limited Period" A Free 4 Channel Stereo Adaptor to all purchasers of the Viscount Amplifier. Available separately. **£3.95** + p & p £1.00

SPECIAL OFFER for example, Duo Speaker system II or II Viscount Amplifier, MP60 type turntable complete

DEDUCT 10% DEDUCT 15%

On complete stereo systems using starred Products

PERSONAL SHOPPERS ONLY

PLINTH & COVER BSR OR GARRARD TEAK FINISH **£4.95**
GOODMAN 5" approx. 7 watt bass speaker **£2.70**
ARM. FM. TUNER P.C.B. with Multiplex L.P. 1186, 1186.1181 modules **£5.50**
CROWN 1 watt Bulton car radio, AC. MW. 12v Pos. neg. earth 5 watts **£12.95**
output, tone control complete with speaker and fixing kit, in dash type
STEREO CASSETTE TAPE PLAYER Negative earth only, 3 watts **£16.95**
per channel output
AM. FM. STEREO MULTIPLEX CAR RADIO/cassette player in **£36.00**
dash fixing Negative earth 5 watts output
I.C. Stereo 8 Track to Cassette adaptor converts, any 8 track **£18.95**
player to cassette player.
GLOBAL Spherical speaker 8 ohms. 5 watts **£3.50**
100K Miniature Volume tuning pots 6 for **£1.00**
HEAVY DUTY FIBRE GLASS COPPER CLAD BOARD **£1.00**
27" × 17" + ½" Approx. per sheet, only
DECCA DC1000 Stereo Cassette Record deck P.C.B. complete with **£2.95**
switch oscillator coils and tape-heads and circuit diagrams.

VISCOUNT COMBI £65.00

For personal shoppers only, this unit comprises : The 20 + 20 Viscount amplifier BSR MP60 Type turntable housed in an attractive teak finished console with smoked acrylic cover. Approx. 30½" × 14½" × 7½" complete ready to connect to the speaker system of your choice.

callers only

BSR TURNTABLES

BSR MP60 TYPE
Single play record player (Chassis form) **£15.95**
less cartridge. P & P £2.00

Cartridges to suit above ACOS MAGNETIC STEREO **£4.95**
CERAMIC STEREO **£1.95**

BSR automatic record player deck (Chassis form) with cueing device and stereo ceramic head. **£9.95**
P & P £2.00

TURNTABLE illus. Popular BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover. Ready wired

£29 + p & p £4.50

30 x 30 WATT AMPLIFIER KIT

Specially designed by RT-VC for the experienced constructor, this kit comes complete in every detail. Some facilities as Viscount IV amplifier. Chassis is ready punched, drilled and formed Cabinet is finished in teak veneer, Silver fascia and easy-to-handle aluminium knobs.

Output 30 + 30 watts rms, 60+60 peak. **£29.00** + p & p £2.10

DECCA 20 WATTS STEREO SPEAKER

This matching loudspeaker system is hand made, kit comprises of two 8" diameter approx. bass drive units, with heavy die cast chassis laminated cones with rolled P.V.C. surrounds, two 3½" diameter approx. domed tweeters comp with crossover networks + £4.00 p & p stereo pair **£20.00**

Order giving your credit card number ONLY

ALL PRICES INC. VAT AT 13½% GOODS NOT DISPATCHED OUTSIDE UK
All items subject to availability. Price correct at 4/7/77 and subject to change without notice.
We are unable to show all our products, so Send stamped addressed envelope for our fully descriptive catalogues and any further information.

ACCESS BARCLAYCARD

R T V C

323 EDGWARE ROAD, LONDON W2
Personal Shoppers 1000 EDGWARE ROAD 9.30am–5.30pm. Half day Thurs.
21C HIGH STREET, ACTON, LONDON W3 6NG
ACTON: Mail Order only No callers

PORTABLE MONO DISCO

with built-in pre-amplifiers

Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. p & p £6.50

Simply connects into your existing sleeve or external amplifier. **£64.00**

35-WATT MONO DISCO AMP

£27.50 + p & p £2.50

Size approx 13" × 5½" × 6½"

Here's the mono unit you need to start off with. Gives you a good solid 35 watts rms, 70 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

100 WATT MONO DISCO AMP

Size approx. 14" × 4" × 10½".

Sloping facia,you can use the controls without fuss or bother. Brushed aluminium fascia and rotary controls. Five smooth acting, vertically mounted slide controls – master volume, tape level, mic level, deck level, PLUS INTER-DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control (PFL) lets YOU hear next disc before fading **£65.00**

it in. VU meter monitors output level.

Output 100 watts RMS 200 watts peak. p & p £4.00

PRACTICE GUITAR AMPLIFIER WITH BUILT-IN SPEAKER

This budget practice amplifier, has been specially designed for the amateur, who requires a quality self-contained unit with all facilities. 2 inputs – 1 for mic or guitar, the 2nd for record player or cassette deck, it also can be used for cine-sound amplification. 2 volume controls, 1 for each input, also base and treble controls. Power output with internal speaker, 10 watts RMS, with remote speaker (not supplied) 20 watts RMS. Size approx. 17" × 9" × 11". **£32.00** + p & p £3.00

HOME 8 TRACK CARTRIDGE PLAYER

Automatically switches programmes monitored by indicators, with manual override track selection. This unit will match with the Unisound modules and is compatible with the Viscount IV amplifier with Sim teak cabinet. approx. 9" × 8" × 3½" p & p £1.50 **£14.00**

4 x 4 STEREO AMP KIT £14.50 P & P £2.00

For the experienced constructor, who wants to design his own stereo. Kit includes all necessary components including constructors manual. Plus Pair of easy to build 4 watt speakers in kit form, with teak simulate finish cabinets 12" x 8" x 5" approx.

PYE STEREO GRAM CHASSIS

(Complete with circuit-diagrams)

Complete ready to install–Wave bands LM, VHF STEREO, VHF MONO. Controls for tuning volume, balance, bass and treble. Power output 7 watts R.M.S per channel 14 watts peak 8 ohms.

2" × 8" approx chassis speakers and BSR auto record player deck.

PERSONAL SHOPPERS ONLY **£35.00**

Newnes 2 new books Technical

LATEST TITLE in The Master Series

Master Creative Tape Recording

by JOHN GARDNER

In this book the theory of recording and reproduction is covered, as well as the choice of your machine and microphone, improvising a studio, and setting up of equipment. Guidance is given on the general organisation of recording sessions, and on the problems of recording drama, features and music, and of tape editing.

CONTENTS: Recording and reproduction. Choosing a suitable machine. Choice and use of microphones. Mixers, monitoring and installation. Improvising a studio. Organisation and method. Drama and features. Music. Editing. Appendix. Index.

May 1977 140 pages £2.50

Other titles in the Master series : Master In-Car Entertainment – Capel. Master Electronics in Music-Towers. Master Hi-Fi Installation – King. Master Stereo Cassette Recording – Sinclair.

LATEST TITLE in The Beginner's Guide Series

Beginner's Guide to Audio

by IAN R. SINCLAIR

Covers the working principles of devices ranging from the microphone to the louspeaker and examples of the electronic circuits which are used. Starting with the behaviour of sound waves the text continues with chapters on microphones, pickups, preamplifiers and amplifiers and loudspeakers.

CONTENTS : Sound and recording. Replay and Reception. Voltage amplifiers. Equalisation, filtering and tone controls. Output stages. Loudspeakers. Recording and reproduction systems. Index.

April 1977 192 pages £2.75

Other Beginner's Guides in Electronics : Beginner's Guide to Electronics –Squires & Deason. Beginner's Guide to Radio – King. Beginner's Guide to Transistors – Reddihough & Sinclair.

ORDER NOW

ORDER NOW from your bookseller or in case of difficulty from **BUTTERWORTHS, Borough Green, Sevenoaks, Kent TN15 8PH**

Your career in Electronics?

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, WD9/7
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

_____ (Block caps please)

VALVE BARGAINS

Any 5-64p, 10-£1·20, 50-£3·00. Your choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL86, PCL805, PL504, PY81/800, PY88, 30PL14, 6F28, PFL200.

Colour Valves—PL508, PL509, PL519, PY500/A. All tested. 35p each.

Aerial Splitters—2 way, 75 OHMS, Inside Type, £1·50

AERIAL BOOSTERS

Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

B11 For THE stereo and standard VHF/FM radio.

B12—For the older VHF television —Please state channel numbers.

B45—For Mono or colour this covers the complete UHF Television band.

All boosters are complete with battery with Co-ax plugs & sockets. Next to the set fitting. **£4·20**

Press Button UHF Tuners—4 Button Transistor—British made—£2·50 each.

250,000

CAPACITOR CLEARANCE SALE

All Mullard C280 and C281 range of Polyester film capacitors 250 and 400 volts working. Very good mixed selection of values from ·01μf to 1·5μf.

PRICE 100-£1·50, 500-£7·00, 1,000-£12·00.

All prices include VAT. P&P 30p per order. Please send uncrossed P.O. or cheques for returning if we are out of stock of capacitor bargain packs. Exports welcome at cost.

ELECTRONIC MAILORDER LTD.
62 BRIDGE STREET, RAMSBOTTOM, BURY, LANCS.
TEL: RAMS (070 682) 3036.

SAXON ENTERTAINMENTS LTD

SYSTEM 7000—GUARANTEED MODULES FOR ALL DISCO/PA APPLICATIONS

POWER AMPLIFIER MODULES 30—240 WATTS

- Fully tested & guaranteed.
- Full RMS Sine Wave output.
- Distortion typically 0·2%.
- 10 Transistors, 4 Diodes.
- Response 30HZ-30KHZ.
- Fully short & open circuit proof
- Sensitivity suits most mixers
- Built-in surge suppression & compensation
- Twin D.C. & output fuses.
- Top-grade components throughout.

30 Watts rms	60 Watts rms		120 Watts rms		240W rms
SA308 30W rms/ 8 ohms £9·50	SA604 60W rms/ 4 ohms £13·50	SA608 60W rms/ 8 ohms £13·50	SA1204 120W rms/ 4 ohms £14·50	SA1208 120W rms/ 8 ohms £21·00	SA2404 240W rms/ 4 ohms £35·50

POWER SUPPLIES FOR THE ABOVE MODULES—READY WIRED & FUSED ON GLASS FIBRE PCB

PM301 For 1/2 SA308 £9·90	PM601/4 For 1/2 SA604 £12·50	PM601/8 For 1/2 SA608 £12·50	PM1201/4 For 1 SA1204 £12·50	PM1201/8 For 1 SA1208 £12·50	PM1202/4 For 2 SA1204 £19·50	PM1202/8 For 2 SA1208 £19·50	PM2404/1 For 1 SA2404 £19·50

SYSTEM 7000 COMPLETE DISCO MIXERS (with Autofade)

Mono or Stereo

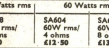

- Ready to plug in & use
- Automatic Mic override
- Two tone panel
- Twin deck & mic & tape inputs
- Left/Right deck fader
- 20Hz-20kHz Noise —77dB

The choice of the professional D.J.

Controls: Mic volume, Bass, Treble, A/Fade Depth, Tape, L/Deck, R/Deck volumes, Bass, Treble, Master, Headphone volume, Selector & On/Off.

Mono 18v **£37·50** Mains **£43·50** Stereo 16v **£53·50** Mains **£59·50**

IN MODULAR FORM—All you require is front panel (see below) knobs & sockets, Mains etc. All electronics are assembled & tested.

- Specification as for complete mixer
- All Potentiometers supplied & fitted
- Low cost do it yourself with step by step easy to follow instructions.

Mono **£19·50** Stereo **£29·50** Panel **£3·50** Supply unit **£8·50**

SYSTEM 7000 LIGHTING CONTROL UNIT MK II (Four channel)

Has your light unit got?

- 4,000 W handling
- Sequence facility
- Smart 2 tone panel
- Advanced IC circuitry
- Top grade components

All your needs in the superbly designed unit

- Integral dimmers
- Automatic audio level

OURS HAS!

ONLY £42·50

IN MODULAR FORM—THE QUADRAFECT **£29·50** (Panel £2·50)

As with the mixers the MK II L.C. unit may be purchased in module form with all controls, requiring only a panel, case & knobs etc. There are 13 simple connections.

- 1-240w Audio
- 8A RCA trixes
- 0·5-20Hz Sequence
- Fully suppressed

CUSTOM MIXER MODULES (Complete or in printed circuit form only)

Make your own mixer, mono or stereo, up to 2 channels, with full monitoring facilities. and provision for echos end/return etc.

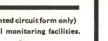

- Inputs for low and high 2 mic, ceramic & magnetic cartridge etc.
- Up to 20 input modules per single mixing module
- Feed most types of amplifier—accepts all inputs
- Professional low noise circuitry 20Hz-30kHz
- Infinitely adaptable—Extremely economical

COMPLETE MODULES With facia panel, Knobs & sockets, Monitor buttons, Ready wired & tested

Mono input	**£8·50**	Mono mixing stage	**£8·50**
Stereo input	**£12·00**	Stereo mixing stage	**£12·00**

- 0·5W headphone circuit
- Full range bass/ treble controls
- Noise—80dB

PRINTED CIRCUIT MODULES With controls fitted, requires only sockets, facia & knobs

Mono Input	**£5·50**	Mono mixing stage	**£5·50**
Stereo Input	**£9·00**	Stereo mixing stage	**£9·00**

Power supply for up to 20 channels—PPM18—**£8·50.**

SYSTEM 7000 SOUND—LITE (3-CHANNEL) IN COMPLETE OR MODULAR FORM (Modular form illustrated)

- Complete unit similar to Mk II unit above
- Long established & proven design
- 3 Channels—100W per channel
- RCA 8A Trixes—individual channel fuses
- 1-240 W Inputs—master audio level plus Bass/Middle/Treble

COMPLETE UNIT—Fully cased with rear terminations—just plug plug in and go! **£24·75**

MODULAR FORM Facia & knobs etc. Needs only 11 simple connections **£16·50** (Panel £2·50)

COMPLETE DISCO SYSTEMS FROM ONLY **£16·06** DEPOSIT

WITH TWO YEAR GUARANTEE—LOW INTEREST CREDIT

CENTAUR 100W STEREO

with TWIN LOUDSPEAKER, SOUND to LIGHT SEQUENCER **PLUS** DISPLAY. **£225** + £10 carr. (Dep. £28·80, 12 months at £21·33 or 24 months at £12·01)

SUPER CENTAUR 200W STEREO

As above but with 200 WATTS OUTPUT and larger TWIN CABINETS.
£275 + £10 carr. (Deposit £32·80, 12 months at £29·39 or 24 months at £15·21).

GXL CENTAUR 200W STEREO

As the SUPER CENTAUR but with extra large twin 200 WATT CABINETS, DECK LIGHTS, DECK STARTS & SUPERIOR DECKS.
£349 + £10 carr. (Deposit £42.72, 12 months at £36·58 or 24 months at £20·54)

- Cue Light + Head Phone monitoring
- Mic & Tape inputs
- Crossfade & Override
- Logic Circuitry Lightshow
- Complete and ready to use
- Extremely Rugged construction
- Twin BSR Decks

Send today for Free illustrated Leaflet on Saxon Complete Discos & Package PA Systems.

All Equipment subject to a Two Year Guarantee.

Deliveries in the UK by our own vans.

50W MINI DISCO £139·50 + £5 carr. (Dep. £16·05, 12 months at £13·30 or 24 months at £7·46)

100W MINI DISCO £159·50 + £5 carr. (Dep. £22·66, 12 months at £14·73 or 24 months at £8·27)

Two extremely compact mono systems complete with loudspeakers and leads.

- TWIN BSR DECKS
- HEADPHONE MONITORING
- MIC INPUT

100W PACKAGE P.A. £145 + £7·50 carr. with twin loudspeakers and PIEZO HORNS Dep. £19·70, 12 months at £13·70 or 24 months at £7·73)

SEND YOUR SPECIAL REQUIREMENTS FOR A CUSTOM DISCO QUOTATION

SYSTEM 7000 MINOTAUR 100—All Purpose Wide Range Amplifier

- 100W rms & 1dB
- Standard 8 ohm output
- Twin mixed inputs accept a wide range of signals
- 20HZ-30KHZ @ 2dB
- 23dB base/treble

A four Input, high power amplifier which will deliver up to 130 watts output. An absolute must where multiple mixing & power are required

- Four individually mixed inputs
- Wide range bass/treble + master

An extremely compact and versatile amplifier with full protection and a clean, attractive appearance. Ideal for all groups, disco's & clubs

£49·50

- Vynide covered case.
- Fully short proof
- Superb value for money

SAXON 150 HEAVY DUTY AMPLIFIER **£59·00**

STROBES & PROJECTORS (We stock the full Pluto range) Send for details

SUPERSTROBE **£19·75**

- 3-3 Joules
- 80W Tube for long life
- Compact 4" × 4" × 4"

PROJECTROBE **£32·50**

- 6-8 Joules
- External trigger
- Long Life tube timer circuit

150 WATT LIQUID WHEEL PROJECTOR

- Accepts all accessories
- C/w with wheel & motor plate
- Sturdy steel construction

Remarkable value—Sold elsewhere at £39·50. Our price is only:

£33·00

ACCESSORIES

Condenser mics ECM77 600 ohms **£13·50**
ECM81 Dual Impedance **£14·95**
Heavy duty boomstand **£14·50**
Crown headphones **£6·75**

All prices subject to VAT @ 8% except SA308/PM301, mics. and headphones (12½%
Add 50p post & packing on all orders except where already shown.
Ordering: By Telephone —Access, Barclay Card or COD Ring (01) 684 6385/0098
By post —Send cheque or crossed P.O's or 60p for COD
or send in your Access/Barclay card NUMBER ONLY

327-333 Whitehorse Road, Croydon, Surrey CR0 2HS
24 Hour Ansafone service (01) 684 6385

PIEZO HORNS!! UP TO 150 WATTS HANDLING. NO X-OVER REQUIRED £7·50 ea.

Exporters to 17 countries—enquiries welcomed
Ring Sue Abegg on (01) 684 6385 for U.K. trade enquiries

CRESCENT RADIO LTD.

164-166 HIGH ROAD, LONDON N22 6EJ 888-3206
(also) 13 SOUTH MALL, EDMONTON, N.9 803-1685
MAIL ORDER DEPT.
1 ST. MICHAELS TERRACE, WOOD GREEN, LONDON N22 4SJ Phone 888 4474

3-WAY MULTIPLE AC ADAPTOR
This compact adaptor allows a large range of battery powered equipment to be operated from A.C. mains (220-240V A.C.). Switchable for 6, 7.5 or 9 volts, current rating is 300 m/A max. A polarity reversing coupler is incorporated and the lead is terminated by a four way plug offering connections by 2·1 and 2·5mm sockets, 3·5 and 3·0mm plugs. The sealed transformer unit is fitted with a 2 pin 13A mains plug and measures 70 x 60 x 45mm approx. Only **£6·90** + 8%.

GOODMANS 8in. LOUDSPEAKER
Goodmans "Audiom 8PA" 15ohm speaker, impedance 8 ohm, power handling 10W nominal. Our price **£6·38** + 12½% VAT.

"C100" 100 WATT AMPLIFIER
All built and tested, mounted on a plain aluminium chassis which measures 19" x 9¼" x 4" and which you can mount into a cabinet of your choice. Four controlled inputs, master volume, treble, middle and bass controls. R/c protected output. 100 watts clean into 8ohm 2/8. Ideal for disco, music groups, P.A. and clubs. A bargain at **£48** + £1·50 carr. + 8% VAT.

P.C. ETCHING KIT
This kit contains all that the constructor will need to etch the circuits of his own design.
Contents—Plastic etching dish. Sample copper clad board. Laminate Cutter. 1 lb Ferric Chloride. Large Plastic Spoon. Etch Resist Pen. Full Etching Instructions.
Complete and Big Kit Value at **£4·25** + 8% VAT.

POWER SUPPLY UNITS + 8%

FP1 switched 3, 4½, 6, 7½, 9 and 12 volts at 500 m/a, with on/off switch and pilot light. Size: 130mm × 85mm × 76mm.
ONLY **£6·50**

M3 CONDENSER MICROPHONE
Cardioid and omni-directional 600 ohm and 50K ohm impedance. 20-18,000 Hz. On/off switch and wind shield. Complete with stand adaptor. Packed in presentation box.
Price **£14·00** + 12½% VAT.

HEAVY DUTY 12 VOLT POWER SUPPLY
13 amp at 12 volt power supply approx. size 9" × 5" × 3". Ideal for using your car entertainment in the home from domestic mains. Suitable for 8 track cartridge or 4 track cassette machines. Price **£7·50** + VAT 8%.

2 WAY AND 3 WAY CROSSOVERS + 12½%
NT200 3-way network for 8 ohm speakers up to 20 watts. Price **£2·50**.

NT200H 2-way, as above, 100 watts. Price **£2·25**.
NT300 3-way network for 8 ohm speakers up to 30 watts. Price **£3·25**.
NT300H 3-way, as above, 100 watts. Price **£4·00**.

TIE-CLIP CONDENSER MICROPHONE
Omni-Directional 600 ohm 40–15,000Hz.
Extra long lead. Ideal for stage work, conferences, etc. Price **£9·50** + 12½% VAT.

LOW NOISE LOW PRICE CASSETTES + 8%
Good quality tape in well made screw type cassettes. Presented in single plastic cases.
C90—60p C90—80p C120—60p
10% Discount on ten or more cassettes of one type

LOUDSPEAKERS + 12½%

2½" 8 ohm	90p
2½" 40 ohm	90p
2½" 80 ohm	90p
3" 8 ohm ceramic	£1·00

MAINS 'KEYTECTOR'
This connecting block connects any electrical equipment to the mains supply in seconds.
Ideal for bench, garage, demonstrations, etc. Max. load 13A fused.
Price: **£2·50** + 8% VAT.

MULTI-METER MM12
50,000 o.p.v.

If you need to construct your own work/hobby set and you're not prepared to settle for a small one and pocket pinch, then read the specifications for the MM12, and send for one! AC volts: 0 to 1·5, to 6/300 in 10 ranges. DC volts: 0 to 0·5, to 6/300 in 12 ranges. DC current: 0 to 25 µA, to 6/10 amps in 16 ranges. Resistance: 0 to 100 ohms, to 6/10 meg ohms in 6 ranges. Decibels: −20 to +62 db in 10 ranges. Size: 6¼ × 4¼ × 2¼inch.
Price **£21** + 8% VAT.

BARGAIN PROJECT BOX
A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied). SIZE (internal) 81mm × 81mm × 28mm.
OUR PRICE **50p.** +8%

MAINS
PIEZO ELECTRIC HORN UNITS
New high quality high power tweeter, no fuss or crossover network required as low frequency voltages simply have no effect on the tweeter.
Specification:—
Frequency response: 3·6kHz to 28kHz ± 5db. (Input 4V rms pink noise—output 105db). Max. continuous rms Input voltage: 25V
Minimum series resistor: 10ohm at 1w
Weight: 63 gm. (2.35oz.)
Panel Cut Out: 76mm dia. (3in).
Size: 81mm × 58mm × 76mm
Rating: Depending on connections up to 100W approx. Price: **£9·00** + 8% VAT.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel Bass, Middle, Treble, Each channel has its own sensitivity control. Just connect the input to the 8 ohm tweeter terminals of an amplifier and connect three 2500 watt to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)

£18·50 plus 1·25 P. & P.+8%

BARGAIN TRANSFORMERS
12-0-12 volt 500m/a
240 volt primary transformer bargain.
approx size 65mm × 40mm × 50mm,
fixing centres 75mm
our price £1·20 + 8%

EFFECTS PROJECTOR "150"
No Disco should be without our new effects projector, we believe that this is the most versatile machine for projecting coloured images to supplement your music or lighting. Operates on AC 50Hz. Lamp—115/187 150 watts. Standard Lens—60 m/m.

A sturdy metal construction and takes a range of lenses and accessories. Comes complete with 6" liquid wheel and ready to use. A bargain at **£30** + £1·25 p. & p. + 8% VAT.

ABS PLASTIC BOXES
Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

1004—76mm × 73mm × 45mm	60p
1006—152mm × 74mm × 57mm	80p
1007—182mm × 154mm × 66mm	£1·00
1022—107mm × 86mm × 46mm (sloping front)	£1·00

Plus 8% VAT

MAINS INTERFERENCE SUPPRESSOR
A mains suppressor designed to reduce unwanted mains interference caused by fridges, boilers etc.
Best results are obtained by plugging the item causing the interference directly into the suppressor which is fitted with a 2 pin 13A mains socket. The suppressor is fitted in a black plastic box with three 2BA terminals and measures 70mm × 57mm × 44mm. The unit comes fitted with 1·5m of 3 core cable and has a max. current rating of 5A. Price: **£9·00** + 8%.

U.K. CARRIAGE 50p UNLESS OTHERWISE STATED
ACCESS AND BARCLAYCARD ACCEPTED
VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

YOU CANNOT SKI DOWN OUR SLOPES

vero

But VERO SLOPING FRONT CASES do make attractive housings for many projects.

They are available in two sizes, made from high quality, two tone plastic, with anodised aluminium front panels. Both cases have integral circuit board fixing points in the base.

65 – 2623E and 75 – 1798K make ideal housings for test equipment, audio gear (faders, mixers, rhythm generators etc.) and control boxes.
See them at your local electronics shop and judge for yourself.

Send for our booklet which describes Veroboard, Plain board, DIP board, Pins, Tools, Plastic boxes etc. S.A.E. 7" x 9" plus 10p to:—

VERO ELECTRONICS LTD. RETAIL DEPT.
INDUSTRIAL ESTATE, CHANDLERS FORD, HANTS. SO5 3ZR.

FANTASTIC SAVINGS GOLDRING

GOLDRING G103 Belt Drive Turntable
Famous name turntable slashed to near half price. Complete with plinth, cover and leads. Accepts any standard cartridge (not included)
FULL 12 MONTH GUARANTEE

OUR PRICE £29.95
R.R.P. £54 (+p/p & Ins £2.25)

SAVE OVER £24

Build your own GOLDRING CK2 Belt Drive Turntable

Beautifully engineered unit from the famous Goldring company, comes complete with instructions and all necessary parts. Ready to incorporate into your design plinth and cover. The pleasure of assembling your own deck. (Plinth, cover and cartridge not included).
Usually sold for £54.95 with plinth and cover.
Call in or send cheque, P.O, M.O, Access, Barclaycard, Diners Club or American Express Number.

ONLY £16.95 (+ p.p & Ins. £1.50)
ALL PRICES INC. VAT

Sonic Sound Radio
248/250 TOTTENHAM COURT ROAD, LONDON W1. TEL: 01-637 1908

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz 30KHz ± 3db. Fully integrated pre-amplifier stage with separate Volume, Bass and Treble cut controls. Suitable for 8-15 ohm speakers. Input for

ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input & output sockets. Overall size 3" high × 6" wide × 7½" deep. AC 200/250V. PRICE £13·75. P. & P. £1·20.

HARVERSONIC MODEL P.A. TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Organ, etc. Features 3 individually con-

trolled inputs (each input has a separate 2 stage preamp.). Input 1 5mv into 47k. Input 2 5mv into 47k, (suitable for use with mic. or guitar etc.) Input 3 100mv into 1 meg. suitable for gram. tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for use 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished panel with knobs made from black vynil covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240 volts. Size approx. 12¾" w. × 5" h. × 7½" d.

Special introductory Price £28·00 + £2·50 carriage & packing.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit techniques with

built in short term thermal overload protection. All components including rectifier smoothing capacitors, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec. (play) socket mounted on the printed circuit panel, size approx. 9½" × 22" × 1" max. depth. Supplied tested and working, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £9·00 plus 50p P & P. Mains transformer with an output of 17v a/c at 500m/a and 6v a/c at 1·5 amp + 40p P & P if required. Full connection details supplied.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS

app. 54 in. wide, Our price £1·50 yd. length. P. & P. 50p per 1 yd. (min.) Any length supplied.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS,

Giving 13 alternatives. Primary: 0–210–240v. Secondary conditions 0–9–12–15–18–24–30–36–48v. 60v. half wave at 1 amp, or 10–0–10, 20–0–20, 30–0–30v. at 2 amps full wave. Size 3¼ high × 3¼in. wide × 3 in. deep. Price £2·90 P. & P. £1·00.

MAINS TRANSFORMER.

For power supplies. Pri: 200/240v. Sec. 6–9 at 150 mA. £1·50. P. & P. 65p. Pri: 200/240v. Sec. 12–0–12 at 1 amp. £1·65. P. & P. 65p. Pri: 200/240v. Sec. 20–0–20 at 1 amp. £2·35. P. & P. 85p. Pri: 200/240V Sec. 23V at 1·5 amp, 6V at 6 amp. 8V at 50mA. £2·00 + 85p P. & P.

ALL-PURPOSE POWER SUPPLY UNIT

200 240v. A.C. input. Four switched fully smoothed D.C. outputs at 250v. 150mA 7½v. and 9v. and 12v. at 1 amp on load.

Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" × 5" × 3". Ready built and tested. Price £6·75 P. & P. 95p.

STEREO-DECODER

SIZE 2" × 3". Ready built, Prealigned and tested. Sens. 20-560 mV for 30-15 c. stereo. Can easily be fitted to almost any FM VHF radio or tuner. Stereo light output can be fitted if required. Full details and connections supplied with price and data supplied. £5·62 plus 20p P. & P. Stereo beacon light if required 40p extra.

QUALITY RECORD PLAYER AMPLIFIER MK. II

A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with printed circuit panel and 3 ohm speaker. Size 7in. wide × 3in. deep × 6in. high. Ready built and tested. PRICE £7·00. P. & P. £1·25. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £8·00. P. & P. £1·30.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER

200/240V Mains operated Solid State F/M A/M Stereo Tuner. Covering M.W. A.M. 540-1605KHz VHF/FM 88-108MHz.

Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by front control. Max o/p 9watts R.M.S into 4ohms 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8¼" w × 4"h × 9¼"d approx.

LIMITED NUMBER ONLY at £28.00 + £1·50 P. & P.

SPECIAL OFFERS

Mullard LP1159 R.F.–I.F. Double Tuned Amplifier Module for nominal 470 KHz. Size approx. 2¼" × 1¼" × 1" 7·6 Volt + earth. Brand new pre-aligned. Full specification and connection details supplied. £2·25. P. & P. 20p.

Pye VHF/FM Tuner Head covering 88-108 MHz, 10·7 MHz I.F. output. 7·8 Volt + earth. Supplied pre-aligned, with full circuit diagram. Connection details supplied. Beautifully made with precision-geared FM gang and 323PF + 323PI A.M. Tuning gang only £3·15 + P. & P. 35p.

PRECISION MADE

Push Button Switch bank. 8 Buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5" × 2½" × 1". Supplied complete with chrome finished switch buttons. 2 for £1·50 + 20p P & P.

HI-FI LOUDSPEAKER SYSTEM MK II

Beautiful teak, medium oil finish enclosure with attractive slatted front. Size 16½" high × 10½" wide × 6½" deep (approx.) Fitted with E.M.I. Ceramic Magnet 13" × 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE AS TERMINAL

4 Ohm. 8 Ohm or 15 Ohm impedance (state which). Handling power 10 watts R.M.S.

OUR PRICE £12 each. Carr. £2·20 ea.

Cabinet Available Separately £7·60. Carr. £1·60 each. Also available in 8 ohms with EMI 13" × 8" bass speaker with parasitic tweeter £11·10. Carr. £2·20 each.

LOUDSPEAKER BARGAINS

Sin. 3 ohm 8–10 watt 6000 lines. Only £2·35. P. & P. 48p. 10 × 6in., 3 or 15 ohm £3·20. P. & P. 75p. 7 × 5in. 3 ohm 4 watt. Frequency response 63–00. P. & P. 35p. Tweeter. Approx. 3½". Available 3 or 8 or 15 ohms. 4–5 watt 5,000 c/s. Only £1·25. P. & P. 20p. Matching HF Tweeter 4 ohm £3·50 per matched pair + 50p P. & P.

HIGH POWER HI-FI 8 OHM DOME TWEETER. 1"

voice coil, magnet size 3" dia. suitable for use in up to 30 watt systems. Only £2·50. P. & P. 20p.

SPECIAL OFFER. 6¼" long throw, roll surround, ceramic magnet 8 ohm 10 watt speaker chassis. Specially suitable for HiFi £3·95 + 75p P. & P.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11⅛" × 14⅛" × 1⅝" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz–20kHz. Can be mounted on ceilings, walls, floors, in any box, and used with or without baffle. Send S.A.E. for full details. Only £8 each. P. & P. £1·00. Pair £15·00. Two £1·00. Now available in either 8" round version or 4½" × 8½" rectangular. Response 60Hz–20kHz. £5·25 + P. & P. one (65p, two 75p).

SPECIAL LINES

OFFERED SUBJECT TO STOCK AVAILABILITY

Limited number of British manufacturer's surplus professional 100 watt RMS slave amplifiers. Special features, 2 separate power modules, 1 for Bass response and 1 for mid-range/tweeter. 5 stage LED display for power o/p indication. A/C mains supply available for 110 or 240v. Can easily be converted to Stereo. AVAILABLE TO PERSONAL CALLERS ONLY. PLEASE PHONE TO CONFIRM AVAILABILITY. Brand new & tested only £33·75.

Prices include VAT at Current Rate

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved reliability. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response ±3db 12–30,000 Hz Sensitivity: better than 80mV into 1M Ω. Full power bandwidth: ±3dB 12–15,000 Hz. Bass boost approx. to ±12dB. Treble cut approx. to −16dB. Signal/noise ratio better than 60 over main amp. Power requirements 35v. at 1·0 amp.

Overall Size 12"w. × 8"d. × 2¼"h.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT . . . . . £13·50 P. & P. 80p
(Magnetic input components 33p extra)

POWER PACK KIT . . . . . £5·50 P. & P. 95p

CABINET . . . . . £5·50 P. & P. 95p

SPECIAL OFFER—only £23·75 if all 3 items ordered at one time plus £1·25 p. & p.

Full after sales service

Also available ready built and tested £31·25. P. & P. £1·50

3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records, etc. Mains operation. Ready built on heavy gauge metal chassis, size 7¾"w. × 4"d. × 4¼"h. Employs ECL83, EL84, EZ80 valves. Heavy duty double wound mains transformer and output trans-

former matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4½ watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £7·50. P. & P. £1·40.

HSL "FOUR" AMPLIFIER KIT.

Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £7·60 P. & P. £1·40.

10/14 WATT HI-FI

A superb finished monaural amplifier with a output of 10 watts from 2 EL84s in push-pull. Super response for HiFi, for music and speech. With negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output trans-

former. Separate bass and treble controls with 14dB cut and boost. Valve line-up 2 ECL86s, ECC83, EF86 and EZ80 rectifier. Simple construction booklet 25p + SAE (Free with parts).

All parts sold separately. ONLY £12·00 P. & P. £1·40.
Also available ready built and tested £16·50 P. & P. £1·40.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Radio, Guitar etc. and suitable for use with valve or transistor equipment. 9-18v. battery or 20-30v. mains supply. Frequency response 15Hz—25KHz. Gain 26dB. Solid encapsulation size 1¼" × 1¼" × ¾". Brand new complete with instructions. Price £1·80 P. & P. 15p.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9.30–5.30 Monday to Friday. 9.30–5 Saturday
Closed Wednesday.

All prices and specifications correct at time of press and subject to alteration without notice.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S. W.19. Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station.

For personal callers only we can now offer a full repair service on all Hi-Fi Equipment, Disco, Cassettes, Car Radio etc. SEND S.A.E. WITH ALL ENQUIRIES

B. BAMBER ELECTRONICS

Dept PW, 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

15V DC RELAYS, 4 pole change-over (double contacts) (will work from 14-24V DC). Brand New, boxed, good quality, made by AEI **40p each.**

Slider Switches, 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins), 4 for **50p.**

Smart Min. Rectangular Push to Make Switches, black rectangular surround with white rectangular button, overall size 12 × 17mm, 5 for **50p.**

A NEW RANGE OF QUALITY BOXES & INSTRUMENT CASES.
Aluminium Boxes with Lids.

AB10	5¼ × 4 × 1½	**60p**
AB13	6 × 4 × 2	**80p**
AB14	7 × 5 × 2½	**£1-00**
AB15	8 × 6 × 3	**£1-60**
AB16	10 × 7 × 3	**£2-00**
AB17	10 × 4½ × 3	**£1-80**
AB20	6 × 4 × 3	**£1-00**

Vinyl Coated Aluminium Instrument Cases with Light Blue tops and White lower sections. Very smart finish.

WB2	5 × 3½ × 2½	**80p**
WB2	6 × 4½ × 1½	**£1-10**
WB3	8 × 5 × 2	**£1-60**
WB4	9 × 5½ × 2½	**£2-00**
WB5	11 × 6½ × 3	**£2-60**
WB6	11 × 7½ × 3½	**£2-80**
WB7	12 × 8½ × 5½	**£2-90**
WB8/83	8 × 4½ × 3	**£1-80**

MAGNETIC DEVICES PROGRAMMERS. Contain 9 fully adjustable cams and 9 change over micro-switches (rated approx. 1A at 240VAC). Needs slow-motion motor to drive (not supplied). Ideal for disco lights, sequence switching, etc. ex equipment **£1-50 each.**

GARRARD 9V DC MINIATURE MOTORS. Type 318M, 3200 RPM governed, size approx. 1¼in. dia. × 1¼in. high, with 3mm spindle. Brand New **65p each or 2 for £1.**

QUARTZ-XTAL CONTROLLED CLOCKS, 9 to 12V DC @ approx. 3mA required. Dial size approx. 2½" high, of unit approx. 4" square overall, sunlit only, smart modern appearance, black face with white lettering, 12hr. with second hand, and red hour and minute hands (Costs over £40 to produce) **£18** each while stocks last, tested before despatch.

RED LEDs (Min. type) 5 for **70p.**

VIDICON SCAN COILS (Translator type, but no data) complete with vidicon base **£8-99 each.** Brand New.

FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK. S.A.E. FOR LIST.

NEW FOR THE VHF CONSTRUCTOR. A range of tuned circuits on formers with slugs and screening cans. Frequencies quoted are approximate, and range can be greatly extended by using varying capacitors in parallel.
Type S (pin. square, dumpy type)
Type SA 30 to 50MHz (when 20pF fitted in parallel).
Type SB 35 to 50MHz (with link winding).
Type SC 50 to 100MHz (with link winding).
Type SD 100 to 150MHz (with link winding)
Type M (miniature pin. square type)
Type MA 19 to 30MHz (when 20pF fitted in parallel).
Type MB 22 to 32MHz (when 20pF fitted in parallel).
Type MC 30 to 50MHz (when 20pF fitted in parallel).
Type MD 36 to 55MHz (when 20pF fitted in parallel).
Type ME 45 to 65MHz (when 20pF fitted in parallel).
Type MF 100 to 200MHz (without slug) when 0 to 30pF variable fitted in parallel.
All the above coils available in packs of five only (same type) at **five packs at £5.**

PLASTIC PROJECT BOXES with screw on lids (in black ABS) with brass inserts.

Type NB2 3¼in. × 2¼in. × 1in.	**50p** each.
Type NB3 approx. 4¼in. × 3¼in. × 1¼in.	**65p** each.

MULLARD BSA2 85V STABILISER VALVES (Brand New) **70p each or 2 for £1-20.**

TO3 translator insulator sets. 10 for 50p

BSX20 (VHF Osc/Mult). 3 for 50p.
BC108 (metal can). 4 for 50p.
PBC108 (plastic BC108). 5 for 50p.
BFY51 Translators. 4 for 50p.
BCY72 Translators. 4 for 50p.
PNP audio type TO5 Transistors. 12 for 50p.
BF152 (UHF amp/mixer). 3 for 50p.
BC107/8/9. 5 for 50p.
BC148 NPN SILICON. 4 for 50p.
BC158 PNP SILICON. 4 for 50p.
BAY31 Signal Diodes. 10 for 50p.
BA121 Varicap Diodes. 4 for 50p.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

SMALL MAINS SUPPRESSORS (small chokes, ideal for radio, Hi-Fi inputs, etc.), approx. ¾in. × ¼in., 3 for **50p.**

PERSPEX TUNER PANELS (for FM Band 2 tuners) marked 88–108MHz and Channels 0–70, clear numbers, mat blacked out, smart modern appearance, size approx. 8¼in × 1¼in., 2 for **50p.**

PLUGS AND SOCKETS
Hi-Type Plugs 50 ohm. **60p** each, 3 for £1-50.
PL259 Plugs (PTFE), brand new, packed with reducers, **25p** or 5 for **£1.**
SO239 Sockets (PTFE), brand new (4-hole fixing type). **50p** each or 5 for **£2-20**

SOLDER SUCKERS (Plunger type). Standard Model, **£5.** Skirted Model **£5-20.** Spare Nozzles **50p** each.

WELLER SOLDERING IRONS
EXPERT. Built-in-spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.
EXPERT SOLDER GUN #1000 £9-95.
EXPERT SOLDER GUN KIT (spare bits, case, etc.) **£12-90.**
Spare bits **50p** pair.

NEW MARKSMAN RANGE OF SOLDERING IRONS.
S115D 15W 240V **£2-50.**
S125D 25W 240V **£2-50.**
S140D 40W 240V **£4-20.**
S125DC 25W 240V + bits etc.. **KIT £4-50.**
SPECIAL 12V version S125-12 25W 12V **£3-50.**
BENCH STAND with spring and sponge for Marksman irons **£2-30.**
Spare bits M4 MT9 (for 15W) **50p,** MT5 (for 25W) **45p,** MT10 (for 40W) **50p.**
ALL PRICES + 8% VAT.
TCP3 TEMPERATURE CONTROLLED IRON. Temperature controlled iron and PSU. **£28 + VAT** (£2-40).
SPARE TIPS
Type CC single flat. Type K double flat fine tip. Type P, very fine tip. £1 each + VAT (8p).
MOST SPARES AVAILABLE.

MULTICORE SOLDER
Size 18 SWG. 18 s.w.g. in alloy dispenser. **50p** + VAT (5p).
Size 22 SWG Sn/Pb 18 s.w.g., **50p** + VAT (4p).
5 Kg. (11 lbs) 60 × 40, 20 s.w.g. on plastic reel **£12** (24p).

14 DIL REED RELAYS, 5 to 12V DC, 450 ohm coil.Designed to work directly from TTL Logic. Single Pole Change over. Contact ratings 28V 1A 3W. **£1-75 each.**

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES. PLEASE ENQUIRE.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. **£2** per pack, while stocks last.

ALL-SOL ALUMINIUM SOLDER (made by Multicore). Solders aluminium to itself or copper, brass, steel, nickel, tinplate, 16 s.w.g. with multicore flux, with instructions. Approx. 1 metre coil **60p** pack. Large reel **£2-75.**

VARICAP TUNERS Mullard type ELC1043/05. Brand New, **£4-48 + 12½% VAT.**

BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS. Up to 50V working. Bestmard Manufacture. Approx. 100, **£1-98 per pack + 12½% VAT.**

OSMOR RESET RELAY COILS (for reed relays up to pin dia., not supplied) 12V, 800 ohm coil, 2 for **50p.**

We now stock Spiralux Tools for the electronic enthusiast. Screwdrivers, Nut spinners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

TWIN L.P. CANNELS, approx. 1in. × ¼in. × 1in. high, around 3–5–5MHz. 4 channels transformers in 1 can, internally screened, 5 for **50p + 12½% VAT.**

Dubilier Electrolytics, 50uF, 450V, 2 for **50p.**
Dubilier Electrolytics, 100uF, 275V, 2 for **50p.**
Hunday Electrolytics, 4700uF, 50V, 8 for **50p.**
TCC Electrolytics, 1000uF, 30V, 3 for **60p.**
Dubilier Electrolytics, 5000uF, 50V, **80p** each.
Dubilier Electrolytics, 5000uF, 50V, 65p each.
TCC Electrolytics, 8800uF, 50V, high grade, screw terminals, with mounting clips, **85p** each.
PLEASE ADD 12½% VAT TO ALL CAPACITORS.

TV PLUGS AND SOCKETS
TV Plugs (metal type). 5 for **50p.**
TV Sockets (metal type). 4 for **50p.**
TV Line Couplers (back-to-back sockets). 4 for **50p.**
Please add 12½% VAT.

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES. *Please* PLEASE ADD VAT AS SHOWN. *ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS WELCOME BY APPOINTMENT ONLY.*

THIS is the Catalogue you need to solve your component buying problems!

HOME RADIO COMPONENTS

- The finest components catalogue yet published.
- Over 200 A-4-size pages.
- About 5,000 items clearly listed and indexed.
- Nearly 2,000 illustrations.
- Bargain List sent free.
- At £1·40, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.

HOME RADIO (Components) LTD., Dept. PW, 234-240 London Road, Mitcham, Surrey CR4 3HD

POST THIS COUPON with cheque or P.O. for £1·40

Please write your Name and Address in block capitals

NAME .....

ADDRESS .....

.....

.....

HOME RADIO (Components) LTD., Dept. PW., 234-240 London Road, Mitcham, Surrey CR4 3HD (Regn. No London 912666)

NEWMART ELECTRONICS

for all your hi-fi needs.

Stockists of: Amstrad • Teleton • Akai • Sansui • Wharfedale • Pioneer • Rotel • Garrard • Connoisseur

BATTERY ELIMINATORS P&P 25p
240v input 6, 7·5 or 9v output at 00mA .. .. £3·25

CARTRIDGES & STYLI D—D & RPL Styli
P&P 25p

Cart.	Styli
Acos GP91/3CS (ster. comp)	£1·50	£1·50
GP93/1 or 99/1 ster. crystal	£2·00	£1·50
GP94/1 or 96/1 ster. ceram.	£2·00	£1·50
GP101 crystal. comp.	£1·00	—
GP106 ster. ceram	£2·00	£1·50
BSR X5M or X5H cryst. comp.	£1·75	£1·00
SX6M or SX6H cryst. star.	£2·25	£1·50
SC6M ster. ceram.	£2·75	£1·50
Sonotone 9TAHC or 9TAHC/G (Diam.)	£2·00	£1·50
3000	£2·50	£1·50
Audio Technica AT35	£2·25	—
Goldring G800	£3·75	£1·75
G800	£3·50	£1·75
G800E	£3·00	£1·50

Shure Cartridges & Styli

M44G/M44C	£7·70	£8·20
M55E	£8·20	£7·15
M75ED Type 2	£11·15	£12·00
M75EJ Type 2	£14·30	£8·70

M.O. prices only. VAT inc. Subject to Availability & manufs. increase. **Send 39p for Catalogue, Barclay/Access.**

Callers Welcome at Manchester 30-32 Shudehill Tel. 061-832 7710. Leeds 4 New Market St. Tel. 0532 42705. Liverpool 15 Whitechapel, Tel. 051-236 0738

SPEAKERS P&P 85p
EMI 13" x 8", 8 ohm Plain 8" x 5" 2-Way, 5 watt, 3.8 or 15 ohm .. .. £3·40
8" x 5" Dualcone 8 ohm, 10 watt .. .. £3·70
8" x 5" Dualcone .. .. £3·40
10" Dualcone .. .. £4·10
Richard Allan 80w 12" 8 or 15 ohm .. .. .. £19·00

MICROPHONES P&P 45p
UD 130 50K/600 ohm uni-dir. dual metal .. £8·35
Cassette Stick Mic. with R/Control .. .. £1·65
Cass. Stick Mic. with R. Control (Philips type) .. £1·93

CASSETTES P&P 1–3 25p, 4 and over 50p

	C60	C90	C120
Low Noise	£0·37	£0·49	£0·70
Philips	£0·79	£1·08	£1·73
Memorex	£0·81	£1·08	£1·89
Cassette Head Cleaner	..	..	£0·55
Bib Head Cleaner Dc-magnetiser	..	..	£1·98

RECORD DECKS P&P £1·65
GARRARD SP25 Mk IV £84·99
GARRARD SP95 Mk IV/G800 with Plinth & Cover £39·50
BSR MP60 (P128R) £37·50
Plinth & Cover for Garrard, BSR & .. .. .. £4·95
BD1 Kit .. .. .. £17·25

Mail Order Dept PW/9
Belmont St, Edmonton, Eccles, Manchester.
Tel 061-789 5268

15–240 Watts!

HY5
Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag, ceramic cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise —Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:
INPUTS. Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; Input impedance 4·7kΩ at 1kHz.
OUTPUTS. Tape 100mV; Main output 500mV R.M.S.
ACTIVE TONE CONTROLS. Treble ± 12dB at 10kHz; Bass ± at 100Hz.
DISTORTION. 0·1% at 1kHz. Signal/Noise Ratio 66dB.
OVERLOAD. 35dB on Magnetic Pick-up. SUPPLY VOLTAGE ± 16-50V.

Price £5·22 + 65p VAT P&P free.

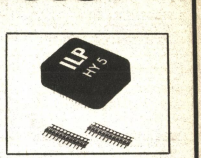

HY30
15 Watts into 8Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

SPECIFICATIONS:
OUTPUT POWER 15W R.M.S. into 8Ω; DISTORTION 0·1% at 1·5W.
INPUT SENSITIVITY 500mV. FREQUENCY RESPONSE 10Hz-18kHz—3dB.
SUPPLY VOLTAGE ± 18V.

Price £2·22 + 65p VAT P&P free.

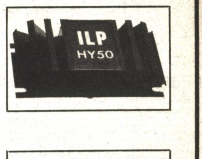

HY50
25 Watts into 8Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier

SPECIFICATIONS: INPUT SENSITIVITY 500mV
OUTPUT POWER 25W RMS into 8Ω LOAD IMPEDANCE 4-16Ω DISTORTION 0·04% at 25W at 1kHz.
SIGNAL/NOISE RATIO 75dB FREQUENCY RESPONSE 10Hz-45kHz—3dB.
SUPPLY VOLTAGE ± 25V SIZE 100 50 25mm

Price £4·32 + 85p VAT P&P free

HY120
60 Watts into 8Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

SPECIFICATIONS
INPUT SENSITIVITY 500mV.
OUTPUT POWER 60W RMS into 8Ω LOAD IMPEDANCE 4-16Ω DISTORTION 0·04% at 60W at 1kHz
SIGNAL/NOISE RATIO 90dB FREQUENCY RESPONSE 10Hz-45kHz—3dB SUPPLY VOLTAGE ±45V
SIZE 114 50 85mm

Price £15·84 + £1·27 VAT P&P free.

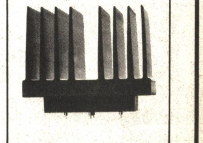

HY200
120 Watts into 8Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink —No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS
INPUT SENSITIVITY 500mV
OUTPUT POWER 120W RMS into 8Ω LOAD IMPEDANCE 4-16Ω DISTORTION 0·05% at 100W at 1kHz
SIGNAL/NOISE RATIO 96dB FREQUENCY RESPONSE 10Hz-45kHz—3dB SUPPLY VOLTAGE ±45V
SIZE 114 50 85mm

Price £22·32 + £1·67 VAT P&P free.

HY400
240 Watts into 4Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4Ω ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power modular module.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components.

APPLICATIONS: Public address—Disco—Power slave—Industrial

SPECIFICATIONS
OUTPUT POWER 240W RMS into 4Ω LOAD IMPEDANCE 4-16Ω DISTORTION 0·1% at 240W at 1kHz.
SIGNAL NOISE RATIO 94dB FREQUENCY RESPONSE 10Hz-45kHz—3dB SUPPLY VOLTAGE ±45V
INPUT SENSITIVITY 500mV SIZE 114 100 85mm

Price £32·17 + £2·57 VAT P&P free.

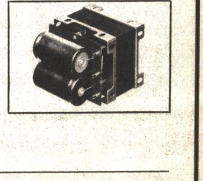

POWER SUPPLIES

PSU35 suitable for two HY30's £2·22 plus 65p VAT. P/P free.
PSU50 suitable for two HY50's £2·65 plus 85p VAT. P/P free.
PSU70 suitable for two HY120's £3·75 plus £1·10 VAT. P/P free.
PSU90 suitable for one HY200 £12·65 plus £1·01 VAT. P/P free.
PSU180 £23·19 + £1·85 VAT.
B1 £2·48 + £0·20 VAT.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

Please Supply _____
Total Purchase Price _____
I Enclose Cheque ☐ Postal Orders ☐ Money Order ☐
Please debit my Access account ☐ Barclaycard account ☐
Account number _____
Name and Address _____
Signature _____

I.L.P. ELECTRONICS LTD., CROSSLAND HOUSE, NACKINGTON, CANTERBURY, KENT, CT4 7AD.

I.C.E. MULTIMETERS

TWICE the information in HALF the size

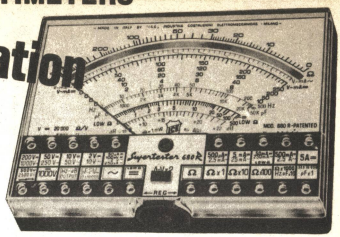

The I.C.E. range of multimeters provide an unrivalled combination of maximum performance within minimum dimensions, at a truly low cost. Plus, a complete range of add-on accessories for more ranges, more functions.

Supertester 680R (illustrated)
* 20kΩ/V, ±1% fsd on d.c.
  4kΩ/V, ±2% fsd on a.c.
* 80 Ranges – 10 Functions
* 140 × 105 × 55mm

£25.25 + VAT
(For Mail Order add 80p P&P)

Supertester 680G
* 20kΩ/V, ±2% fsd on d.c.
  4kΩ/V, ±2% fsd on a.c.
* 48 Ranges – 10 Functions
* 109 × 113 × 37mm

£19.95 + VAT
(For Mail Order add 80p P&P)

Microtest 80
* 20kΩ/V, ± 2% fsd on d.c.
  4kΩ/V, ±2% fsd on a.c.
* 40 Ranges – 8 Functions
* Complete with case – only 93 × 95 × 23mm

£14.95 + VAT
(For Mail Order add 80p P&P)

All I.C.E. multimeters are supplied complete with unbreakable plastic carrying case, test leads, etc. and a 50-plus page, fully detailed and illustrated Operating and Maintenance Manual.
Now available from selected stockists. Write or phone for list, or for details of direct mail-order service.

Electronic Brokers Ltd.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781

V.D.U. AND MICRO COMPUTER

The Crofton V.D.U. is an expandable system built up on a modular basis. The system comprises Rack and P.S.U., Video Sync Generator, Video Control Board, Keyboard, Microprocessor, Memory Extension Board, Cursor Control, Write Control Board, Tape/Phone Interface Board, Microprocessor (SC/MP) Board. The whole system will be gradually extended to make this one of the most versatile on the market. Available in modular form or ready constructed.

Send s.a.e for information

CROFTON ELECTRONICS LTD.
Dept. E, 35 Grosvenor Road, Twickenham Middx. Tel. 01-891 1823
Secondhand cameras and monitors always available

INTRODUCING THE CROFTON EXPANDABLE V.D.U. SYSTEM

PRACTICAL WIRELESS T.V. SOUND TUNER
(Nov. 75 article by A. C. Alnalie) *Copy of original article supplied on request*

IF Sub-Assembly (G8) **£6·80.** P & P 75p
Mullard ELC1043 V'cap UHF Tuner **£4·50.** P & P35p.
3-way Station Control Unit **£1·20.** P & P 25p.
6-way Station Control Unit (Special Offer) **£1·00.**
Power Supply Prtd Circuit Board **£1·00.** P & P 30p.
Res, Caps, Semiconds, etc. for above **£5·80**
Mains Transformer for above **£2·50.** P & P 30p

Add 12½% VAT to price of goods. P & P all items 85p.

Callers welcome at shop premises.

MANOR SUPPLIES
172 WEST END LANE, LONDON NW6
(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

THE OPEN DOOR TO QUALITY

Latest revised issue (4th Edition, Cat. 8). Includes new ranges of meters and switches as well as price adjustments together with items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The Company's own computer expedites delivery and maintains customer satisfaction. Attractive discounts are allowed on many purchases. ACCESS AND BARCLAYCARD ORDERS ACCEPTED.

144 pages
40p
POST PAID inc. 40p Refund Voucher

+ FREE POSTAGE *on all C.W.O. mail orders in U.K. over £2·00 list value (excluding V.A.T.) If under, add 15p handling charge.*

All communications to Dept. PW 5
28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Tel Egham 3603. Telex 264475 Shop 9-5.30, 9-1 pm Sats
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA. Tel: (061) 432 4945. Shop 9-5.30pm, 1 pm Sats.

ELECTROVALUE LTD

Goldring CK2

BELT DRIVE TURNTABLE CONSTRUCTION KIT

Complete with SAU2 arm, template and easy-to-follow instructions. Ready for operation in a short time.

A FEW OF THE MANY BIG FEATURES

- Wow/Flutter 0.15% peak
- Rumble –60dB weighted
- Removeable headshell
- Viscouse damped cueing device
- Easily adjusted tracking force and bias setting
- Two speed, 16 pole synchronous motor
- Dimensions 37.8 x 28.3cms

BRAND NEW IN SEALED CARTONS
12 MONTHS GUARANTEE
OUTSTANDING VALUE
R.R.P. £31.50
OUR PRICE £16·95
(+ £1.50 p/p & ins)

Plinth, cover and cartridge available, P.O.A.
Call in or send a cheque, P.O, M.O, or Access, Barclaycard American Express or Diners Club number.

Lion House
227 Tottenham Court Road, London W.1. Tel 01-580 7383

SCOPES general purpose 3" bench scope single beam Y amp 10c/s to 300Kc sensitivity 10 MIII/V to 100v per Cm, timebase 10c/s to 5Kc in 3 ranges, int or ext sync, provision for beam mod, controls focus, brill, X & Y shift, Y amp atten, T.B. coarse & fine, sync. sel, sync. amp & polarity, etc. Tube green trace 1·5Kv fitted Cm graticule approx. size 12 x 9½ front 23" deep, supplied tested with handbook for use on 200/250v mains **£35.**

I.F.F. TRANSPONDERS for use on the 1 KM/c band contains Tx & Rx tuning cavities, 60 Mc/s I.F. strip, blower, pulse trans & other H.V. parts, normal I/P 115v 400c/s Tx gives approx. 1 Kw peak 1 Usec pulses. Note these are less valves & ext. soiled, with circ. **£10·80. TRANS H.T.** prls. 230v sec. 1125-0-1125v at 585 Ma new **£10·80** also 525-0-525v at 800Ma. **£7·50 STANDARD CELLS** for cal dvm. 1·018 volts **£4·50. SWTS.** miniature toggle S.P.C.O. 3 for **£1·20. INFRA RED T.S.** used for testing image convertor tubes as mains p.u. giving 24v dc stab, 100Ua meter to read o/p of p.c. infra red light source, eht unit giving 12Kv d.c. from I/P of 24v d.c. complete in neat carrying case with cables, etc., recent manufacture **£15. BLOWERS** single ended outlet 2 x 1¾" approx. 50 cfm for 240v new **£8·40. U.H.F.** ground stations 225 to 400Mc/s single channel 100 watt A.M. 230v I/P consists of Tx, Md & Rx with circs etc. **£173.**

THE FOLLOWING FOR CALLERS ONLY.
X BRAND AIRCRAFT SCANNERS AND DRIVES £15.

Above prices Inc. carr./postage & Vat. carriage charges apply to U.K. mainland only, goods ex equipment unless stated new. SAE for list 17|2 or enquiry. Shop open Tues. to Sat.

A. H. SUPPLIES 122 HANDSWORTH RD., SHEFFIELD S9 4AE Ph. 444278 (0742)

ESSENTIAL BOOKS for RADIO AMATEURS

VOLUME 2
completes the
RADIO COMMUNICATION HANDBOOK
(5th edition)

Volume 2 of this standard reference work has now been published. Its contents reflect the ever-expanding scope of amateur radio, with subjects such as fm repeaters and slow-scan television included for the first time in this edition; while a whole chapter is now given over to amateur satellites.

The major part of Volume 2, however, is devoted to the more fundamental aspects of radio communication. The 98-page chapter on hf antennas is a "book within a book", and such vital subjects as propagation, noise and interference are covered in detail in individual chapters.

Chapter titles are: Propagation; HF aerials; VHF and uhf aerials; Mobile and portable equipment; Noise; Power supplies; Interference; Measurements; Operating technique and station layout; Amateur satellite communication; Image communication; The RSGB and the radio amateur; and General data.

324 + xii pages **Price £8·12 post paid**

VHF-UHF MANUAL
(3rd edition)
by D. S. Evans, PhD, AIM, G3RPE, and G. R. Jessop, CEng, MIERE, G6JP

Over 400 large-format (180 x 245mm) pages packed with ideas, information and constructional details of tried and tested equipment, each specialist topic contributed by an acknowledged expert in the field.

The most comprehensive and up-to-date review of vhf and uhf techniques available today.

Chapters on receivers, transmitters, space communications, filters, aerials, microwaves and much more. Simple amateur television is covered and a data section provides valuable facts and figures to help the constructor. Many of the designs make use of integrated circuits, and the microwaves chapter gives details of equipment for use up to 24GHz.

404 + xii pages **Price £6·82 post paid**

RSGB AMATEUR RADIO CALL BOOK 1977

Incorporates all new callsigns and amendments notified between August 1975 and August 1976.

Also includes valuable operating data such as band plans, beacons, prefix list, ITU zone list, beam headings and QSL Bureau sub-managers, and lists of clubs and groups.

176 pages **Price £2·35 post paid**

These are just a few of a complete range of technical publications, log books and maps for the radio amateur. Send a large stamped self-addressed envelope for the complete list.
The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the membership section and ask for full details.

Radio Society of Great Britain
35 DOUGHTY STREET, LONDON, WC1N 2AE

MINI CONSOLES

Ideal for small desk control panels and consoles. Moulded in orange, blue, black and grey ABS. Incorporates slots for holding 1.5mm thick pcb's. Aluminium panel sits recessed into front of console and held by screws running into integral brass bushes.

MC 161 x 96 x 58mm	£1.53 (1-9)	£1.50 (10+)
MC 215 x 130 x 76mm	£2.20 (1-9)	£2.17 (10+)

Add 25p per £1 order value for Post & Packing

ECONOMY QUALITY LED's

50 for only £5 – 100 for only £9
Mixed bags, all sizes, various colours

FULL SPECIFICATION LED's

Red (specify size) 75p per pack
Green, Yellow, Orange (specify size) £1.20 per pack
(Each pack contains 5 LED's, Mounting Clips and Data)

TYPE A NEON INDICATORS

Supplied with resistor for 240 Volts operation
Held in 8mm hole by plastic bezel
150mm wire leads

Red, Amber, Clear, Opal	19p each
Green	28p each

12 VOLTS MINI HAND DRILL

Ideal for drilling pcb, chassis etc as well as model making. Supplied with 2 collets that accept tools and drills with 3/32" and .050" dia. shanks. £7.56 (Includes VAT & P.P.)

Stop wasting time soldering
The NEW MW BREADBOARD accepts
Transistors, LED's,Diodes, Resistors, Capacitors and all DIL packages with 6 to 40 pins

Includes slot-in Component Support Bracket and has over 400 individual sockets, plus Vcc and Ground Bus Strips
Price £9.72 (includes VAT & P.P.)

TYPE MP NEON INDICATOR

Supplied with resistor for 240 Volts operation
150mm leads, held in 6.4mm hole by nut

 

Red, Amber, Clear, Opal 20p each

SEVEN SEGMENT DISPLAYS

Economy Quality
Common Anode – 0.3" — Left Decimal
Red, Yellow and Green @ 45p each

Full Specification
Common Anode – 0.3" - Left Decimal
Red @ 98p each
Green and Yellow @ £1.35 each
(Data supplied with Full Spec. displays only)

Quantity quotations on request

P.P. Note Unless included in price add 25p Post & Packing for orders totalling under £10. All prices include VAT and are valid in UK only for 2 months from journal issue date

Michael Williams Electronics
47 Vicarage Av. Cheadle Hulme, Cheshire SK8 7JP

SC BOXES (square corners)

Easily drilled or punched, orange, blue, black and grey ABS. Incorporate slots for holding 1.5mm thick pcb's. Aluminium panel sits recessed into front of the box and held by screws running into integral brass bushes.

SC 85 x 56 x 35mm	80p (1-9)	77p (10+)
SC 111 x 71 x 48mm	£1.07 (1-9)	£1.04 (10+)
SC 161 x 96 x 59mm	£1.49 (1-9)	£1.46 (10+)

Add 25p per £1 order value for Post & Packing

240 VOLTS MINI HAND DRILLS

Ideal for drilling pcb's, chassis etc as well as model making. Supplied with 3 collets that accept tools and drills with 1mm, 2mm and 1/8" dia shanks.
£9.72 (Includes VAT & P.P.)
Accessory tools... 8 Burrs, 1mm, 2mm, 1/8th Drills, 3/32" Collet Price £1.75 (Includes VAT & P.P.)

RC BOXES (round corners)

Easily drilled or punched, orange, blue, black and grey ABS. Incorporate slots for holding 1.5mm thick pcb's. Close fitting flanged lids held by screws running into integral brass bushes.

RC 100 x 50 x 25mm	51p (1-9)	49p (10+)
RC 112 x 62 x 31mm	59p (1-9)	52p (10+)
RC 120 x 65 x 40mm	68p (1-9)	62p (10+)
RC 150 x 80 x 50mm	77p (1-9)	74p (10+)
RC 190 x 110 x 60mm	£1.33 (1-9)	£1.30 (10+)

Polystyrene version
in grey only with no slots, no integral brass bushes
RC(P) 112 x 61 x 31mm 36p (1-9) 32p (10+)
Add 25p per £1 order value for Post & Packing

Speed up your precision work with

MINIATURE POWER EQUIPMENT

SUPER 30 KIT – 30 tools incl. drill without stand £19·39 pp £1
PIS DRILL STAND £5·13 pp 38p
PI DRILL £9·67 pp 38p
FLEXIBLE DRIVE SHAFT £5·94 pp 34p
TRANSFORMER continuous ac/12v dc £7·56 pp 81p
VARIABLE SPEED TRANSFORMER £9·50 pp 81p

Replacement drills, stones, burrs, etc. 40p each. Circular saw blades set of 4 with arbor £2·50. P. & P. any quantity 25p. 9" × 4" S.A.E. please for leaflet and order form

Drill can be held in the hand.

PP LTD
PRECISION PETITE LTD
119a HIGH STREET TEDDINGTON MIDDLESEX TW11 8HG
Tel. 01-977 0878 24 Hour recorded service

MAINS INTERCOM

NO BATTERIES NO WIRES ONLY
£29·99
PER PAIR + VAT £3·75

The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range 1-mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom. between office and warehouse in surgery and to homes. P. & P. 97p.

4-STATION INTERCOM

£18·95
+ V.A.T. £1·32
Solve your communication problems with this 4-station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Visual call signal. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 97p.

NEW! AMERICAN TYPE CRADLE
TELEPHONE AMPLIFIER

ONLY
£14·95
+VAT £1·20

Latest transistorised Telephone Amplifier with detached ping-pa speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume. Direct tape recording model at £16·95 + VAT £2·50. P. & P. 87p.
10-day price refund guarantee on all items.
WEST LONDON DIRECT SUPPLIES (FW9)
169 KENSINGTON HIGH STREET, LONDON, W8
01-937 5048

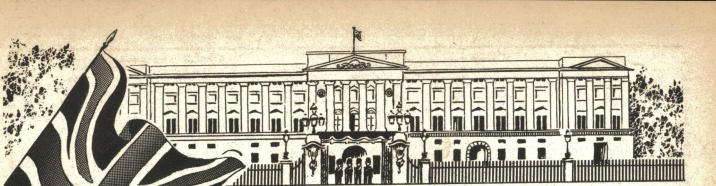

JUBILEE SALE

74 SERIES TTL IC's

Type	Quantity 1	Quantity 100	Type	Quantity 1	Quantity 100
	£ p	£ p		£ p	£ p
7400	0·09	0·08	74LB	0·70	0·68
7401	0·11	0·10	74S00	0·12	0·10
7402	0·11	0·10	74S01	0·12	0·10
7403	0·11	0·10	74S03	0·12	0·10
7404	0·11	0·10	74S04	0·12	0·10
7405	0·11	0·10	74S05	0·12	0·10
7406	0·28	0·25	74S10	0·24	0·23
7407	0·28	0·25	74S11	0·24	0·23
7408	0·13	0·11	74S13	0·24	0·22
7409	0·12	0·11	74S14	0·24	0·23
7410	0·09	0·08	74S15	0·24	0·23
7411	0·23	0·20	74S16	0·24	0·23
7412	0·23	0·20	74S20	0·24	0·23
7413	0·26	0·25	74S21	0·24	0·23
7416	0·28	0·25	74S22	0·24	0·23
7417	0·26	0·25	74S30	0·24	0·23
7420	0·11	0·10	74S40	0·85	0·80
7423	0·19	0·18	74S50	0·12	0·10
7423	0·21	0·20	74S86	0·28	0·26
7425	0·28	0·23	74S89	2·70	2·50
7426	0·25	0·23	74S90	0·38	0·32
7427	0·25	0·23	74S91	0·65	0·62
7428	0·36	0·34	74S92	0·43	0·35
7430	0·12	0·10	74S93	0·38	0·35
7432	0·20	0·19	74S94	0·70	0·68
7433	0·38	0·36	74S95	0·60	0·58
7437	0·26	0·25	74S96	0·70	0·68
7438	0·26	0·25	74S100	0·95	0·90
7440	0·12	0·10	74S104	0·90	0·85
7441	0·60	0·57	74S105	0·90	0·85
7442	0·80	0·70	74S107	0·30	0·25
7443	0·95	0·90	74S110	0·48	0·45
7444	0·95	0·90	74S111	0·75	0·72
7445	0·80	0·75	74S112	0·48	0·45
7446	0·80	0·75	74S119	1·30	1·20
7447	0·70	0·68	74S121	0·28	0·26

Devices may be mixed to qualify for quantity price. Data is available for the above series of IC's in booklet form **Price 35p**

CMOS ICs

CD4000	£0·18		CD4022	£0·80	
CD4001	£0·18		CD4023	£0·18	
CD4002	£0·18		CD4024	£0·64	
CD4006	£0·80		CD4025	£0·18	
CD4007	£0·18		CD4026	£1·85	
CD4008	£0·80		CD4027	£0·60	
CD4009	£0·50		CD4028	£0·80	
CD4010	£0·50		CD4029	£0·90	
CD4011	£0·18		CD4030	£0·46	
CD4012	£0·18		CD4031	£1·90	
CD4013	£0·42		CD4035	£1·10	
CD4014	£0·90		CD4040	£0·90	
CD4015	£0·42		CD4041	£0·68	
CD4016	£0·45		CD4042	£0·68	
CD4018	£0·85		CD4043	£0·78	
CD4019	£0·45		CD4044	£0·78	
CD4020	£0·95		CD4045	£1·15	
CD4021	£0·95				

CD4046	£0·95
CD4047	£0·90
CD4048	£0·46
CD4049	£0·95
CD4050	£0·95
CD4051	£0·90
CD4052	£0·90
CD4053	£0·22
CD4054	£1·20
CD4055	£1·20
CD4056	£1·20
CD4057	£1·20
CD4059	£3·20
CD4060	£1·20
CD4061	£2·20
CD4070	£0·20
CD4071	£0·20
CD4072	£0·20
CD4073	£0·20
CD4075	£0·20
CD4077	£0·20
CD4078	£0·20
CD4081	£0·20
CD4082	£0·20
CD4510	£1·10
CD4511	£1·32
CD4518	£1·10
CD4520	£1·10

ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED NOT FORGETTING TO INCLUDE OUR "J" NUMBERS

V.A.T.

ADD 12½% TO PRICES MARKED * ADD 8% TO ALL OTHERS

POSTAGE AND PACKING

ADD 25p FOR POSTAGE AND PACKING UNLESS OTHERWISE SHOWN. ADD EXTRA FOR AIRMAIL MINIMUM ORDER £1·00

TESTED TRANSISTOR PAKS

All devices brand new, tested and coded

J1	3 x AC128/AC176 each	J16	2 x BFY30/81/83 each
J2	10 x BC107	J17	6 x OC71
J3	10 x BC108	J18	4 x ZTX108/9 2 x ZTX107* each
J4	10 x BC109	J19	2 x ZTX301/2 4 x ZTX300* each
J5	3 each BC148/149-2 BC147* each	J20	2 x ZTX3001/2* each
J6	BC169/171/172—3 each*	J21	4 x 2N706/2N708 each
J7	3 each BC177/8/9 each	J22	1 x 2N2218/19/21/22 each
J8	2 each BC182/3* each	J23	2 x 2N904/05 each
J9	2 each BC212/3* each	J24	2 x 2N2907 2 x 2N2906 each
J10	2 x BC327 3 x BC328*	J25	7 x 2N2926 G*
J11	2 x BC337 2 x BC338*	J26	4 x 2N3053
J12	2 x BF115—BF167—BF173 each	J27	2 x 2N3055
J13	4 x BF184/6* each	J28	2 x 2N3702/03/04* each
J14	2 x BF258	J29	3 x 2N3904/06* each
J15	5 x BFX29 3 x BFX84		

PRICE 60p PER PACK

TESTED DIODE PAKS

J30	12 x OA81	J35	20 x IN4001
J31	12 x OA91	J36	15 x IN4002
J32	12 x OA200	J37	10 x IN4004
J33	12 x OA202	J38	5 x IN4007
J34	15 x IN4148		

J39	5 x IN5400
J40	5 x IN5401
J41	4 x IN5404
J42	3 x IN5408

PRICE 60p PER PACK

OPTOELECTRONICS

J43	4 x DL707 + Data	£3·90
J44	5 x .125 Red LED	£0·50
J45	3 x .2 Red LED	£0·50
J46	5 x .2 and .125 LED's mixed colours	£0·50
J47	3 x ORP12 equivalents	£1·20
J48	5 x OCP71	£1·00

THYRISTOR PACKS

J49	2 x 1 amp 1 x 400 / x 600	£1·50
J50	Same as J49 + 2 x 30 2 x 400 / x 600	£1·80

UNIJUNCTION F.E.T. PAKS

J51	6 x TIS43/UT46	£1·00
J52	4 x 2N3819	£0·60

P.C.B. PRODUCTS

J53	2x Etch resistanc pens	£1·00
J54	2 x Etchant paks	£0·60

D.I.Y. PRINTED CIRCUIT KIT

CONTAINS 6 Pieces copper laminate, box of etchant powder and measure, tweezers, marker pen, high quality pump drill, Stanley knife & blades, 6 inch metal rule. FULL Easy to follow instructions.

J59 ONLY £5·50

RESISTOR PAK

J55	240 first quality ¼W resistors—mixed from 100ohm—820k	£1·60*
J56	160 first quality ½W resistors—mixed from 100ohm—820k	£1·60*

ELECTROLYTIC PAK

J57 54 first quality miniature electrolytics from .47µF—1000µF £1·20*

CERAMIC PAK

J58 93 first quality ceramic capacitors—mixed from 22pF—.047µF £1·60*

I.C. SOCKET PAKS

J60	11x 8 pin D.I.L. Sockets	£1·00
J61	10 x 14 pin D.I.L. Sockets	£1·00
J63	9 x 16 pin D.I.L. Sockets	£1·00

ZENER PAKS

J63	20 mixed value 400mW zener diodes 3-10V	£1·00
J64	20 mixed value 400mW zener diodes 11-33V	£1·00

BI-PAK

Dept. P.W.9, P.O. Box 6, Ware, Herts

ASSISTANT EDITOR
Eric Dowdeswell G4AR

ART EDITOR
Peter Metalli

TECHNICAL EDITOR
Ted Parratt, BA

NEWS & PRODUCTION EDITOR
Bill Tull

TECHNICAL ARTIST
Alan Martin

TECHNICAL SUB-EDITOR
Frank Ogden

SECRETARIAL
01-634 4292 Linda Walji
Belinda Mould

ADVERTISING MANAGER
01-634 4612 Roy Smith

CLASSIFIED ADVERTISING
01-261 5762 Colin R. Brown

BINDERS

Binders, for either the old or the new format, are £2·10 and Indexes are 45p (Inc VAT) and can be obtained from the Post Sales Department, IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF. Remittances with overseas orders for binders should include 60p to cover despatch and postage.

BACK NUMBERS

We are very glad to announce the re-establishment of a PW Back Numbers Service for our readers. In future back numbers dated from June 1977 only will be available from our Post Sales Department for 65p, which includes postage and packing. Cheques and Postal Orders should be made payable to IPC Magazines Ltd.

Send your orders to:- Post Sales Department, IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

Our Face-lift

Well, here it is! The new and, we hope, more attractive, larger version of **Practical Wireless**, as promised last month. PW has gone through other changes of size in the 45 years that it has been around and when it was first published in 1932 the page size was just the same as our 'new' format! So we seem to have gone through the whole cycle! In the 60's PW was quite small, about 9 × 6in., with correspondingly more pages but it was quite popular since one could roll or fold it up to fit the coat pocket, and I would imagine that there are many readers who would still prefer it that way!

Those that know all about these things have now been able to produce a bigger page area from the same size reel of paper, although the printing costs are marginally higher. We trust that you will like the slightly larger type face, being easier to read. Anyway, if you do favour the new-look **Practical Wireless** do not hesitate to let us know. No doubt the disapprovers will also be in touch but their letters will be equally welcome.

As the compiler of the amateur bands section of our monthly feature "On the Air" I know something of the problems that can be encountered by the very keen listener to the amateur bands who wants to get on and obtain the amateur transmitting licence. Although many schools, colleges and radio clubs run classes for the Radio Amateur's Examination there are many potential candidates who just cannot reach such places and who must rely on their own studies at home.

This month sees the start of a new series aimed not only at the the person who, perforce, has to be a loner, but all those who aspire to the RAE. Remember, it is unlikely that any two candidates will be starting from precisely the same level. There is the newcomer to electronics, who, by sheer enthusiasm, will spend every possible moment studying both the theoretical and practical side of our hobby, and there is the electronic engineer, with degrees after his name, who needs to swot up on certain aspects of the subject before sending in the rather exhorbitant entrance fee. Today, it behoves every candidate for the RAE to be really sure that he is prepared for the exam. Whatever his capabilities may be on the technical side he must still swot up on the legislation governing the issue of an amateur licence. Part 1 of the exam is not in the least difficult but a failure in this part means a failure of the whole paper, even if you are a veritable genius at electronics!

So we hope that our RAE course will help readers of all technical abilities and, probably, many other readers too, who may never have heard of the RAE!

Eric Dowdeswell *Assistant Editor*

PLEASE NOTE

We do not operate a Technical Query Service except on matters concerning constructional articles published in PW. We do not supply service sheets or information on commercial radios, TV's or electronic equipment.
All queries must be accompanied by a stamped self-addressed envelope otherwise a reply cannot be guaranteed.

NEWS... NEWS... NEWS...

New catalogue

Bi-Pak has announced the publication of its latest catalogue containing over 120 pages of electronic component listings. There are numerous, albeit rather small, pictures and line drawings. The semiconductor section generally includes pinout details and limited operational parameters. The cost is 50p + 15p postage.

Bi-Pak Semiconductors, The Maltings, 63A High Street, Ware, Herts SG12 9AD.

Audio Fair '77

Don't forget that the Audio Fair '77 is coming shortly and promises to be the most comprehensive ever staged. Displays will range from the most sophisticated BBC/IBA/GPO Data transmission modes to the more mundane HiFi equipment, TV games and home movie apparatus.

The show which is at London's Olympia will open from 2pm-9pm on September 13th, from 10am to 9pm on September 14th, 15th, 16th and 17th, and from 10am to 8pm on Sunday, September 18th. Admission will be 70p for adults, and children under 14, 30p.

New distributor

Plessey Aerospace has appointed Sasco as sole stockist for their complete range of Plessey miniature relays. Products covered by this agreement include half-crystal-can and full-crystal-can types (sealed and unsealed), hermetically sealed 10A crystal-can versions, and rotary armature Type II relays.

Sasco, PO Box 2000, Crawley, Sussex.

New service

Audio Workshops Ltd., have now opened their new showroom at 33 London Road, Southborough, Tunbridge Wells, Kent, where they will be stocking a wide variety of FM aerials, aerial accessories, cables, rotators and electronic car aerials.

The showroom also displays a wide variety of aerial amplifiers from simple low-cost single transistor amplifiers to high quality semi-professional low noise masthead amplifiers.

Full advice as to which aerial or accessory should be purchased to obtain optimum performance will be available from the founder of Audio Workshops, Mr Peter Dunkley. And as a small incentive to go along and see what's available, the firm is offering a high quality 8 element FM aerial at £12·75—for a limited period.

A winner

Marshall's have produced a brand new catalogue in a much larger format than before, a bit bigger than this issue of PW. Many new lines include microprocessors and supporting devices, a range of Digital Multi Testers and a pull-out Transistor Guide for the shack wall. Cost is 25p to callers or 35p by post.

A Marshall (London) Ltd., 42 Cricklewood Broadway, London NW2 3ET.

Talking show

An exhibition to commemorate Thomas Edison's invention in 1877 of the Talking Machine is to be held in conjunction with the British Institute of Recorded Sound during August. Comprising some 125 exhibits, the theme of the displays will be the evolution of the phonograph and gramophone from the original hand turned models to today's HiFi. Early original records together with some interesting accessories complete the displays.

Spare parts manufactured by the organisers of the exhibition for collectors will also be available, as will reprints of early catalogues, posters and instruction manuals.

Called "100 years of Recorded Sound" the exhibition will be open to the public from Saturday 13th August to Saturday 27th August (excluding Mondays). Opening times will be 10am until 6pm.

Further information from Goodwin Eve, City of London Phonograph & Gramophone Society, Farm Cottage, High Road, Chipstead, Surrey. Tel: 07375 54827.

Jermyn gen

Jermyn Distribution have now made available the new National Semiconductor MOS/LSI Databook. Containing 400 pages divided into 14 sections, this Databook lists details of electronic organ and TV circuits; A/D converters; communications/CB radio circuits; watches, calculators and keyboard encoders.

In each section, complete characteristics, connection details, function descriptions, and block diagrams are all covered, while the last chapter gives physical dimensions of all National Semiconductor products together with a definition of terms. Priced at £5·95, it can be obtained from *Jermyn Distribution, Sevenoaks, Kent.*

Part of Ron Ham's early wireless collection which is on display at The Cornwall Aircraft Park, Helston, Cornwall until October 31st. Some of the items on exhibition were featured in *Practical Wireless*, September 76. On the left hand side of the show case is a copy of the article which was published in The Times newspaper, September 26, 1975 about the collector and his historic pieces. Ron is a very fervent supporter of the new industrial museum that is to be built at Houghton in Sussex and which, he expects, will be the permanent home of his collection that dates back to 1900.

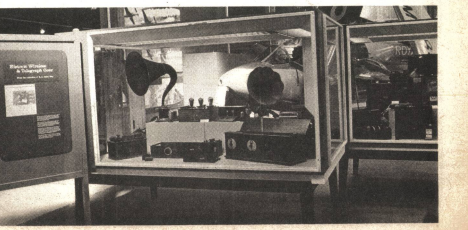

So you want to pass the R.A.E. (Radio Amateurs' Examination)?

No. 1

John Thornton Lawrence GW3JGA & Ken Mc Coy GW8CMY

The passing of the Radio Amateurs' Examination, set by the City and Guilds, requires a certain level of theoretical technical knowledge. Whether one considers that this level is too high or too low is beside the point. The course that follows is intended, with the help of certain external aids, to prepare the reader to pass the examination. It will not teach him all about electronics!

The Radio Amateur is a privileged person indeed, he has access to various parts of the radio frequency spectrum which enable him to talk to other amateurs near to him or in any other part of the world. The Radio Amateur has his own international language, he belongs to a worldwide brotherhood of Radio Amateurs whose "Ham Spirit" takes no account of race, colour, political or social outlook. To ensure that these privileges are not abused, the Licensing Authority (the Home Office) require some test of the would-be amateur's technical competence and knowledge of the radio "Highway Code", before giving him a licence to drive on the frequency motorways of the world, in short, the Radio Amateurs' Examination.

ABOUT THE AUTHORS

John Thornton Lawrence. T.Eng. (C.E.I.), F.S.E.R.T., *is a Senior Scientific Officer concerned mainly with electronic instrumentation, measurements and calibration. He obtained his licence GW3JGA in 1953 and his amateur TV licence GW3JGA/T (later GW6JGA/T) in 1958. He is a Committee member of the British Amateur Television Club and a Founder of the University College of North Wales ARS.*

His hobbies include amateur VHF, UHF and TV equipment, collecting antique radio gear, particularly valves, wine and beer making and helping the local Scout Group. He is married with two sons, 19 and 9.

Ken McCoy *holds an HNC in Electrical and Electronic Engineering and is concerned with instrumentation and electron microscopy. He is a part-time lecturer for the Radio Amateur's Examination course at the Gwynedd Technical College.*

He obtained his licence GW8CMY in 1967 and his main interest is in building portable 2m equipment. His other hobbies include mountaineering in the UK and on the Continent, photography and DIY home improvements. He is a team leader in the Ogwen Valley Mountain Rescue Organisation. He is married with a son, 14, and two daughters, 12 and 6.

. . . 'writing to the City and Guilds'

Maybe you are one of those whose interest in Amateur Radio has been building up steadily for some time and the point has now been reached where you have to decide whether or not to enter for the R.A.E. If you are dithering on the brink, you may be interested to know that this is the first of a series of articles concerned with preparing for and successfully taking the Radio Amateurs' Examination. It is not intended to be a complete course leading up to the R.A.E. but more of a progressive clarification of some of the problem areas which can be the undoing of many candidates.

The main core of information is best obtained from books specially written for the Radio Amateur and for the R.A.E. in particular and these will be referred to from time to time. Practical work is an important part of preparing for the R.A.E. and suggestions for this will be included where necessary. If by now you have decided to proceed, then please read on.

Taking stock

We are very pleased to see that you have now made up your mind to have a go at the R.A.E. Before we do anything else, let's take stock of the situation. You say that you did the usual basic arithmetic in school (but that seems a while ago!) and you naturally feel a bit rusty in that area and with electrical theory, even more so. OK, so some work is definitely required to bring these up to scratch.

How about circuits? You're able to follow some of the simple circuits without much difficulty but find it quite a struggle to explain, in so many words, how they work. Well, perhaps this is just because you are not looking at them in the right way, so more about that later.

Now the practical side. You say that you have built up the odd electronic circuit from *PW* and have got it working OK, fine! By the way, do you go to the

local Amateur Radio Club meetings? No? Pity! You see, it's very helpful if you can do some practical work in connection with the R.A.E. and membership of the local Radio Club is very useful in this respect as it will give you the chance to see amateur radio equipment being used and to obtain some guidance and help when you are building things for yourself. Write to the R.S.G.B. for details of your local club as many clubs are affiliated to the R.S.G.B.

Preparations

You will need to get some books and information on the examination, past R.A.E. papers and so on. These take a little time to come so I suggest that you order these now. First write to: The City and Guilds of London Institute, 76 Portland Place, London W1N 4AA, for Pamphlet 765 Radio Amateur's Examination 1976-1978, including a set of Question Papers for the last three years. Remember to enclose a cheque or P.O. for 40p. This represents very good value, as usually each set of City and Guilds Question Papers is extra.

The Home Office publishes a useful document about becoming a Radio Amateur and this is available free of charge. Write to: The Home Office, Radio Regulatory Dept., Waterloo Bridge House, Waterloo Road, London SE1 8UA, for leaflet "How to become a Radio Amateur".

Now, moving on to textbooks and booklets, these can be roughly divided into two categories, the essential, and the desirable but not essential. The essentials, which are all published by the Radio Society of Great Britain, can be obtained from your local bookshop (if you want to use up that birthday book token from auntie!) or, cash with order, from: R.S.G.B. Publications (Sales), 35 Doughty Street, London WC1N 2AE.

They are:

"A Guide to Amateur Radio" by Pat Hawker G3VA. £1·35.

"The Radio Amateurs' Examination Manual" by G. L. Benbow G3HA. £1·35.

"Radio Amateurs' Revision Notes" by G. L. Benbow G3HA. 61p.

The books in the second category are much more comprehensive and naturally cost more. These are also available from R.S.G.B. Publications (Sales) but as an alternative to immediate purchase, they may be obtained from your local library. They are: Radio Communication Handbook (R.S.G.B.) 5th Edition Vols. 1 and 2, or Radio Amateurs' Handbook 1977 (A.R.R.L.).

Getting down to it

The method of studying for the R.A.E. depends on your personal circumstances. The various ways are:

(a) Evening classes.
(b) Correspondence course.
(c) Home study, with or without some tuition.

If you live near a technical college or school which runs evening classes, then this is probably the best way for you to study. A direct approach to the college or school will provide you with full details. Correspondence courses or home study for the R.A.E. require continuous and regular work sessions. Home study requires a lot more personal discipline to get through the more difficult items as you will find it a great temptation to leave them until the end, when it is usually too late!

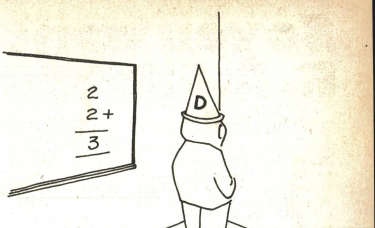

. . . 'mathematics a bit rusty?'

It is always useful, and particularly so in the case of home study, if you can enlist the help of a local Radio Amateur or suitably qualified friend, who will talk-through any problems you may have.

Here we are then, you have registered at your local evening institute for the R.A.E. course, the books are ordered and you are ready and waiting to get down to the "nitty gritty".

Arithmetic

Let's start with arithmetic (we always think that the word arithmetic is less daunting than mathematics). There are going to be some calculation questions in the R.A.E. and if you can do these correctly, you can gain full marks on each question in a matter of minutes. Even fairly straightforward electrical calculations can present very real difficulties if you have not seen the sharp end of a blackboard pointer since you left school, so the purpose of this section is to remind you of the basics involved in these sums and to suggest a few tricks to make them easier to execute and remember.

If you have read through the instruction book of a pocket calculator you will know that there are four "basic arithmetical functions", namely, addition, subtraction, multiplication and division.

Addition and Subtraction—So far as the problems that you will meet in the R.A.E. are concerned, addition and subtraction will take care of themselves, for example, $3+7=10$ and $4-2=2$. Multiplication and division may be written down in several different ways, so here are a few alternatives.

Multiplication—$A \times B$ can also be written as A.B. or simply AB.

Division—$A \div B$ can also be written as $\frac{A}{B}$. Thus $1 \div 2$ is the same as $^1/_2$ ("one upon two" or "one over two").

Now for the not-so-basic arithmetic functions, reciprocals, squares and square roots.

Reciprocals—The reciprocal of A is $\frac{1}{A}$ or from division $1 \div A$ or "one upon A", and to put it numerically, the reciprocal of 4 is $^1/_4$ and of 100 is $\frac{1}{100}$.

This function, together with the squares and square roots, occurs often in resonance and frequency calculations.

Squares—If a number is multiplied by itself the answer is known as the square of the number. For example, $A \times A$ is written as A^2 or "A squared". Thus A^2 is the square of A. And, to put it numerically, 9 is the square of 3, since $3 \times 3 = 9$.

Square Roots—The square root of a number is a figure which, when multiplied by itself, is equal to the original number. For example, the square root of 9 is 3 because when 3 is multiplied by itself, it equals 9, written $\sqrt{9} = 3$ because $3 \times 3 = 9$. Similarly, $\sqrt{25} = 5$ (because $5 \times 5 = 25$) and $\sqrt{4}$ or "Root 4" $= 2$ ($2 \times 2 = 4$) and so on.

Incidentally, not all square roots are whole numbers. For instance, $\sqrt{2}$ has been calculated to at least 50 decimal places, but is used most often as 1·41. Finally, $\sqrt{2} \times \sqrt{2} = 2$ and $\sqrt{5} \times \sqrt{5} = 5$ and $\sqrt{25} \times \sqrt{25} = 25$.

Problems in the actual R.A.E., which involve finding the square roots of numbers, can be dealt with by looking up the value in the square root tables which are provided.

Multiples and sub-multiples

Some of the electrical units that are used in radio are inconveniently small for practical purposes and so a multiple of the unit is used. Some others, for example, the Henry and the Farad, are inconveniently large. A one Farad capacitor having a particular dielectric between its plates, might occupy a volume similar to that of a block of flats!

The capacitors and inductors used in radio work have values which are sub-multiples of the Farad and the Henry. You will, therefore, need to be able to recognise multiples and sub-multiples in words and in figures.

Multiples—Multiples are described by a prefix to the unit in question. For example, 1 Megohm = 1,000,000 ohms. A list of multiple prefixes is given below.

Prefix	Letter		Index Form
tera	T	one million million	10^{12}
giga	G	one thousand million	10^{9}
mega	M	one million	10^{6}
kilo	k	one thousand	10^{3}
hecto	h	one hundred	10^{2}

Sub-multiples—Sub-multiples are described by a letter prefix in a similar fashion. For example, 0·000,001 Farad = 1 microfarad = 1μF. A list of sub-multiple prefixes is given below.

Prefix	Letter		Index Form
deci	d	one tenth	10^{-1}
centi	c	one hundredth	10^{-2}
milli	m	one-thousandth	10^{-3}
micro	μ	one millionth	10^{-6}
nano	n	one thousand millionth	10^{-9}
pico (or $\mu\mu$)	p	one million millionth	10^{-12}

Indices

You will notice from the previous sections that the multiplier and sub-multiplier are written as a figure followed by or preceded by a number of noughts. This number, when expressed in what is known as "index form", uses a special notation which is best shown by example:

mega = 1,000,000 In index form 10^6
giga = 1,000,000,000 In index form 10^9

In the case of multiples, the index number is equal to the number of noughts following the figure, so that, for example:

2·2 Megohms is written as $2 \cdot 2 \times 10^6$
and 7·3 Gigahertz is written as $7 \cdot 3 \times 10^9$ Hertz.

Sub-multiples use the same notation but with a slight difference:

pico $= 0 \cdot 000,000,000,001 = 10^{-12}$
micro $= 0 \cdot 000,001 = 10^{-6}$

You will notice that in the case of sub-multiples, the index number is **minus** and equivalent to the **number of noughts** plus one following the decimal point. For example:

2·2 picofarads $= 2 \cdot 2 \times 10^{-12}$ Farads.
7·3 microhenrys $= 7 \cdot 3 \times 10^{-6}$ Henrys.

It is often desirable to convert from one multiple of an electrical unit to a different multiple and this can be done by moving the decimal point and at the same time changing the index number accordingly. For example:

$2 \cdot 2$ Megohms $= 2{,}200{,}000$ ohms
$= 220{,}000 \times 10$ ohms
$= 22{,}000 \times 10^2$
$= 2{,}200 \times 10^3$ ohms (kilohms)
$= 220 \times 10^4$ ohms
$= 22 \times 10^5$ ohms
$= 2 \cdot 2 \times 10^6$ ohms (Megohms)

Similarly,

$0 \cdot 000,000,002$ Farads $= 0 \cdot 002 \times 10^{-6}$ Farads
$= 0 \cdot 002$ microfarads (μF)
$= 2 \times 10^{-9}$ Farads
$= 2$ nanofarads (nF)
$= 2{,}000 \times 10^{-12}$ Farads
$= 2{,}000$ picofarads (pF)

Multiplying—When **multiplying** figures in index form it is only necessary to **add** the indices. For example:

$10^4 \times 10^6 = 10^{10}$
$10^4 \times 10^{-6} = 10^{-2}$
$10^{-4} \times 10^6 = 10^2$
$10^{-4} \times 10^{-6} = 10^{-10}$

Dividing—when **dividing** figures in index form it is only necessary to **subtract** the indices. For example:

$$\frac{10^6}{10^4} = 10^6 \div 10^4 = 10^2$$

$$\frac{10^{-6}}{10^{-4}} = 10^{-6} \div 10^{-4} = 10^{-2}$$

$$\frac{10^{-6}}{10^4} = 10^{-6} \div 10^4 = 10^{-10}$$

Also

$$\frac{10^{-6}}{10^4} = 10^{-6} \times 10^{-4} = 10^{-10} *$$

* An alternative way to deal with an index quantity that you are dividing by is to change the sign of the index and multiply, by adding the indices.

continued on page 342

GENERAL PURPOSE SW RECEIVER

Part 1

F.G.RAYER G3OGR

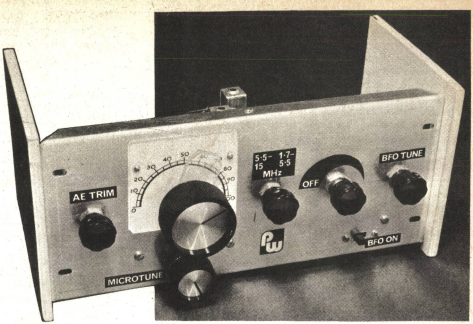

A frequency coverage of approximately 1·7MHz to 15MHz includes many useful bands and is obtained in this receiver by two switch-selected ranges. The tuned circuits comprise the four coils shown in **Fig. 1**, and a few points should be noted.

As an intermediate frequency of 1·6MHz is used, greater freedom from second channel interference is obtained than with a 470kHz IF. Despite this, it is not possible to avoid such interference with a single tuned circuit, especially at higher frequencies, so a matching tuned RF preselector unit is advisable and this can be added later if wished (Part 2). With the RF preselector connected the RF stage drain is supplied via R1, to make use of the primaries of the coils L1 and L2. **C1 is external to the receiver.** If it is not intended to add the RF unit, C2 and R1 can be omitted, and pins 9 of L1 and L2 connected to chassis.

Circuit Description

The 4-pole switch S1a-d selects the appropriate pair of coils. These are tuned by the ganged capacitor VC1/2. Instead of having four pre-set trimmers, TC1 is provided across VC2, and VC3 is a panel control. This provides much more latitude in alignment. VC4 is the oscillator bandspread or fine tuning capacitor, which is useful for precise tuning or listening over a narrow band.

Data for the coils used specify a 960pF padder CP1 for L3, and 340pF padder CP2 for L4 using a 2 x 315pF gang. However, 1000pF and 330pF will be suitable and are more easily obtainable. The larger capacity gang is also a standard item and simply increases coverage slightly.

In **Fig. 2**, Tr1 is the mixer with L1/L2 switched to gate 1 and the oscillator coupled to gate 2 via C6. Tr2 is the oscillator with C7 going to L3/L4 and drain feedback via S1c. As Tr1 is a protected gate device no particular care is needed beyond that generally taken to avoid overheating while soldering.

IFT1 couples the mixer output to the first IF amplifier Tr3, which also receives AGC base bias through R8 and R10, from D1. Tr4 is the second IF stage. D1 provides AGC and the audio signal developed across the volume control VR1. When S5 is closed, the BFO oscillator Tr5 is on and it is coupled to D1 by C15. This allows reception of CW (Morse) and SSB (single sideband) signals. The panel control VC5 is for adjusting the BFO frequency. Should the receiver be required for ordinary SW broadcast reception only, then S5, R14, R15, C14, C15, C16 and Tr5 and the associated circuitry may be omitted as this stage is not used for AM reception, but this is not recommended.

This circuit is assembled on a single board, with the exception of controls VR1 and VC5.

The audio amplifier consists of a TBA800 IC, **Fig. 3**, and provides useful gain and output without too much

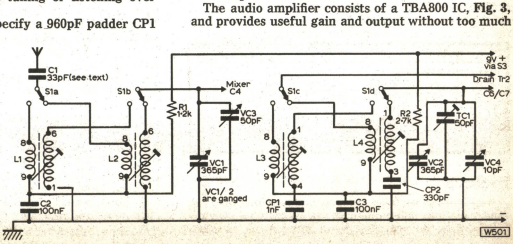

Fig. 1: The circuit diagram is shown in three parts. This circuit is of the four-coil switched aerial and mixer input section. Two bands, 1·7 to 5·5 and 5·5 to 15MHz are provided.

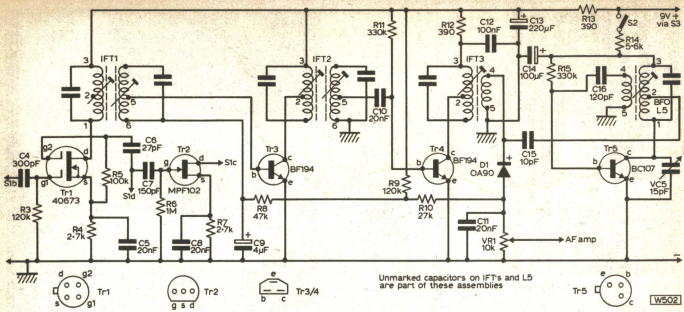

drain on the battery. It is intended for use with a 16Ω speaker but may be used with phones for individual listening.

The audio amplifier is wired on its own board which fits under the chassis. R19 can be two 2·2Ω resistors in parallel if any difficulty arises in obtaining 1Ω.

Metalwork

Flanged "universal chassis" members from Home Radio allow an inexpensive case to be made easily. The panel used is 9 x 4in and the chassis 8 x 4in so that it may fit inside. It is secured 1in up, with three bolts. If panel and chassis members are the same length, two corners of the chassis part must be cut away so that it will fit inside the flanges on the panel.

A clearance hole is required for the ganged capacitor which has an integral ball drive. The BFO switch S2 occupies a slot, which can be made by drilling a few small holes and filing. The mixer-IF board has four fixing bolts, and the AF board two bolts. To assure an easy fit, boards and chassis can be drilled together before mounting any components.

Construction

Two 4BA bolts secure the ganged capacitor. Solder a lead to the central frame tag of this before fixing it in place. It is necessary to use washers or other spacers between it and the chassis, and to watch that the bolts do not project very far inside the front of the capacitor. VR1 and other controls can then be fixed to the panel. When placing the coils on the chassis, tighten their fixing nuts **with the fingers only.** Most of the wiring in Fig. 1 can then be finished, keeping leads reasonably short and direct. If the coil pins are dull clean them before soldering. It is necessary to avoid lengthy heating of the pins and to see that they are not displaced.

Fig. 4 will assist in wiring. One tag of S6 is used as a point for R1, R2, S2 and R13 positive connections. The AF amplifier positive circuit is made at S2, under the chassis. VC4 is directly under the ganged capacitor, so a lead passes down through a hole to it from VC2. **Fig. 5** will allow the switch wiring to be checked.

Fig. 6 shows both sides of the mixer-IF board. It should first be drilled for the IFTs, including the

Fig. 2: above, shows the mixer stage Tr1 and oscillator Tr2. Tr3 and 4 are the IF amplifier stages feeding the diode detector D1.Tr5 is the optional BFO stage. Fig. 3: below, is the IC audio amplifier.

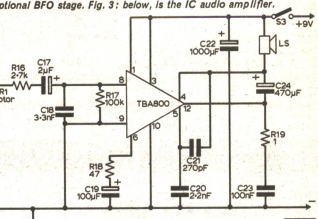

centre holes so that the lower cores can be reached. Each of the points MC is a tag secured with a $\frac{1}{2}$in 6BA bolt. Later, extra nuts allow the board to be mounted by these bolts, with clearance for wiring. Sleeving should be put on the positive circuit wiring to pins 3 of the IFTs, but is not needed elsewhere.

Provide coloured insulated leads for all external connections. These can be yellow for VC1 (S1b), black for VC2 (S1d), brown for S1c, red for positive, pink for S2, and yellow-green for VR1. When the board is fixed with lock nuts, cut these leads as required and solder them to the capacitor and other components.

The audio board is wired as in **Fig. 7**, and is mounted in the same manner as described for the other board. Connect R16 to VR1 wiper and positive to the positive line at S2. The board is placed under the chassis, at the right. It is important to note that both sides of the speaker circuit are insulated from the metal and negative line.

IF Alignment

As the IFTs are pre-tuned by the manufacturer they should not be adjusted until reasonable reception is being obtained. They can then be set for maximum volume, by rotating the cores with a proper trimming tool. Choose a weak, steady signal for this

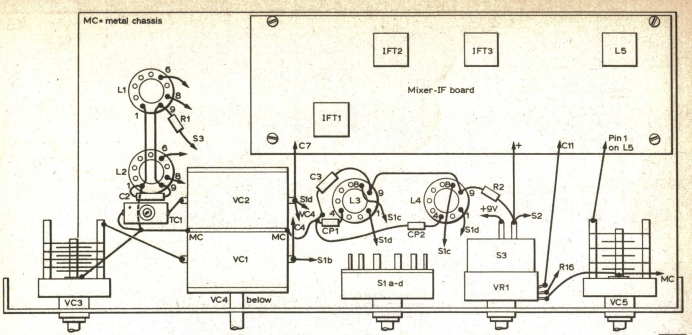

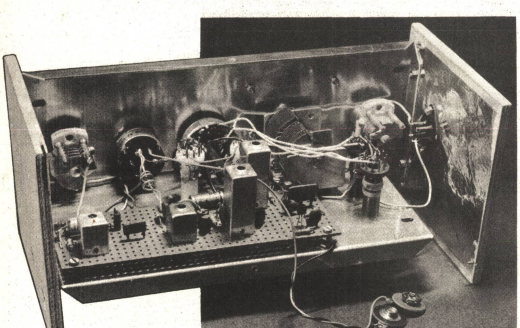

Fig. 4: above, shows the layout of the panel-mounted controls and the position of the mixer-IF board on the chassis. The photograph of the back of the receiver complements Fig. 4 and also shows the piece of aluminium foil stuck to the inside of the case to shield the coils when the pre-selector is used with the receiver. Fig. 5: below left, is the wiring between the band switch and the four coils.

W505

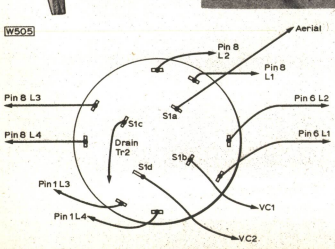

operation. It is a good idea to place the audio board so that the lower cores of IFT1 and IFT2 can be reached through holes in the chassis, or to raise the IF board sufficiently to reach these cores. If the latter method is used, provide a return lead from the negative line to chassis. When the five cores have been peaked up for best results, they need no further adjustment. Alternatively, a signal generator, set to 1·6MHz, may be used for precise alignment after the set is working.

BFO Adjustment

Initially tune in a steady AM signal precisely and set VC5 half closed, then switch on the BFO with S2. Set the core in L5 so that a strong audio heterodyne is heard and rises in pitch when VC5 is turned either way from the central, zero beat position. This oscillator is never in use for AM reception, only for CW

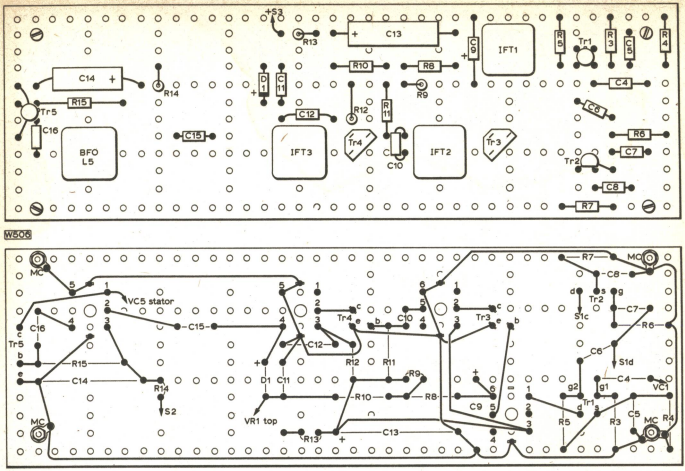

Fig. 6: Wiring and component location on the mixer-IF board is given here, from above and below. The drawings are not to scale.

★ components

Resistors

R1 1·2kΩ	R8 47kΩ	R15 330kΩ	
R2 2·7kΩ	R9 120kΩ	R16 2·7kΩ	
R3 120kΩ	R10 27kΩ	R17 100kΩ	
R4 2·7kΩ	R11 330kΩ	R18 47Ω	
R5 100kΩ	R12 390Ω	R19 1Ω	
R6 1MΩ	R13 390Ω	VR1 10kΩ log pot	
R7 2·7kΩ	R14 5·6kΩ	with switch S3	

All ¼ or ⅓W 5%

Capacitors

C1 33pF see text	C13 220μF 10V		
C2 100nF	C14 100μF 10V		
C3 100nF	C15 10pF silver mica		
C4 300pF silver mica	C16 120pF ,, ,,		
C5 20nF	C17 2μF 10V		
C6 27pF silver mica	C18 3·3nF		
C7 150pF ,, ,,	C19 100μF 10V		
C8 20nF	C20 2·2nF		
C9 4μF 4V	C21 270pF silver mica		
C10 20nF	C22 1000μF 10V		
C11 20nF	C23 100nF		
C12 100nF	C24 470μF 10V		
CP1 1nF silver mica	CP2 330pF silver mica		
VC1/2 2 x 365pF with slow motion (Jackson type O2)			
VC3 50pF variable (Jackson type 804)			
VC4 10pF ,, ,,			
VC5 15pF ,, ,,			
TC1 50pF compression trimmer			

Note:—1 nanofarad (1nF) = 1000pF

Semiconductors

Tr1 40673	Tr5 BC107		
Tr2 MPF102	D1 OA90		
Tr3 BF194	IC1 TBA800		
Tr4 BF194			

Inductors

IFT1 Denco type IFT18/1·6
IFT2 Denco type IFT18/1·6
IFT3 Denco type IFT17
L5 Denco type IFT17
L1 Denco range 4, blue, valve type
L2 Denco range 3, blue, valve type
L3 Denco range 4, white, valve type
L4 Denco range 3, white, valve type

Miscellaneous

S1, 4-pole 2-way rotary switch. S2, on-off slide switch. S3, on-off switch, part of VR1. Perforated board 0·15in. matrix 5½ x 1⅛ and 3½ x 2in. Knobs. Flanged members for panel and chassis (Home Radio). Battery PP6 9V with terminal connectors. Material for cabinet.

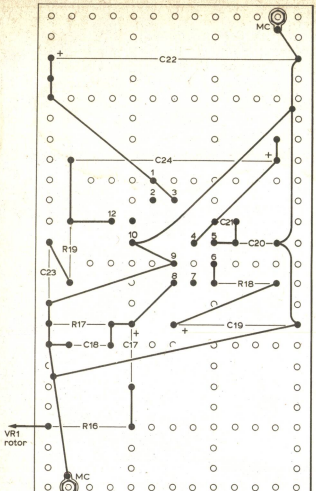

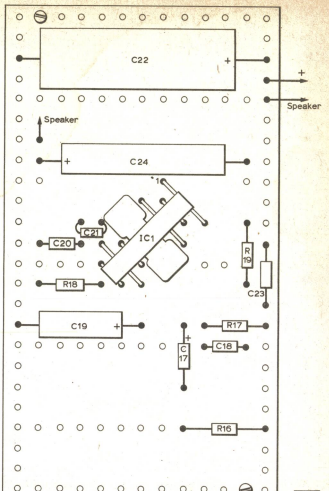

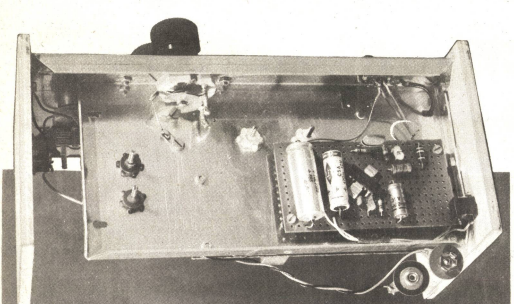

Fig. 7: above, is the piece of Veroboard, 0·15in. matrix, carrying the IC audio amplifier stage. Again, this is not to scale. This board is mounted underneath the chassis as can be seen in the photograph, left. The variable capacitor, top left, is the Microtune or bandspread tuning control, VC4.

or SSB. For CW, set VC5 to produce the wanted audio pitch. With SSB, more critical adjustment of VC5 is necessary, to obtain the best resolution of speech. Remember that lower sideband is used below 10MHz and upper sideband above.

Due to the way in which D1 operates, satisfactory resolution on SSB makes it necessary that the signal at the diode should not be too strong. When the RF stage is built, a control on this allows gain to be reduced. However, when the receiver is operated without this stage other means of reducing the input from strong SSB signals will have to be employed. Trouble from excessively strong signals at D1 will be unlikely with weak stations and a short aerial, but

will certainly occur with a better aerial, and with strong transmissions. A 50pF or similar variable capacitor in the aerial lead will then be worth while, or a small fixed capacitor as in Fig. 1.

Aerial/Oscillator Tuning

Trimmer TC1 is screwed down about half way so that when the coil cores are adjusted, signals peak up with VC3 about one-third to two-thirds closed. Band coverage is adjustable between quite wide limits and depends largely on the positions of the cores. For approximately 1·7MHz to 15MHz, set them so that about $\frac{1}{2}$in of the 6BA screwed rod projects. Subsequently, adjust the aerial coil cores, one for each band, so that VC3 allows peaking up of signals throughout each range.

Should alignment here be somewhat in error, it will be necessary to re-adjust VC3 for best reception when tuning. This will not cause any lack of efficiency, provided VC3 is neither fully open nor fully closed. Adjust the aerial coil cores near the low frequency end of the bands to minimise this. The bands covered are approximately 1·7 to 5·5MHz and 5·5 to 15MHz.

Operating Notes

Space is left inside the receiver for a PP6 9V battery. Any wire aerial, including an indoor wire, may be used. Long wire aerials should be coupled with a trimmer or other capacitor, as described, to help reduce the second channel interference which will otherwise arise. (This is greatly reduced by the RF preselector mentioned.) An earth connection will sometimes increase the volume of weak signals, especially at the lower frequencies. It is possible to arrange the coverage to tune to 1·5MHz if required, but whistles must be expected around 1·6MHz (the receiver IF).

A fairly large speaker in a suitable cabinet is best. High resistance or high impedance headsets can be used, provided a resistor is connected across them, about 16Ω. The combination is much less sensitive than when using 16Ω phones, but this is not too important because of the high audio output available.

Note that C1 cannot be left in circuit when using the preselector.

Tuning dial

The main tuning dial cursor is made from a small piece of thin clear plastic sheet. A hairline is scribed length-wise on the back. A hole is drilled to take a $\frac{1}{4}$in. internal diameter grommet which is pushed on to the spindle of the tuning capacitor before the knob is fitted. The tuning scale is also clear plastic sheet, backed with white card.

Cabinet

The cabinet can be made from universal chassis members, or some parts may be of wood. Using 6mm ply, the sides should be $4\frac{1}{2}$ x $4\frac{1}{2}$in each, and the top and back each 9 x 4in. The side near L1/L2 is lined with an aluminium plate or kitchen foil 4 x 4in to avoid coupling with the preselector coils when this unit is adjacent to the receiver.

Part 2 next month will give full details of the RF preselector for use with this receiver.

R.A.E.—*continued from page 336*

Squares and square roots

If you wish to square an index quantity it is necessary to double the index figure. For example:

10^3 squared $= 10^6$ and 10^{-6} squared $= 10^{-12}$

If you wish to find the square root of an index quantity it is necessary to half the index figure. For example:

$\sqrt{10^6} = 10^3$ and $\sqrt{10^{-6}} = 10^{-3}$

If the index quantity contains a number, for example:

$\sqrt{81 \times 10^8}$ this may be represented by $\sqrt{A \times B}$. First, square root part A, second, halve the index figure of B, thus: $\sqrt{81 \times 10^8} = 9 \times \sqrt{10^8} = 9 \times 10^3 = 9{,}000$.

Indices in calculations

Let's look at a typical problem that might arise in the examination, such as finding the resonant frequency of a capacitor—inductor combination,

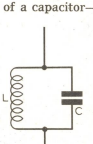

L = 1 microhenry (1μH)
C = 1 microfarad (1μF)

$$f = \frac{1}{2\pi\sqrt{LC}}$$

If this equation is written out in figures, it is rather large and cumbersome, as shown below:

$$f = \frac{1}{2 \times 3 \cdot 142 \times \sqrt{0 \cdot 000{,}001 \times 0 \cdot 000{,}001}}$$

By using indices it is possible to make the whole calculation much simpler. So now re-write in index form:

$$f = \frac{1}{6 \cdot 284 \times \sqrt{1 \times 10^{-6} \times 1 \times 10^{-6}}}$$

add the indices:

$$f = \frac{1}{6 \cdot 284 \times \sqrt{1 \times 10^{-12}}}$$

square root by halving the indices:

$$f = \frac{1}{6 \cdot 284 \times 10^{-6}}$$

rearrange:

$$f = \frac{1 \times 10^6}{6 \cdot 284} = \frac{1}{6 \cdot 284} \times 10^6$$

$$f = 0 \cdot 16 \times 10^6 \text{ Hertz}$$

$$f = 160 \times 10^3 \text{ Hertz}$$

$$f = 160 \text{ kilohertz (kHz)}$$

The values of L and C used in this example are not typical for this frequency but were chosen to demonstrate the use of indices in calculations.

Next month a start is made on Electricity and Magnetism, reviewing the characteristics of common components such as resistors, capacitors, transformers and magnets.

FREE BLOB BOARD

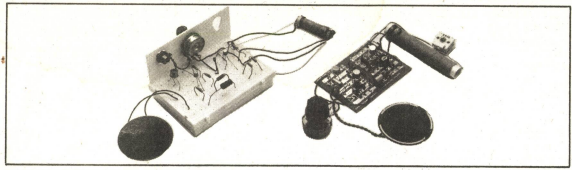

Build this radio-receiver, electronic flasher, binary counter, LC Oscillator, 3 stage amplifier, morse practice oscillator, light-operated switch, CR Oscillator, Wien Oscillators, S-DeC + control panel + 9 project instruction book + **Free Blob-Board** Only **£2.25** + £0.40 post and VAT.

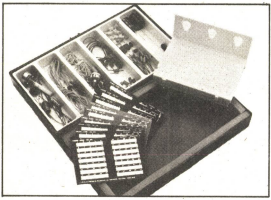

S-De-K-IT

This **S-De-K-IT** contains 1 S-DeC + Control panel + 9 Blob-Boards + 20 double-ended leads + Instructions to build 9 projects. Complete in work box with component tray. **S-De-K-IT** Only £4.95 + £1.00 post and VAT. + Free 9 Extra Blob Boards.

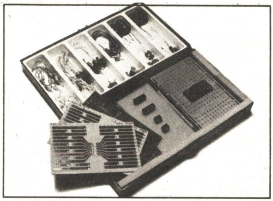

T-De-K-IT

This **T-De-K-IT** contains 1 T-DeC + Contol panel + 16 Dill carrier + 4 IC Blob Boards + 41Cs + Components + Leads + Circuit Diagrams + Instructions to build, Burglar Alarm + Sound Fuzz Circuit + SR Latch + Two Tone Siren. Complete Kit with all Components **£13.00** + £1.66 post and VAT. + **Free 4 extra IC Blob Boards.**

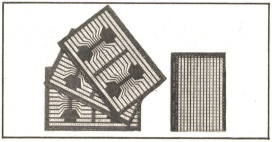

Buy pack of 3 2V5 Blob-Boards and Get 1 21C Blob-Board Free
Please rush me
.....Packs of 3 2V5 + My Free 21C Blob
For only £0.62 per pack of 3.
Please add 20p for Post + VAT for all orders

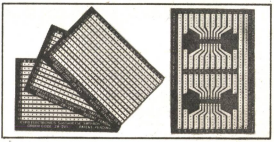

Buy pack of 3 2-IC Blob-Board and Get 1 2V5 Blob-Board Free.
Please rush me
.....Packs of 3 21C + My Free 2V5 Blob
For only £1.01 per pack of 3.
Please add 20p for Post + VAT for all orders

Offer available from all good component stockists. Save on post.

PB Electronics (Scotland) Ltd.
57 High Street, Saffron Walden, Essex CB10 1AA England. Tel: Saffron Walden 22876.

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT @ 8%

12 AND 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS

Ref	12V	24V	£	P & P
111	5	0-5	2-29	0-75
113	1-0	0-5	3-49	0-75
71	2	1	3-49	0-75
72	3	1-5	4-49	0-75
100	4	2	5-35	0-96
101	5	3	6-49	1-14
102	10	5	7-67	1-14
116	12	6	8-99	1-32
117	16	8	10-39	1-32
115	20	10	13-19	2-08
187	30	15	17-95	2-08
286	60	30	29-95	O/A

30 VOLT RANGE

Prim 220/240V Sec 0-12-15-20-24-30V
Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 16, 20, 24, 30V 15-0-15V, 12-0-12V

Ref	VA	£	P & P
112	2-5	4-49	0-75
70	3	5-27	0-96
80	3-0	5-27	0-96
81	3-0	6-28	1-14
82	4-0	7-44	1-14
83	5	8-37	1-32
84	6	9-49	1-32
85	8	11-73	1-64
89	10-0	13-33	1-64

60 VOLT RANGE

Prim 220/240V Sec 0-24-30-40-48-60V
Voltages available 5, 8, 10, 12, 15, 16, 20, 24, 30, 36, 40, 48, 60V or 24-0-24V or 30-0-30V

Ref	VA	£	P & P
124	0-5	3-88	0-96
126	1-0	5-58	0-96
127	2	7-90	1-14
125	3-0	10-54	1-32
123	4-0	12-23	1-64
40	5-0	13-95	1-64
120	10-0	16-95	1-64
121	8-0	20-15	O/A
122	10-0	24-03	O/A
189	12-0	27-13	O/A

MAINS ISOLATING (SCREENED) PRIM 105/240 SEC 120/240 CT

Ref	VA (Watts)	£	P & P
113	20	5-115-210-240	2-48 0-71
150	75	5-115-210-240	3-66 0-96
4	150	5-115-210-240	5-35 0-96
66	250	5-115-210-240	7-75 1-14
160	350	5-115-210-240	10-99 1-14
161	500	5-115-210-240	14-49 1-32
95	1000	5-115-200-220-240	34-82 O/A
96	2000	5-115-200-220-240	64-95 O/A

AUTO TRANSFORMERS

Ref	VA (Watts)	Volts	£	P & P
113	20	0-115-210-240	2-48	0-71
150	75	0-115-210-240	3-66	0-96
4	150	0-115-210-240	5-35	0-96
66	250	0-115-200-220-240	7-75	1-14
160	350	0-115-200-220-240	10-99	1-14
161	500	0-115-200-220-240	14-49	1-32
95	1000	0-115-200-220-240	34-82	O/A
96	2000	0-115-200-220-240	64-95	O/A

CASED AUTO TRANSFORMERS

240V cable in & 115V USA 2 pin outlet

Va	£	P & P	
20	2-96	0-96	113W
150	5-48	1-14	114W
200	9-82	1-45	66W
250	10-49	1-45	66W
350	12-53	1-64	53W
500	15-73	1-64	67W
750	18-55	1-76	83W
1000	22-68	O/A	94W
2000	37-65	O/A	95W

HIGH VOLTAGE MAINS ISOLATING

Prim 200/220V or 400/440V Sec 100/120V or 200/240V

Va	Ref	£	P & P
60	163	5-29	1-32
350	247	14-11	1-84
1000	250	35-95	O/A
2000	252	54-25	O/A

SCREENED MINIATURES

mA/ch	Volts	£	P & P
1A, 1A	0-6, 0-6	1-99	0-55
1A, 1A	0-6, 0-6	2-85	0-78
1A, 1A	0-9, 0-9	2-14	0-78
330, 330	0-9, 0-9	1-99	0-38
500, 500	0-9-0-, 0-9-0	2-59	0-71
1A, 1A	0-8-9, 0-8-9	3-53	0-78
200, 200	0-15, 0-15	1-99	0-38
300, 300	0-20, 0-20	2-56	0-78
700 (DC)	20-0-20 (DC)	3-53	0-78
1A, 1A	0-15-20-0-15-20	4-63	0-96
1A, 1A	0-15-20-30-0-15-20-30	5-38	0-96
1A, 1A	0-15-27-0-15-27	5-38	0-96
5112 500	0-15-20-30-40	5-64	1-14

PLUS

HIGH QUALITY MODULES

15 Watts RMS AMPLIFIER £3-98
25 Watts RMS AMPLIFIER £4-57
45 Watts RMS AMPLIFIER £5-95
15W RMS AMPLIFIER *£6-95
PRE-AMP for 15/45W £6-95
PRE-AMP for 25W £3-75
POWER SUPPLIES 5-10W £1-35
POWER SUPPLIES 25W £3-75
TRANSFORMER 15/45W £4-75
TRANSFORMER 25W £4-75
P & P Modules 35p. Trans 96p. VAT 12½% *VAT 8%

PRINTED CIRCUIT KIT

PC Board, Circuit Marking Pen, Etchant Crystals, Solvent, £2·40 VAT 8%, P & P 40p.

BLOB BOARD (Pack of 3)

0·1" x 0·1" - 1" or 3·75" x 1" - 15" £0·75
0·175" x 0·1" - 1" or 3·75" x 1" - 15" £1·14
0·175" x 0·1" - 2" or 7·5" x 1" - 15" £2·79
IC Range
1·4 - 8·2" £0·96. 4·78" x 7·5" £2·13
VAT 8% P & P 43p

ELECTRONIC CONSTRUCTION KIT

10 projects (including electronic organ). No soldering needed £7·95. VAT 8% P & P 70p.

COMPONENT PACKS

200 Mixed value resistors (count by weight)
200 Mixed value capacitors (count by weight)
30 Mixed value precision resistors 1W 2%
5 Assorted pots and presets
10 Reed switches
5 Assorted slide switches—mixed wattage
5 Pack wire 50 metres assorted colours
Please specify required. 60p per pack
VAT 12½% P & P 40p

Prices correct 23-6-77. Please add VAT after P & P.

BRIDGE RECTIFIERS

		P & P
200V	2A	£0·65 0·09
400V	2A	£0·85 0·09
600V	2A	£0·95 0·09
400V	4A	£0·80 0·23
600V	4A	£1·05 0·23
500V	10A*	£2·25 0·29

VAT 12½% *VAT 8%.

TEST METERS

AVO MK5 £88·95
AVO 71 £28·00
AVO 8 £39·00
AVO MM5 £21·94
AVO 71 in circuit
Transistor Tester £29·00
UA315 in. case £14·95
VAT 8% P & P £1·15
AVO cases and accessories

AUDIO KIT 25W

2+2/5W Amplifiers
1+Pre-Amp
1+Power supply
1+Transformer
1+Front Panel
1+Kit of parts to include on-off switch, neon ind. Stereo headphone socket. Plus instructions book £27·95.
Teak veneered cabinet aluminium chassis, heat sink and front panel brackets plus back panel and sockets etc. £9·20
P & P £1·73 VAT 12½%

RECORD DECK

BSR P184 Single Player with Cartridge £16·90 P&P £1·50

MAGNETIC TO CERAMIC CARTRIDGE CONVERTOR MATCHING VOLTAGE £4·95 ONLY £3·99 P & P 35p VAT 12½%

POWER UNITS

Stabilised 6-12V 1000mA £5·95
3300 fits into 13A socket 6-12V 300mA £3·30
12/8 3, 4, 5, 6, 7·5, 9, 12V 1000mA £5·22

VAT 12½% P & P 55p

DECS SOLDERLESS BREAD-BOARDING

S Deck 70 contacts £1·98
T Dec 208 contacts £2·99
U Dec "B" for I.C.s etc £2·99
U Dec "B" for I.C.s etc £3·79
VAT 8% P & P 43p

ANTEX SOLDERING IRONS

15W £3·49 Stand £1·48
25W £3·49 Stand £1·48
Soldering Iron kit £3·15
VAT 8% P & P 43p

TI MINI-MULTIMETER

DC-1000V AC-1000V 10Meg-ohm A Res-150Ω Ω 1000Ω/V Bargain £5·99
VAT 8% P & P 55p

STEREO FM TUNER WITH PHASE-LOCK LOOP

4 Pre-selected stations supply 20-35V 90mA Max £28·45.
VAT 12½% P & P 70p

CASES

MT58	£10·92
MS56	£12·42

VAT 12½% P & P 85p

CRYSTALS

AT55	£4·43
SOKOTONE	
V100	£4·45
ATAHC	£4·45
ACOS	
GP95-1	£2·15
GP95-1	£2·49
B.S.R.	
SX6M	£2·25
SC10M	£2·95
GOLDRING	
G800	£5·63
G850	£4·05
SHURE	
M75B	£10·92
M55E	£12·42

VAT 12½% P & P 85p

TRANS-FORMERS

SPECIAL OFFER

(Limited Stocks)

BG1 Prim 0-120, 0-160V (110 or 240V) Sec 24V 10A £9·95 P & P £1·66

BG2 Prim 0-90-110-200-220-240V Sec 0-110V 0-20-24V, 0-15A £8·25 P & P 95p. VAT 8%

CARTRIDGES

V100	£4·45
ATAHC	£4·45
ACOS	
GP95-1	£2·15
GP95-1	£2·49
B.S.R.	
SX6M	£2·25
SC10M	£2·95
GOLDRING	
G800	£5·63
G850	£4·05
SHURE	
M75B	£10·92
M55E	£12·42

VAT 12½% P & P 85p

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/7/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

Get a great deal from

Marshall's

A. MARSHALL (LONDON) LTD. DEPT. P.W.
LONDON – 40-42 Cricklewood Broadway, NW2 3ET
Tel. 01-452 0161, Telex 21492

GLASGOW – 85 West Regent Street, G2 2QD
Tel. 041-332 4133

BRISTOL–1 Straits Parade, Fishponds Rd., BS16 2LX
Tel. 0272 654201

CALL IN AND SEE US
9-5.30 Mon-Fri.
9-5.00 Saturday

EXPRESS MAIL ORDER
Tel Orders on Credit Cards £10 minimum.

POPULAR SEMICONDUCTORS

2N706	28p	2N3569	40p	BC178	39p
2N708	28p	2N3569	40p	BC179	33p
2N1131	28p	2N3638	28p	BC182	15p
2N1132	28p	2N3642	28p	BC182L	15p
2N1302	28p	2N3643	28p	BC183	15p
2N2102	60p	2N3645	28p	BC183L	15p
2N2218	28p	2N3702	15p	BC184	15p
2N2219	35p	2N3703	15p	BC184L	15p
2N2220	28p	2N3704	15p	BC212	15p
2N2221	25p	2N3705	15p	BC212L	15p
2N2222	25p	2N3706	15p	BC213	15p
2N2368	25p	2N3707	15p	BC213L	15p
2N2369	25p	2N3708	15p	BC214	15p
2N2369A	28p	2N3709	15p	BC214L	15p
2N2484	28p	2N3710	15p	BC237	15p
2N2646	75p	2N3711	15p	BC238	15p
2N2904	28p	2N3713	75p	BC239	15p
2N2905	28p	2N3715	75p	BC251	25p
2N2906	28p	2N3716	75p	BC252	25p
2N2907	28p	2N3771	75p	BC253	25p
2N3053	28p	2N3772	75p	BC307	15p
2N3054	75p	2N3773	75p	BC308	15p
2N3055	75p	2N3819	75p	BC309	15p
2N3390	28p	2N3820	75p	BC327	15p
2N3391	28p	2N3823	75p	BC328	15p
2N3442	1·35	2N3866	75p	BC337	15p
2N3702	15p	2N3903	28p	BC338	15p
2N3704	15p	2N3904	28p	BC347	15p
2N3705	15p	2N3905	28p	BC348	15p
2N3706	15p	2N3906	28p	BC349	15p
2N3707	15p	2N4058	28p	BC461	75p
2N3708	15p	2N4059	28p	BC477	75p
2N3709	15p	2N4060	28p	BC478	75p
2N3710	15p	2N4061	28p	BC547	15p
2N3711	15p	2N4062	28p	BC548	15p
2N3713	75p	2N4302	75p	BC549	15p
2N3715	75p	2N4303	75p	BC550	15p
2N3716	75p	2N4304	75p	BC556	15p
2N3771	75p	2N4871	75p	BC557	15p
2N3772	75p	2N4872	75p	BC558	15p
2N3773	75p	2N5172	28p	BC559	15p
2N3819	75p	2N5245	75p	BC560	15p
2N3820	75p	2N5246	75p	BC639	25p
2N3823	75p	2N5247	75p	BC640	25p
2N3866	75p	2N5248	75p	BCY70	28p
2N3903	28p	2N5457	75p	BCY71	28p
2N3904	28p	2N5458	75p	BCY72	28p
2N3905	28p	2N5459	75p	BD115	89p
2N3906	28p	2N5460	75p	BD131	89p
2N4058	28p	2N5461	75p	BD132	89p
2N4059	28p	2N5462	75p	BD133	89p
2N4060	28p	2N5463	75p	BD135	39p
2N4061	28p	2N5464	75p	BD136	39p
2N4062	28p	2N5465	75p	BD137	39p
2N4302	75p	2N5466	75p	BD138	39p
2N4303	75p	2N5467	75p	BD139	39p
2N4304	75p	2N5484	75p	BD140	39p
2N4871	75p	2N5485	75p	BD237	39p
2N4872	75p	2N5486	75p	BD238	39p
2N5172	28p	2N5550	75p	BD239	39p
2N5245	75p	2N5551	75p	BD240	39p
2N5246	75p	2N5589	1·70	MJE340	59p
2N5247	75p	2N5590	1·70	MJE370	59p
2N5248	75p	2N5591	1·70	MJE371	59p
2N5457	75p	2N5592	1·70	MJE520	39p
2N5458	75p	2N5769	3·95	MJE521	39p
2N5459	75p			MJE520	65p
2N5460	75p			MJE521	65p
2N5461	75p			MPF102	39p
2N5462	75p			MPF105	39p
2N5463	75p			MPS706	28p
2N5464	75p			MPSA06	25p
2N5465	75p			MPSA13	39p
2N5466	75p			MPSA56	25p
2N5467	75p			TIP29A	65p
2N5484	75p			TIP29C	60p
2N5485	75p			TIP30A	75p
2N5486	75p			TIP30C	65p
2N5550	75p			TIP31A	65p
2N5551	75p			TIP31C	60p
2N5589	1·70			TIP32A	75p
2N5590	1·70			TIP32C	70p
2N5591	1·70			TIP33A	1·50
2N5592	1·70			TIP33C	1·40
2N5769	3·95			TIP34A	1·50
				TIP34C	1·40
				TIP35A	3·95
				TIP35B	3·95
				TIP35C	3·95
				TIP36A	3·95
				TIP36B	3·95
				TIP36C	3·95
				TIP41A	65p
				TIP41B	70p
				TIP41C	75p
				TIP42A	75p
				TIP42B	80p
				TIP42C	85p
				TIP2955	65p
				TIP3055	60p
				TIS43	43p
				TIS90	75p
				TIS91	75p
				TIS98	75p
				TIS98A	75p
				TIS99	75p
				TIS92	33p
				TIS93	33p
				TIP29A	65p
				TIP29B	60p
				TIP29C	55p
				TIP30A	75p
				TIP30B	70p
				TIP30C	65p
				TIP31A	65p
				TIP31B	60p
				TIP31C	55p
				TIP32A	75p
				TIP32B	70p
				TIP32C	65p
				TIP33A	1·50
				TIP33B	1·45
				TIP33C	1·40
				TIP34A	1·50
				TIP34B	1·45
				TIP34C	1·40
				TIP35A	3·95
				TIP35B	3·95
				TIP35C	3·95
				TIP36A	3·95
				TIP36B	3·95
				TIP36C	3·95

Prices correct at 14 July 1977, but please add VAT p&p 40p

OPTOELECTRONICS

Full range of Opto devices in our new catalogue

LEDS

3mm Red 19p. Gr 25p. Y 25p
5mm Red 21p. Gr 28p. Y 39p
TIL209 Rs. OPP12 84p
BPX 25 1·65

DISPLAYS 7 Segments

	Single	Double	Display
DL704	2·00	3·00	0·3in Red
DL707	2·50	3·50	0·3in Red
DL747	2·50	3·50	0·6in Red
DL750	2·50	3·50	0·6in Red

WE ALSO STOCK

- NATIONAL LINEARS IC's
- TEXAS AUDIO & TV IC's
- MULLARD CONSUMER IC's
- VOLTAGE REGULATORS
- TTL, CMOS, SCHOTTKY
- MICRO PROCESSOR DEVICES
- TOOLS&SOLDERING EQUIPMENT

TRIACS Plastic case with HEATSINK

6 amp	70	16 amp	1·10
8 amp	75	20 amp	1·70
12 amp	85	25 amp	2·00

DIACS

ST2 39p
BR100 48p

BRIDGES

Range of Bridge Rectifiers and Diodes listed in new catalogue

THYRISTORS Plastic C106 116

4 amp 100V	0·35	8 amp 100V	0·43
4 amp 200V	0·48	8 amp 200V	0·48
4 amp 400V	0·49	8 amp 400V	0·62

- SWITCHES, PLUGS, SOCKETS & CONNECTORS
- POTS, PRESETS, RESISTORS & CAPACITORS
- CASES, KNOBS, CABLES & METERS
- VALVES, CHOKES, FUSES & CRYSTALS
- TRANSFORMERS & HEAT SINKS

SPECIALIST CONSUMER

NEW CATALOGUE

Stocking Distributors Officially Appointed

- NATIONAL
- VERO
- TEXAS
- ANTEX
- MULLARD
- ELECTROLUBE
- SIEMENS
- SIFAM
- SESCOSEM
- ARROW HART

MAKES COMPONENTS BUYING EASY

Quality components all brand new and fully guaranteed.
Britain's leading distributors of components to the Amateur Market and Consumer Orientated Manufacturers.
FULL RANGE OF COMPONENTS FOR PROJECTS AND SPARES

ORDER NOW!

35p Post Paid or 59p To Callers LARGE 32 PAGES packed with over 8500 LINE ITEMS

S-DeCnology

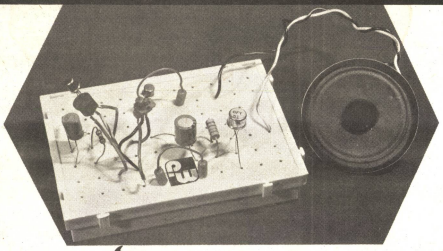

DAVID GIBSON

10

THIS MONTH

'Record Player Amplifier'

This month's project is a simple record player amplifier which is suitable for use with a ceramic cartridge. Although the output could not be fairly described as hi-fi, it does give useful volume which is acceptable in terms of quality.

The prototype used a small 58mm diameter 80Ω loudspeaker but a larger diameter unit would undoubtedly improve the apparent volume and quality, particularly in the base notes. Any speaker with an impedance from 60Ω to 80Ω will be satisfactory.

Circuit description

The circuit, **Fig. 1**, is basically a two-stage amplifier. Transistors Tr1 and Tr2 connected in a Darlington pair configuration form the first stage. This useful arrangement has two main advantages. The first is that a great deal of amplification is possible. The total current gain from such a circuit is found by multiplying the gain of Tr1 by that of Tr2. In practice it is difficult to calculate exactly what the gain will be because individual transistors have quite a spread in their gain characteristics.

Secondly, the Darlington stage also keeps the input currents very small indeed. In terms of power consumption the two Darlington connected transistors drew less than one fortieth of the total current of the whole amplifier.

Resistor R2 forms an audio load for the Darlington pair while base bias and DC stabilisation is provided by negative feedback resistor R1.

The first stage is capacitor coupled to the output stage, Tr3 via capacitor C2. Again, in the interests of simplicity, a lone resistor R3 provides bias and

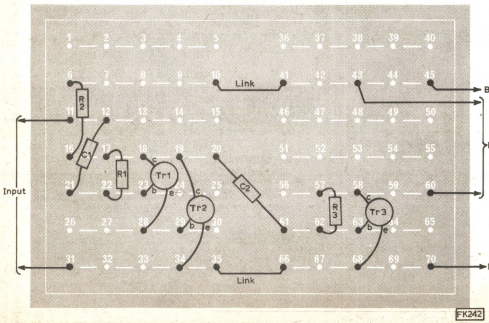

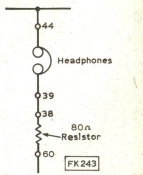

The left-hand drawing is a full-size S-DeC layout showing component locations The smaller drawing (above) shows how a series resistor of about 80Ω must be used when operating the amplifier with low impedance headphones.

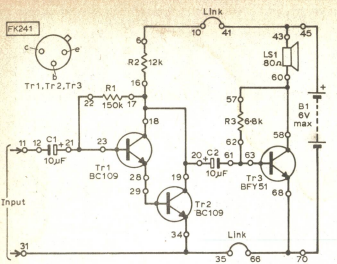

Fig. 1 : Circuit diagram of amplifier.

stabilisation. There are two important points to note. First, do not use very low impedance speakers in this circuit, i.e. 3, 4, 8 or 16Ω units. Secondly, note that both capacitors are electrolytics and must be connected with correct polarity. The positive lead of C1 must go to S-DeC hole 21 and the positive lead from C2 must be pushed into hole 20.

Remember the two shorting links which connect together holes 10/41 and holes 35/66 respectively. It is all too easy to forget these since they are not actual components.

This little amplifier works well from any voltage between 1·5V and 6V although sensitivity and output are lower at the lower voltages. At 1·5V the circuit draws approximately 6·5mA; at 3V it is 16mA, at 4·5V it is 25mA and at 6V, 34mA. With 6V applied, the current taken by Tr1 and Tr2 was found to be well under 1mA.

The lead from the record player pick-up should be of the screened variety. The centre conductor should be connected to hole 11 while the screening wire mesh goes to hole 31.

you will need . . .

R1	150kΩ	R3 6·8kΩ	Tr1 BC109
R2	12kΩ		Tr2 BC109
C1	10μF		Tr3 BFY51
C2	10μF		LS1 60 – 80Ω loudspeaker
One S-DeC			6V Battery

The amplifier provides an excellent and inexpensive general purpose unit and to this end is probably well worth transfering to a piece of Blobboard to form a permanent piece of equipment.

A crystal microphone connected to the input (holes 11 and 31) worked well; the unit would make a very useful intercom amplifier by using another, similar speaker as a microphone and connecting this to the input. The amplifier could also be used as the audio section of a radio receiver—even a crystal set—and headphones may be connected if required. Most types offered for hi-fi and record monitoring purposes are of the low impedance kind and it would be wise to insert an 80Ω resistor in series with the phones if this application is envisaged. ●

next month in Television

● ONE-CHIP TOUCH TUNING

Mechanical station selection using a combined potentiometer/switch assembly is the most common method employed in sets equipped with varicap tuners. Our constructional project next month describes an exceptionally easy method of going "all electronic", based on a Plessey touch-tuning i.c. Connection to the receiver is via the existing leads used for the mechanical selector. The unit is powered from the 33V tuning supply and uses i.e.d.s for channel indication.

● A DAY IN THE LIFE OF . . .

It's that man again. Who else but Les LJ, commenting on an average (?) day's business, faulty sets, dropped Avos, troublesome customers and all.

● IC BURST GATE GENERATOR

A precisely timed burst gate pulse is essential for correct colour reception. This can present problems for the constructor, especially if his test equipment is limited. An effective answer is the use of a simple monostable i.c. to provide the pulse.

● PYE HYBRID COLOUR SETS

The Pye 691/693/697 chassis were produced in large quantities: Andy Denham provides a run down on the stock faults.

● VCR RECEIVER CONVERSION

Older TV sets were not designed to operate with VCRs and can't usually follow the more variable line sync pulses in a VCR's signal. A complete solution is to fit a modern line oscillator i.c. designed for switching between off-air and VCR operation.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:-

TO.....

(Name of Newsagent)

Please reserve/deliver the SEPTEMBER issue of TELEVISION (45p), on sale August 15th, and continue every month until further notice.

NAME.....

ADDRESS.....

.....

.....

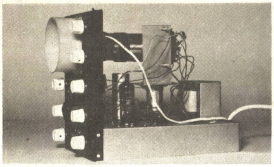

1 Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

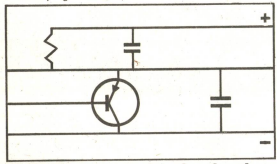

2 Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

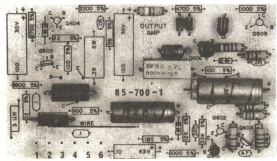

3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

'There's only one way to master electronics... to see what is going on and learn by doing.'

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Write to:- British National Radio & Electronic School
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

_____

_____

WB 9/7

GREENWELD

443 Millbrook Road Southampton
SO1 OHX Tel:(0703) 772501

7lb BARGAIN PARCEL
Hundreds of new components—pots, switches, resistors, capacitors, PC Boards with semiconductors, loads of odds and ends. Amazing value at only £3·45.

COMPUTER PANELS
Large quantity always available; 31b assstd. £1·99; 7lbs £3·99; 36lb £17. Pack with about 500 components inc. at least 30 transistors £1·19; Pack with 12 High quality panels, incl. LED's, power transistors, resistors, capacitors, hundreds of small signal transistors, resistors, zeners, capacitors, etc. Only £2·99.

7400 IC pack—20 74 series IC's on panels £1·25.

PC ETCHING KIT MKIII
Now contains 200 sq. ins. copper clad board, 1lb Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4·25.

FERRIC CHLORIDE
Anhydrous technical quality in 1lb double sealed packs. 1lb £1·10; 3lbs £2·30; 10lbs £5·80; 100lbs £39·00.

FIBREGLASS PCB
Large quantity of offcuts, all usable pieces. 500 sq. ins. single sided, double sided or mixed £1·99.

DEVELOPMENT PACKS
50V ceramic plate capacitors, 5% 10 of each value 68P to 1000pF. Total 250 caps. £1·25.

CR25 carbon film ¼ watt resistors, 5% 10 of each value 10 ohms to 1M. Total 610 resistors £6·50. Electrolytics, wire ended, 25V working 10 each of 1, 2·2, 2, 4·7, 10 22, 47 and 100uF. £2·50.

70 capacitors for £3·50. 400mW zeners 5% 10 each 3V to 30V. 260 in all. Only £15·00.
1 watt Metal Film Resistors, 5% 10 of each value 27R to 10M. E12 series. Total 680 resistors £12·00. Polystyrene capacitors, 160V 5% 10 of each value from 10pF to 10,000pF.

Total 370 capacitors £12·00.

COMPONENT PACKS

400 assstd. carbon resistors	£1·50
100 Wirewounds 2·5W	£1·99
200 Miniature resistors, ½, ¼, and ⅛W	£1·30
200 poly, mica, ceramic caps	£1·29
100 polyester, .01-2·2uF	£1·00
200 PC resistors	75p

TAPE DECKS
Data Tape Deck by D-Mac. Reel-to-reel, takes 3" spool. 2 heads, 12V motor, 3 position switch. 17 transistors, 4 IC's. 200V 6A SCR, min 6V relay, etc. In good condition but not new. Size 225 × 165 × 120mm high. Reduced to clear £4.

TRANSFORMERS
All have mains primaries, secondaries as follows: 6-0-6V 100mA. 95p; 9-0-9V 75mA £1; 12-0-12V 50mA 95p; 12-0-12V 100mA £1·19; 0-3V 1A £1·95; 6-0-6V 1A £2·50; 9-0-9V 1A £2·95; 12-0-12V 1A £2·95; 12V 5A £3·95; 12V 5A £4·95; 20V 50mA 95p; 22V 100mA £1·00; 29V 50mA 39p. Multi-tapped types, 0-10-15-20-24-30V 1A £2·50; 2A £3·00; 20-0-20V 2A £4·40; 24V 500mA £1·95; 20V 2|A £4·15; 30V 1A £3·50.

MULTIMETER MODEL LT 22

AMAZING VALUE !!

Probably one of the lowest priced meters featuring a mirror scale, overload protection and 20000 ohms per volt sensitivity. A modern styled meter with unusually clear scale markings. Ranges: DC Volts 0-0·5-2·5-10-50-250-1000 AC Volts 0-10-50-250-1000 DC Current 0-50uA-2·5mA-250mA. Resistance 0-50k-500k-5M (Mid scale 300-3k-30k) db's 4 ranges 20db to +4db. Size 130 × 90 × 40mm £12·75.

CALCULATOR KEYBOARDS CLEARANCE
Many different types, some as previously advertised at up to £5·00, some off Rapid-man calcs. All types at one price £1·20 each.

THE NEW 1977 GREENWELD CATALOGUE WITH DISCOUNT VOUCHERS IS NOW AVAILABLE— PRICE 30p + 15p post.

ELECTRONIC CAR VOLTAGE REGULATOR

All parts for the project featured in this edition of PW available in kit form for only £4·00.

MOTORS
240V a.c. 60 r.p.m. High Torque: drive to 6mm shaft 20mm long. Size 70mm dia. × 55mm £2·25.

LED DIGIT DRIVER
ITT type 7105. 16PIN DIL package. Supplied with Data sheet. 8 for £1.

VERO OFFCUTS
Pack A, All 0·1"
Pack B, All 0·15"
Pack C, Mixed.
Pack D, All 0·1" plain

Each pack contains 7 or 8 pieces with a to tal area of 100 sq. ins. Each pack is £1·40. Also available by weight; 1lb £3·45, 10lbs £28. (0·1" only).

We are also Vero wholesalers, trade price list on request from Pole Companies.

VEROCASES
Plastic top and bottom, ally panels front and back.

Type 1410 205 × 140 × 40mm	£3·78
1411 205 × 140 × 75mm	£4·17
1412 205 × 140 × 110mm	£5·29
1237 154 × 85 × 40mm	£2·83
1238 154 × 85 × 80mm	£3·05
1239 154 × 85 × 80mm	£3·7

VERO PLASTIC BOXES
Professional quality, two tone grey polystyrene with threaded inserts for mounting PC Boards.

Type 2518-120 × 65 × 40mm	£2·42
2520 150 × 80 × 50mm	£2·68
2522 188 × 110 60mm	£3·72

Sloping front version,
Type 2523 220 × 174 × 100/52mm £6·90
1796 171 × 121 × 75/37 5mm £4·65

Gen Purpose plastic potting box 71 × 49 × 26mm in black or white 49p Hand Controller box, shaped for ease of use in the hand, 94 × 61 × 33mm 84p.

SOLDERING GUN
Instant heat soldering gun, mains voltage, built in illumination, 5 spare tips. ONLY £4·99.

5-DEC £2·39; T-DEC £3·85. Insulation tape, 19mm wide × 5m long, 7 diff coloured reels £1; Switch banks, 4 PO 1000 type lever switches in vertical bank. 3 for £2. Miniature carbon film 5% resistors, all values from 1R to 10M 10p each. Add of one value £1.

5V 12A REGULATED POWER SUPPLY
Brand new boxed fully stabilized PSU. Complete with instruction manual. Load regulation 0·15% Thermal & Electronic overload protection. Only £24.

Our retail shops at 21 Deptford Broadway, London, SE8 (01-692 2099) and 38 Lower Addiscombe Road, Croydon (01-688 2950) stock some of the advertised goods for personal callers only. Ring them for details. All prices quoted include VAT and UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries please. MINIMUM ORDER VALUE £1. Official Orders accepted from Schools, etc. (Minimum value £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

Your carpet is no place for the Black Dyke Mills Band

. . . they should be half way up the wall!
Fidelity Fastenings are the newest, smartest way to place your speakers where they belong – on the wall. Almost undetectable when fitted they are easily adjustable and allow your speaker system to be placed in the best possible acoustical position, where they stay due to the rubber friction mounting. Fidelity Fastenings take a weight of up to 50 lbs and your speakers are easily lifted off for dusting and redecorating.
Available from all good Audio and Hi-Fi shops and stores at £5.49. Look for the red and black box.
If you have any difficulties in obtaining your Fidelity Fastenings, write for details of your nearest stockists to:

fidelity fastenings

The Ridgeway, Iver, Buckinghamshire,
Tel: (0753) 654222.

COMPLETE **digital clock kits** REAL TEAK CASE

"DELTA"
TEAK OR PERSPEX CASE 6" x 2½" x 3"

NON ALARM £10·65 VAT + 85p
ALARM £13·43 +£1·07 VAT INCLUDING P & P

FEATURES: 4 Red ½ inch high LEDS, 12 hour display with AM/PM indication Power failure indicated by flashing display. Precise accuracy from mains frequency. Beautiful Burma Teak case or stylish Perspex (State first & second colour choice: White, Red, Blue, Green, Black).

NON ALARM: Complete kit including Teak Case £11·50 Incl. Module Kit excluding case £9·00 Incl.

ALARM EXTRAS: Pulsed alarm tone. Tilt operated "Snooze" period. Automatic brightness control. Simple setting.

ALARM: Complete kit including Teak case £14·50 Incl. Module Kit excluding case £12·50 Incl.

PERSPEX CASES: 50p LESS than Teak.

READY BUILT: Extra £2·00 on complete clocks. Extra 50p on Modules.

TIMER FACILITY: Count in seconds up to 9m 59sec. Extra 50p.

"ALPHA" £11·00 incl.
Ready Built. Non Alarm. Perspex. 4 digits phosphorescent-green, 1" high 12 or 24 hour display. White, black, blue, red, green.

Discount on orders over 5 clocks or kits. Overseas: Add £2·50 for Airmail.

Send payment with order. SAE for details.

BARON

(PW 1) 6 GOWER RD, SOUTHVIEW HOUSE, ROYSTON, HERTFORDSHIRE
Phone Royston (0763) 43695

PRODUCTION LINES

bill tull

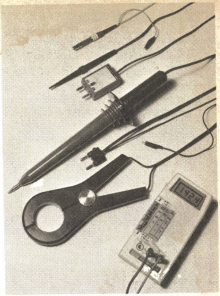

A free hand from Fluke

Possibly a little on the expensive side for a lot of our readers, but if you are in the market for a new multimeter, don't rush out and buy the first you see, think about the new Fluke model 8020A digital multimeter.

Incorporating a ½in 3½ digit LCD, the various functions and range push-button selectors are so arranged as to allow one-handed operation. The latest CMOS/LSI circuitry is used throughout, and this together with an LCD, ensures that the small 9V alkaline cell lasts for up to 200 hours.

Apart from the usual features of a multimeter such as ten voltage ranges, six resistance ranges, and current measurement up to 2A, the 8020A incorporates three diode test functions and two conductance ranges. In the case of the former of these two functions, the meter applies sufficient voltage to turn on a semiconductor junction, so that diodes and transistors can be tested for the correct forward bias voltage in situ. Individual paralleled resistors can also be checked without the need to disconnect them from the circuit.

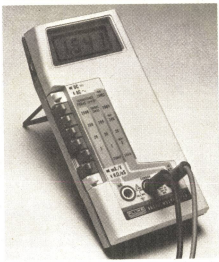

The two conductance ranges enable measurement of resistance as high as 10,000M ohms, thus making possible the checking of HV dividers, leakage in capacitors, PCB's and cables.

Overload protection is also part of this new meter, with full protection against 300V DC continuous, or 6kV transients on any range. Priced at £99 and guaranteed for 2 years the 8020A is complete with test leads and instruction manual, although the versatility of this meter could be extended by purchasing a high voltage probe, RF probes, temperature probe and external battery eliminator.

ITT Instrument Services, Edinburgh Way, Harlow, Essex. Tel: 0279 29522.

IC test clip

Walmore Electronics have introduced a unique DIP test clip which is designed to provide positive contact to eliminate the possibility of accidental disconnection from a device. Called the DIP/LOC it has contacts which provide a wiping action with the DIP leads and end-contacts hook under the DIP's end-leads in a lock-on action.

14 and 16 pin versions are available, while cable connections can be made quickly and easily with barrier strips between contacts to prevent lead shorting.

Walmore Electronics Ltd., 11-15 Betterton Street, Drury Lane, London.

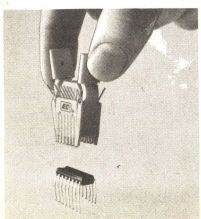

Cassette centre

Not everyone wants a mini-recording studio in their sitting room as would appear from the complexity and price of many of the commercially available cassette decks. Plustronics, who have recently acquired the Aiko brand, are now marketing the Aiko ATP-711 stereo cassette recorder which is complete with twin speakers and microphones, and would suit the person who requires a good quality recording system, and yet is not too expensive.

Power output into the 8 ohm speakers is claimed to be 5W per channel while frequency response is 50 to 12,000Hz. Controls are of the slider type, with recording level monitored by twin VU meters. Priced at around £117 the Aiko ATP-711 can be obtained from the usual Plustronics stockists.

Plustronics Ltd., Hempstalls Lane, Newcastle, Staffs. Tel: 0782 615131.

Flyweight iron

Components seem to be getting smaller and smaller these days, and this coupled with the fact that many of todays IC's are extremely heat and voltage conscious makes the job of soldering a hazardous affair. Now, thought to be the smallest iron in the world, comes the Oryx model 9 low voltage iron that weighs in at only 6 grammes.

Manufactured by Greenwood Electronics, the element is claimed to give an improved and longer working life, and is available in either 6V, 12V or 24V models. The maximum tip temperature reaches 325°C while power consumption is about 8·3W. The complete iron is only 160mm long and costs £3·02 from the manufacturers or from the usual retail stockists.

Greenwood Electronics, Portmann Road, Reading, Berkshire, RG3 1NE. Tel: Reading 595844.

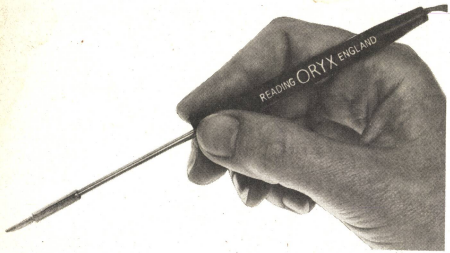

Tidy tubs

Take a look in one of your drawers in the kitchen, the chances are that if not all of them, at least one of them will be full to overflowing with bits and pieces, pens, pencils, clips and other things which may "come in handy" at some future date. Any attempt to tidy up results in the mess being transfered to another draw, but it's just possible that a new device produced by Platignum (the pen people) will solve this age old problem. Called Tidy-Tubs, it comprises six plastic tubs of varying dimensions joined together to form a "hold-all" for all those small bits that lie in the bottom of draws.

Tidy-Tubs come in six colours, cost £1·50 each, and should be available from all good department stores and stationers.

Multi-pin resistor

A new style of resistor recently to enter the UK market, has been launched by National Semiconductors. The resistors comprise 0·1in pitch SIP resistor networks available in 6, 8, and 10pin epoxy coated packages, with two styles being offered for each size package. In styles 605, 807 and 109, pin 1 is common to all resistors in the package, whereas in styles 603, 804 and 105 each individual resistor is brought out to a separate pin.

Line terminating resistor networks are available in 8 and 10pin styles with resistor values R1/R2 being 180/390 ohms or 220/330ohms respectively. All styles are rated at 0·125W, and have a tolerance of ±2%.

Any further information from National Semiconductors Ltd., Stamford House, Stamford New Road, Altringham, Cheshire. Tel: 061-928 3417.

A good case

Recently introduced by Boss Industrial Mouldings is a new range of aluminium containers, notated the BIM7000 range with a choice of either 15° or 30° sloping front panels. They comprise two sections each and are supplied in blue/off white, green/sand and gold/satin black colour combinations for base and sloping panels respectively.

16 sizes are available, all of which have ventilation slots in both the base and rear vertical panels.

Boss Industrial Mouldings Ltd., Higgs Industrial Estate, 2 Herne Hill Road, London, SE24. Tel: 01-737 2383.

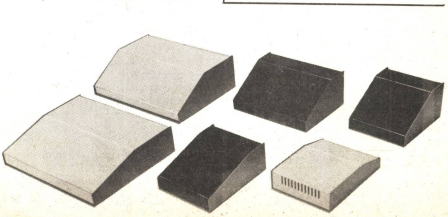

ON SALE SEPT. 2ND.

NEXT MONTH IN...

practical WIRELESS

A FREE POCKET MAGNIFIER

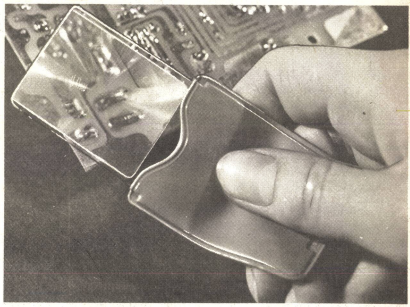

Now! You can avoid disappointing results with that new project by checking for dry joints and solder bridges on your printed circuit boards with our FREE Pocket Magnifier. Inspect your handiwork in detail. There's a dozen other uses for this handy gadget.

ALSO

SOLO SUPERMIND

Losing a few friends through boredom seems to be a hazard of some current "logical" games. October PW features SOLO SUPERMIND, which not only makes the "codemaker" redundant, but permits you to set and break your own codes. Simple circuitry, using readily available transistors disposes of the need for expensive "chips". It's effective, engaging, and cheap to build.

and:

Audio Level Indicator

Inexpensive Sine~Square Wave Generator

The Jubilee is an electronic chord organ with automatic vamping coupled to a three instrument rhythm section. It incorporates a number of features normally found only on the more expensive commercial instruments such as variable sustain length, percussion and other effects. Although automatic organs of this type have been available on the commercial market for a few years they have previously been put out of court for the home constructor because of their inherent complexity and high cost. Nevertheless we have overcome some of the problems with a novel design; simplicity of construction has been obtained by using three specially designed organ integrated circuits—developed for the professional manufacturer by General Instrument Microelectronics. These revolutionary integrated circuits are now available to the amateur.

Vamp playing

The author, like many readers, is fascinated by electronic organs and the sounds that they produce but, unfortunately, is not sufficiently dextrous to get the best out of a conventional instrument. For this reason every effort has been made to design an instrument that will produce a wide variety of sounds and which can be played by the absolute novice. In practice the melody of a tune is picked out by one finger of the right hand and a four or five note chord (Major, Minor, Major 7th or Minor 7th in any key) is selected by one or two fingers of the left hand (the latter depends on the constructional method adopted as will be seen from reading on). The left hand chords can be played in a static form or can be vamped with an alternating bass note by selecting a suitable rhythm on the tab switches.

A vast range of music is available that enables the person with no previous experience to learn to play in a few minutes. Perhaps the best examples are those written with the Lowrey and Farfissa automatic organs in mind; these scores are sometimes referred to as 'Minute Music' or 'Speed Music'. Apart from these specially written music sheets it is easy to play any music that contains guitar chord notation. The Jubilee will capture the interest of any child and, although it is no substitute for proper music lessons, it provides an incentive to learn to play a more conventional instrument in due course. For those of us with somewhat longer teeth it is a superb fun instrument providing hours of relaxation which can be appreciated by other members of the household!

Keyboards

Again, like many readers, the author dislikes messy constructional projects which involve lots of discrete point-to-point wiring. This is usually typical of organs and, apart from leaving plenty of scope for error, it turns an interesting project into a bit of a chore. For this reason we have tried to keep construction to the assembly of components on a single printed circuit board and this includes the novel keyboard arrangement suggested for the *Mark I* version. In this example we have used calculator keys instead of a normal keyboard which would need a wiring loom. Calculator keys can be used quite satisfactorily because generally speaking only one has to be depressed at a time and slick fingering is not necessary because of the built-in sustain facility.

PW presents THE 'jubil

M.J. HUGHES, MA, C.Eng.

★ specifications

Three octaves for melody line with three principal tone colours plus any combination of these.
Variable length sustain.
Variable depth Vibrato.
Percussion effect.
Repeat percussion effect (for banjo and mandolin sounds—by judicious use of length sustain can also simulate xylophone, glockenspiel etc.).
Variable repeat rate.
Two octaves of accompaniment.
Automatic chording giving all major, minor, and seventh chords.
Two principal tone colours plus their combination.
Percussion effect gives piano, guitar or banjo accompaniment.
Automatic vamping with alternating and walking bass.
Rhythm section comprising bass drum, snare drum, and cymbals.
Six selectable rhythms—synchronised with vamping accompaniment.
Rhythms may be mixed.
Variable rhythm speed.
Independent volume controls for melody, accompaniment and drums.
Internal 1W amplifier drives loudspeaker direct or phono output.
Single board construction—no wiring loom needed for keyboard.

ELECTRONIC ORGAN

Part 1

IERE

★ collated components list

Resistors

1 off 5·6Ω ¼W	34 off 10kΩ
3 off 220Ω	1 off 12kΩ
1 off 330Ω	11 off 22kΩ
1 off 470Ω	1 off 33kΩ
3 off 680Ω	1 off 68kΩ
2 off 1kΩ	10 off 100kΩ
2 off 1·2kΩ	2 off 470kΩ
1 off 2·2kΩ	3 off 1MΩ
4 off 3·3kΩ	2 off 3·3MΩ
11 off 4·7kΩ	

All 10% ¼W except where stated

Capacitors

5 off 1nF Polystyrene	1 off 1μF
3 off 33nF Polysytrene	2 off 2·2μF 15V Electrolytic
2 off 10nF	1 off 10μF 25v Electrolytic
1 off 15nF	1 off 47μF 25V Electrolytic
3 off 22nF	1 off 100μF 25V Electrolytic
1 off 33nF	1 off 1000μF 25V Electrolytic
10 off 100nF	1 off 2200μF 25V Electrolytic
5 off 220nF	2 off 4700μF 25V Electrolytic
10 off 470nF	

All polyester 10% (voltage greater than 25V) except where stated

Transistors

1 off BFY71
8 off BC148

Diodes

6 off 1N914 (or 1N4148)
1 off 3V 400mW zener
2 off DIL 1 Amp bridge type VM18 (Marshalls)

Preset potentiometers

1 off 5kΩ
3 off 10kΩ
3 off 100kΩ
5 off 500kΩ

All sub miniature horizontal

Spindle potentiometers

2 off 5Ω lin
3 off 10 kΩ log*
1 off 100 kΩ lin
1 off 1 MΩ lin

* One of these should have ganged mains switch for conventional keyboard version.

Integrated circuits

7 off 741	1 off AY-1-0212 (Top octave generator
1 off NE555	4 off AY-1-5050 (7 stage divider)
1 off 4011	3 off AY-1-1313 (Priority latches)
1 off LM380	1 off AY-5-1317A (Chord generator)
1 off 7812	1 off AY-5-1315 (Rhythm generator)
1 off LM320-12	Specify 'Pattern 004—Jubilee' for the latter

NOTE: All devices prefixed 'AY' are by General Instruments. These devices are available from Technomatic Ltd., Watford Electronics and other advertisers in the magazine.

Miscellaneous

1 off mains transformer (Double 12V 1A secondary)—Douglas type MT71-AT
*13 off single pole one way sub-min toggle switches
*1 off double pole change over sub-min toggle switch
*51 off AB Metals low profile calculator buttons (0·6" square)—available from WKF Electronics, Whitwell, Near Worksop, Notts.
1 off 1A mains fuse and panel mounting holder
*1 off mains slide switch
1 off indicator lamp and holder (optional)
1 off printed circuit board (Reader's PCB Service)
DIL sockets or Soldercons for IC mounting
Board pins (quantity depends on version being built)
Standard jack socket ¼" (for loudspeaker output)
5-pin 180° DIN socket (for phono output)

* If the conventional keyboard version is built the 14 toggle switches can be replaced by organ rocker tabs and the calculator keys by a four octave keyboard with single pole make contacts having common busbars. The mains slide switch is replaced by a ganged switch on melody volume potentiometer. Extra components required for the conventional version are:
stereo jack socket ¼" (for link to foot controlled Minor and Seventh switches)
Pair of foot operated push-to-make switches

Maplin Electronic Supplies are able to supply suitable foot switches. They also have limited stocks of 4 octave keyboards having the lowest octave in reversed colours (white accidentals). They can supply gold wire for making single pole contacts or, alternatively, low cost contact blocks can be obtained from Harmonics (Bromley) Ltd., Oakley Grange, Plaistow Road, Kirdford, Billingshurst, West Sussex. The latter require palladium busbars which Harmonics can also supply.

Some people might feel that they would prefer a conventional keyboard—certainly the sound of the instrument warrants the extra cost and trouble involved—and if so they can use the same printed circuit board with no changes except for the omission of the calculator keys. Flying leads are taken from each key position to the respective single-pole single-way contacts under each note of the keyboard.

In this part we shall describe the overall workings of the instrument and pay special attention to the large scale integrated circuits used. Constructional details will start next month and in order to allow time for ordering and delivery we are publishing a collated components list immediately. This might enable constructors to obtain components on favourable terms if they are purchased as a package deal.

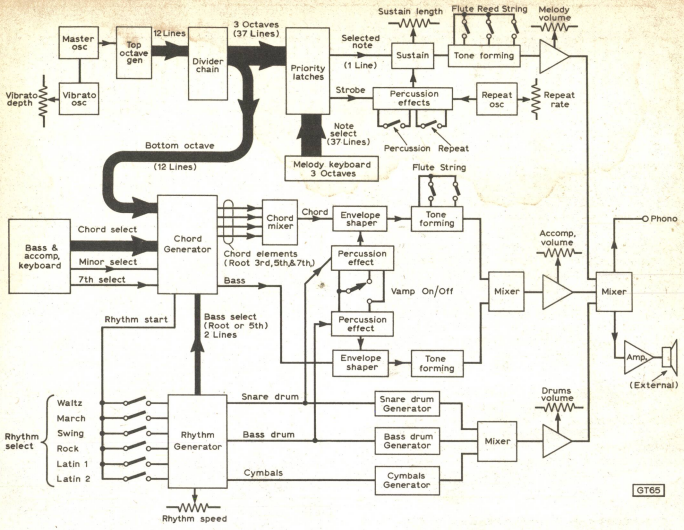

Fig. 1: Block diagram of the complete organ.

System organisation

Constructors who are more inclined to build a conventional organ, or who have already built our previously published *Easibuild Organ*, might find this single board useful in providing an additional keyboard for solo or special effects. In this application some economy can be effected because the tone generator circuitry would already exist.

A block diagram of the complete organ is shown in **Fig. 1.** A master oscillator, frequency modulated at variable depth to give vibrato, drives a conventional top octave generator. Each output of this is fed to a two stage divider except for 'C' which is followed by three stages of division to provide a total of three complete octaves plus 'Bottom C'. These notes are used to drive the priority latches for the melody keyboard and the bottom of the three octaves is fed to the chord generator.

The priority latches are contained in three integrated circuits and in simple terms they are flip-flops which control a gate for each note. Each key of the melody board has its own flip flop/gate arrangement with the associated note fed from the tone generator to that gate. When the key is pressed the flip-flop opens the gate and allows the note to appear at the single line output. At the same time any other flip-flop is reset. This means that only one note at a time can be selected by the melody keyboard—it is monophonic. This, at first, sounds as though the scope of the organ is immediately limited. On the contrary. If the key just selected is released the flip-flop remains in its set state and the note remains active at the output and enables the envelope generator (built into the sustain circuitry) to hold the note over an adjustable period. This allows one note to die away slowly until a second key is pressed.

In order to synchronise the Sustain circuitry with the note selection operation we have to tell it whenever a new key has been depressed. This is easily done by making use of the internally generated 'Priority Output' signal for the priority latches. This signal in conjunction with the 'Inhibit Output' line is used within the priority latches to carry out the reset operation already referred to.

The three priority latch integrated circuits are coupled together in such a way that if two keys are pressed at the same time only the higher note will be selected. A pin connection diagram for this integrated circuit and an illustration to show how the three are coupled together in this application are shown in **Fig. 2.**

Sustain

The synchronising signal from the priority latches is called a 'Strobe'. This is fed to the percussion effects stage which changes the nature of the signal. Normally the signal is high for as long as a key is pressed—thus allowing a continuous tone through the

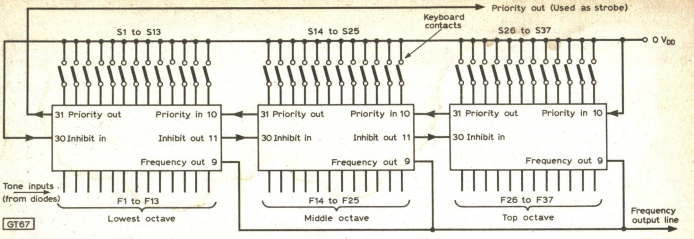

sustain circuit. The percussion effect, when switched in, allows only a short pulse from the strobe line and this occurs on the instant of pressing the key. The effect of this is that the note is generated for a very short period (even though the key is held pressed) and dies away according to the setting of the sustain length. Depending on the setting of the tone forming circuit the sound so produced could be like a drum stick hitting a wooden block if there is zero sustain length or like a bell being struck if there is a long sustain.

Another feature of the percussion circuit is the ability to repeat the pulse, just referred to, at an adjustable rate for as long as the key is depressed. By careful setting of the various controls one can produce sounds ranging from a xylophone to a banjo being strummed. With the repeat rate set close to the vibrato frequency very weird sounds can be produced!

Voicing

The shaped signals from the sustain stage are then fed to the tone forming circuits. We used the absolute minimum of circuitry here to keep construction simple but have managed to provide three basic tone colours. In electronic terms these are a heavily filtered square wave which gets close to sinusoidal, a straight square wave, and a spike waveform. These closely resemble the tone colours usually referred to as Flute, Reed and String respectively. The apparently small choice of tone colours is deceiving. By modifying their envelopes, they provide a wide range of sounds

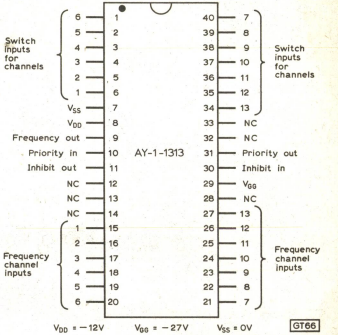

Fig. 2 (above and top) : Pinout and simplified interconnection diagram, for the three priority latch IC's AY-1-1313. Among other functions, these circuits ensure that, if two notes are pressed at the same time, only the higher one will sound.

The picture (below) shows a prototype organ and has been included solely to give readers some idea of the work entailed in construction. The IC's referred to above are hidden from view under the front panel hood.

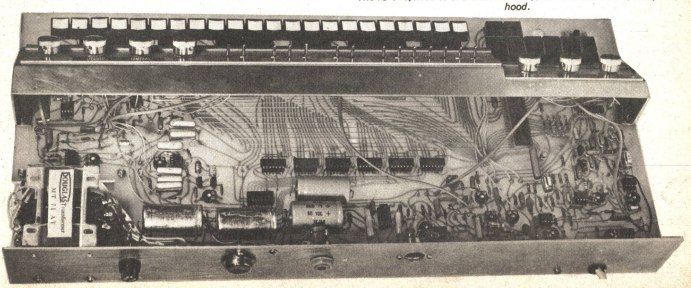

ranging from ecclesiastical to modern plus the instrumental effects, some of which have already been mentioned. The signal is then fed to a pre-amplifier where its volume is independently controlled prior to joining with other signals at the power amplifier.

Chord and rhythm generator

The more complex part of the instrument is the accompaniment section which is built around General Instrument's chord and rhythm generator ICs.

As the chord generator concept is relatively new to the amateur it is worth spending a few paragraphs describing how this chip works. Its pinning diagram is shown in **Fig. 3.** The generator can be used in two configurations. One requires 36 separate keys to select the major minor and seventh chords for a complete octave. The alternative configuration requires 12 contacts to select one of the major chords and utilises two extra switches to convert the selected chord to minor and seventh respectively. The latter configuration is used to economise on keyboard facilities. This means that not all the input pins of the package are utilised. The schematic stage shown in **Fig. 4** might be of more help in describing how the device functions in our configuration.

The twelve notes of the bottom octave from the tone generators are connected directly to input pins 13 to 24 and a capacitor and resistor are needed to set the frequency of the internal keyboard multiplexing oscillator. If the key designated 'C' is pressed the generator switches the respective notes of the bottom octave that go to make up the chord of 'C Major' on to the chord element output lines. 'C' would appear at pin 31 being the root note, 'E' at pin 29 as the third and 'G' at pin 28 as the fifth. These three elements

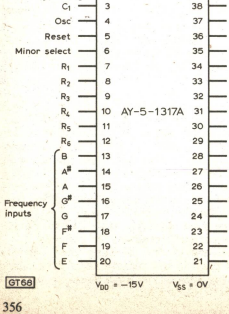

Fig. 3 (below): Pinout details of the AY-5-1317A chord generator.

Fig. 4 (right): Simplified interconnection diagram of the chord generator. This chip operates in conjunction with the AY-5-1315 rhythm generator IC to produce both chords and walking bass effects.

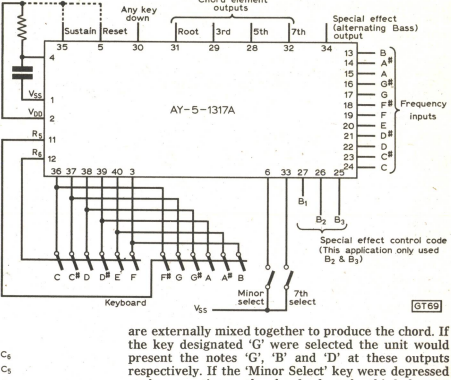

Although we intend to publish reduced scale artwork for the PCB in the next issue, full size etching artwork will be available from the editorial address at the front of the magazine, price 40p. Send a cheque/postal order for 40p together with a large (at least 13" × 11") stamped and self-addressed envelope. Ready-made boards will be available from the Readers PCB service as usual, see ad.

are externally mixed together to produce the chord. If the key designated 'G' were selected the unit would present the notes 'G', 'B' and 'D' at these outputs respectively. If the 'Minor Select' key were depressed at the same time as the chord select, the third element at pin 29 would be changed to a note a semitone lower. If '7th Select' were depressed an extra note would be presented at pin 32. This would be the note a full tone below the root of the chord in question (in both major and minor keys). When this extra note appears it is mixed with the three others producing a very pleasing chord that is frequently used in music notation.

The output designated 'Any Key' is very important. It is made active whenever a key is pressed. It is therefore used to start the rhythm generator in synchronism with a key depression. In the main block diagram this link is anotated 'Rhythm Start'.

Pin 34 is called the 'Special Effects Multiplex Output'. Its effect is not quite so difficult to understand as its name implies. For a given chord selection we can obtain either the root, third, fourth, fifth, sixth or seventh element at this output but naturally only one of these six options at a time. The option is set by the binary code being fed to the control inputs at pins 25, 26 and 27 according to Table 1. If the codes

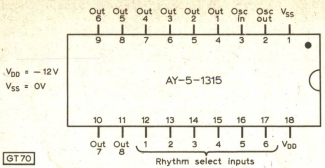

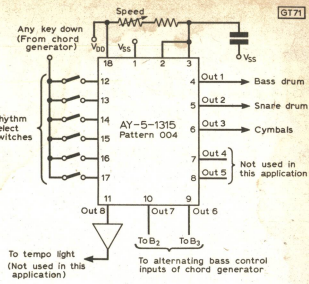

Fig. 5 (above and right) : The pinout and simplified connection diagram of the AY-5-1315 rhythm generator. Readers should specify 'pattern 004' when purchasing this IC.

were generated sequentially, it would create an output sequence of the elements comprising the chords. The chord generator chip divides these elements by 1, 2 or 4 so that they fall at least one octave lower than the chord outputs, thus producing a bass note. If the selection were sequenced while a chord was being held it would have the essentials of a walking bass.

Table 1

Pin 27 (B1)	Pin 26 (B2)	Pin 25 (B3)	Note Selected
0	0	0	No change from last note
0	0	1	Root
0	1	0	Fifth
0	1	1	Third
1	1	1	Seventh
1	1	0	Fourth
1	0	1	Sixth

In our application we do not make full use of all the special effect options—we only use two of the control inputs (pins 25 and 26). These are coupled to the rhythm generator which is pre-programmed to change the code in synchronism with the rhythm patterns. This gives an alternating bass which is sounded at the same moment as the bass drum beat.

Vamp

It should now become easier to understand the details shown in the main block diagram for the accompaniment section. If we assumes that the vamp switch is off, the percussion effect circuits can, for the moment, be ignored. When an accompaniment key is pressed the selected chord elements are presented to the mixer, pass straight through the envelope shaper and on to the tone forming circuits producing two voices 'Flute' and 'String' (Sine and spike respectively). With none of the rhythm select switches closed and the rhythm generator chip outputting the correct code on the bass select lines, there will be a continuous note on the bass output line. This will be the root note of the chord in question.

The bass line from the chord generator is fed to its own envelope shaper and thence to a single tone colour filter. This provides a filtered square wave which sounds reasonably mellow and full. Both the chord and the bass line are mixed before being fed to a volume control and pre-amplifier.

When the Vamp switch is on, the bass note and chord are produced in exactly the same way but do not get through their respective envelope shapers until these receive trigger pulses from the snare drum and bass drum outputs of the rhythm generator. These pulses are short and give a fast attack to the accompaniment which is followed by a decay set by the sustain circuit within the envelope shapers.

Component values are pre-determined to make the bass note sound like the string of a bass guitar being plucked. Depending on whether flute, string or both are selected, the chords will sound as if played on a piano, banjo or guitar. The bass guitar sounds on the bass drum beat while the chord is struck in synchronism with the snare drum.

When switched to Vamp mode, the accompaniment signals will only appear at the output if the rhythm generator is running; ie if one of the rhythm select switches is on.

Rhythm

The GI rhythm generator used in this project **(Fig 5)** is mask programmable so that manufacturers can design their own rhythm patterns. It is not economic to do this for small quantity purchasers so we have settled on one of the standard patterns already being produced by GI. This gives a reasonable selection of six beats, as shown on the figure, but a feature of this circuit is that the rhythms can be mixed by selecting two or more at the same time. Although the chip produces five instrument outputs (plus the alternating bass control signals) we are only using those for bass drum, snare drum and cymbals. These pulses are fed to noise generator circuits which are coupled in a mixer before being fed to their own pre-amplifier. This, again, has its own volume control.

By having separate volume controls on the melody, accompaniment and drum lines the overall balance may be adjusted to individual preference. It also means that the drums can be reduced to zero level while maintaining operation of the rhythm unit which keeps the vamp going. One can operate the accompaniment and drums section in various modes depending on the set of the instrument tabs. For example one can have straight chords with a static root base note; one can have static chords with an alternating bass and drums or a complete vamp—alternating bass syncopated with the chords and drums.

Next month we shall start on constructional details and describe the various circuits as we go along.

If you take delivery of the GI Integrated Circuits before the next part do not remove them from their protective packing unless you take steps to prevent damage from static electricity!

DESIGN YOUR OWN PROJECTS

No.1 LIGHT TRIGGER

TOBY BAILEY & BOB WHITAKER

This series describes how to design experimental projects for yourself. Each month we hope to set ourselves a reasonably simple problem, produce a set of specifications to which we want our circuit to conform, and design an appropriate circuit. We will give an account of the possibilities we explored and the thought processes we used to arrive at the final circuit, together with details of how we calculated (or guessed!) component values and why we chose particular component types. Last, but not least, we will provide an honest report of what happened when we built our circuit.

One point requires particular emphasis. These are meant to be one-off projects and the methods used to design the circuits will, in some cases, be more casual in approach than they might be if the circuit were, for instance, being designed for mass-production or in the form of a kit or completed unit. This is not because we want to be condescending or that we think that you might need protecting from some of the complexities. It is simply because this is the method of design used by almost all amateurs of some experience when they are experimenting.

Problem

For the first circuit we decided to tackle the well-worn problem of producing a device which will turn on a light when the evening becomes dark enough. This old favourite often appears under names such as "electronic candle" or "automatic nightlight" or some similar title. With a bit of luck we will try to show that designing one of these devices for your own specific requirements is not as daunting a task as it might appear at first. Of course designing your own circuit from scratch is not as easy as ferreting out a published design in the back issue of a magazine, but that is not the point.

Specification

So, what exactly are we trying to do? Let's not be overly ambitious, and stick to driving an ordinary torch bulb. The first one we unearthed from the bottom of a drawer has the markings "6V-60mA" still barely decipherable on the side. This seems a pretty reasonable one to use as it doesn't require a terribly unusual power supply anyway. We also need something to sense the light intensity so a light-dependent resistor (LDR) should be just the job. Bob happened to have one of dubious origin attached to a piece of equipment of even more dubious function, from which it was duly severed.

It seemed that the most sensible way of finding out the charactertistics of this LDR was to measure its resistance with a meter. A couple of minutes later we possessed the facts that when it was so dark that we could hardly read the meter the resistance was at least 100kΩ and with rather dingy lighting the value decreased to about 10kΩ. We decided fairly arbitrarily that the circuit should switch somewhere between these points and that we didn't particularly mind where.

Design

It would seem pretty perverse to use anything but 6V for the power supply and, short of using a relay which would be absurdly expensive for our modest

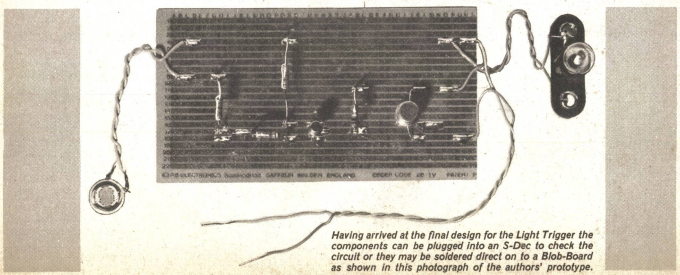

Having arrived at the final design for the Light Trigger the components can be plugged into an S-Dec to check the circuit or they may be soldered direct on to a Blob-Board as shown in this photograph of the authors' prototype.

★ components

R1	2·2kΩ	¼ or ½W 5%
R2	2·2kΩ	
R3	220Ω	
R_F	100kΩ	
LDR	ORP12	Bulb 6V 60mA and holder
Tr1	BC109	Blobboard ZB-1V
Tr2	BFY51	(PB Electronics Ltd.)

requirements, we are going to end up by driving the bulb directly from a transistor. So, let's start from that end and see how we get on. The next question that needs to be answered is "does the bulb go in the emitter or the collector?" If we put it in the emitter circuit we shall have to drive the base between about 0·5V and 6V to turn the transistor off and on, whereas if the bulb is in the collector circuit then a much smaller voltage swing is required to get the same effect. As the textbooks more formally put it: "Emitter-follower and common-emitter amplifiers have about the same current gain but the latter has a much higher voltage gain than the former."

So let us accept the extra voltage gain as a bonus, it's free and there does not appear to be any obvious disadvantages associated with our choice of the common-emitter circuit. We now have a circuit like that of **Fig.1.**

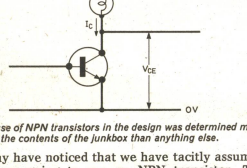

Fig. 1 : The use of NPN transistors in the design was determined more by the contents of the junkbox than anything else.

You may have noticed that we have tacitly assumed that we are going to use an NPN transistor. The reasons for this are by no means deep and not entirely unconnected. Firstly, we both have rather more of the NPN type than PNP and, secondly, they tend to be marginally cheaper. Now we need to decide which particular transistor to use, especially since a collector current of 60mA is not small enough to ensure that any transistor we try won't blow up. The highest power dissipation in the transistor is when the collector is at half the supply voltage, i.e. V_{CE} = 3V. This enables us to calculate the dissipation, given by V_{CE} x Ic, and we get P = 3 x 60 = 180mW. Now the allowable dissipation for most common small transistors (e.g. BC109, 2N3704 etc.) is around 300mW so we seem to be fairly safe here.

But wait a minute! When a light bulb is just turned on the resistance of the filament is much lower than it is after the filament has had a chance to heat up. This means that the current and hence the dissipation will be rather larger at turn-on. We measured the cold resistance and found that this meant that the peak collector current would be about 150mA, giving a dissipation of 450mW for a short time. To be on the safe side let us use a BFY51 which can take up to 800mW. Our catalogue tells us that the minimum gain is 40 but neglects to specify the current to which this figure refers. Oh! well, let's say 30 then. This means that we need 2mA at the base of our BFY51 to turn on the light. The stage we have now reached is summarized in **Fig.2.**

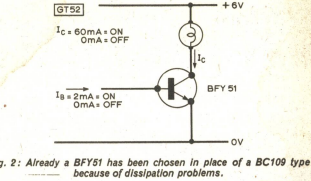

Fig. 2: Already a BFY51 has been chosen in place of a BC109 type because of dissipation problems.

At this point it now becomes abundantly clear that we are going to need another transistor. Since the minimum resistance of the LDR at which the bulb must be turned on is 10kΩ we would need 20V to pass 2mA through the LDR. So how do we connect the second transistor? It can be either NPN or PNP and can be driven from either the emitter or the collector, giving the four possible circuits shown in **Fig.3.**

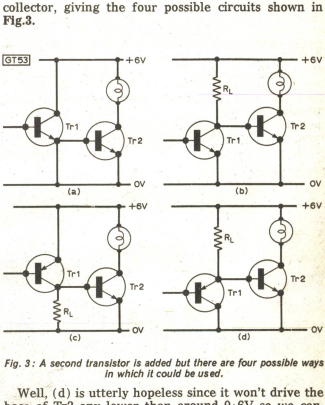

Fig. 3 : A second transistor is added but there are four possible ways in which it could be used.

Well, (d) is utterly hopeless since it won't drive the base of Tr2 any lower than around 0·6V so we cannot even guarantee to turn it off. In (c) Tr2 is not going to last very long if Tr1 turns on heavily since Tr1 will then supply a large base current to Tr2. We now have to choose between (a) and (b) both of which use a NPN Tr1. (a) suffers a similar defect to (c) in that we are going to have to be very careful that we do not supply too much base current to Tr1 in order to protect Tr2. Also it is conceivable that when Tr1 is turned off the leakage current might be high enough to upset Tr2, especially if the latter has rather more gain than our conservative estimate.

Circuit (b) seems to be best and we shall now proceed, using this one.

Practical Values

The next thing to work out is the value of RL. When Tr1 is turned off there will be about 5·5V across RL which then has to supply 2mA to the base of Tr2 (we are ignoring the leakage of Tr1 which should be negligible). For this condition we get $R_L = \frac{5 \cdot 5}{2} = 2 \cdot 75k\Omega$ so let's use a 2·2kΩ resistor to be on the safe side. Having fixed this value we can now work out that Tr1 will have to sink a current of $\frac{6}{2 \cdot 2} = 2 \cdot 7mA$ in order to turn off Tr2. So we want a nice little low power high gain device for Tr1, something like the ubiquitous BC109 should be sufficient, **Fig.4.**

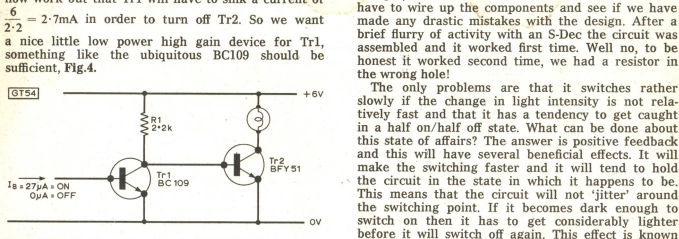

Fig. 4: The value of the load resistor for the BC109 has been decided upon.

The gain of a BC109 is stated as lying in the range 200 to 800. If we assume a value of 100 at worst we're going to need a base current of up to 27μA to turn on Tr1. Well, we want the BC109 to turn on when the resistance of the LDR drops to a low enough value so we are going to have to connect the LDR from the base up to the positive power supply line as shown in **Fig.5.**

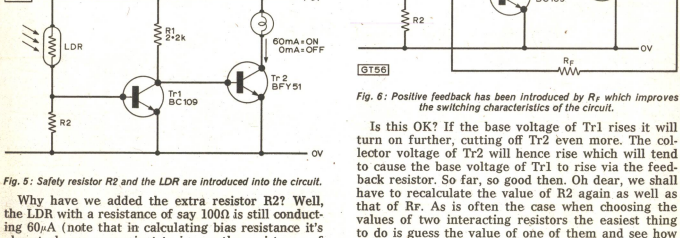

Fig. 5: Safety resistor R2 and the LDR are introduced into the circuit.

Why have we added the extra resistor R2? Well, the LDR with a resistance of say 100Ω is still conducting 60μA (note that in calculating bias resistance it's almost always convenient to ignore the resistance of the base-emitter junction: more correctly the input resistance). Let's assume that if the LDR is at 100kΩ then we want to pull the base of Tr1 down to a 3V to leave a good safety margin. For this condition R2 has to have a value of at most $\frac{0 \cdot 3}{5 \cdot 7} \times 100 = 5 \cdot 3\Omega$ so 4·7kΩ seems safe enough. Now if the value of the LDR drops to 10kΩ the base voltage will rise to $\frac{4 \cdot 7}{4 \cdot 7 + 10} \times 6 =$ 1·9V. We had better just check that the 27μA base current now being drawn by Tr1 does not effect this too drastically. Well, the current being drawn by the bias network of the LDR and R2 is over 400μA so the 27μA not required by the base is going to make hardly any difference and we have a good margin of error with a base voltage of 1·9V.

Moment of truth

Right, now comes the moment of truth when we have to wire up the components and see if we have made any drastic mistakes with the design. After a brief flurry of activity with an S-Dec the circuit was assembled and it worked first time. Well no, to be honest it worked second time, we had a resistor in the wrong hole!

The only problems are that it switches rather slowly if the change in light intensity is not relatively fast and that it has a tendency to get caught in a half on/half off state. What can be done about this state of affairs? The answer is positive feedback and this will have several beneficial effects. It will make the switching faster and it will tend to hold the circuit in the state in which it happens to be. This means that the circuit will not 'jitter' around the switching point. If it becomes dark enough to switch on then it has to get considerably lighter before it will switch off again. This effect is known as 'hysteresis'. How can we achieve this desirable characteristic? Well, the only convenient place from which to take the feedback seems to be at the collector of Tr2, as shown in **Fig.6.**

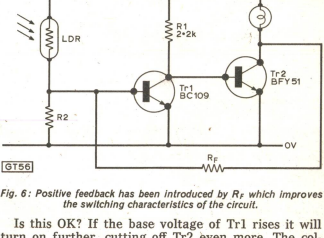

Fig. 6: Positive feedback has been introduced by RF which improves the switching characteristics of the circuit.

Is this OK? If the base voltage of Tr1 rises it will turn on further, cutting off Tr2 even more. The collector voltage of Tr2 will hence rise which will tend to cause the base voltage of Tr1 to rise via the feedback resistor. So far, so good then. Oh dear, we shall have to recalculate the value of R2 again as well as that of RF. As is often the case when choosing the values of two interacting resistors the easiest thing to do is guess the value of one of them and see how it goes. How can we go about guessing a reasonable value for RF then? Looking at the circuit it is apparent that if RF has a much lower value than that of the LDR then the LDR will never be able to change the state of the circuit. If RF is too large its effects will be reduced and we won't get enough hysteresis. Hence we shall choose a value of RF comparable with that of the LDR, say 100kΩ.

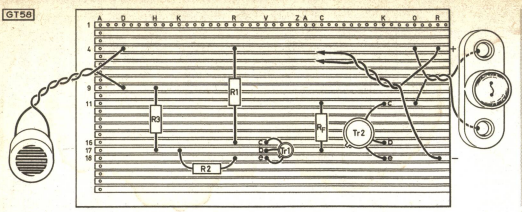

Fig. 8: Layout of components on a Blob-Board, if this method of construction is adopted. A photograph of this board appears on the first page of this article.

Now when the collector of Tr2 is at 6V RF must not be able to turn on Tr1 without the aid of the LDR. Let us aim to try and get the base voltage down to 0·3V, at least. With an LDR resistence of 100kΩ we have an effective resistance between the base and the 6V line of 50kΩ (100kΩ+100kΩ in parallel) so we can calculate R2 to be $\frac{0{\cdot}3}{6{\cdot}0 - 0{\cdot}3} \times 50 = 2{\cdot}63\text{k}\Omega$, so let's say 2·2kΩ. We have now got to check that

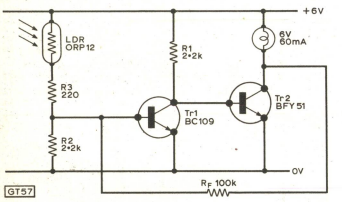

Fig. 7: Final circuit with values of all the components.

when the LDR has a value of 10kΩ the circuit has turned off. If Tr2 is on then RF will effectively be in parallel with R2 and hence the former may be ignored as its resistance is fifty times higher. So, ignoring the base current again, we find that the base voltage of Tr1 is $\frac{2{\cdot}2}{10 + 2{\cdot}2} \times 6 = 1\text{V}$ so this is plenty to turn on Tr1. We can now draw the final circuit as in **Fig.7.**

You will see that a 200Ω resistor has been added in series with the LDR. The truth of the matter is that neither of us noticed until we constructed this stage that there is the possibility that if the LDR resistance drops down to the 100Ω region (in very bright light) then we would have about 6mA of base current in Tr1. Whilst little harm is likely to come to our BC109 because of this it seems wasteful and the series resistor will protect Tr1 if one of us manages to short out the LDR in an aberrant moment.

The circuit now switches cleanly and quickly regardless of the slowness of change of the light intensity and it is impossible to get the output into an intermediate state.

If you wish, you can build the circuit on a PB Electronic's 'blob board' such as the ZB1V as shown in **Fig.8** and the photograph.

Postscript

Well, we have finished now. You may wonder why at each stage we took fairly pessimistic values for the gain of our transistors and chose our resistor values so as to give something in hand over the value we actually calculated. The idea is that all this gives us sufficient in reserve to deal with all the little things we did not consider such as running the transsiistors at voltages and currents different from those at which the gain is specified, resistor tolerances or variation of battery voltage.

We hope that it is going to be one of the main messages of this series. For experimental projects you can ignore all these minor effects providing that you design sensibly with "power in reserve"!

Next month's contribution will describe the design procedure for the circuit of a power supply intended to operate a cassette recorder in a car.

DON'T MISS YOUR FREE POCKET MAGNIFIER IN NEXT MONTH'S PW ON SALE SEPT. 2

PCB SERVICE FOR READERS

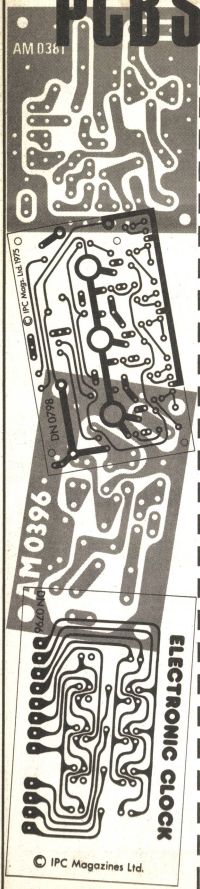

All boards, except SRBP, are glassfibre, drilled and roller-tinned

To:- READERS PCB SERVICES LTD, PO BOX 11, WORKSOP, NOTTS

Please supply PCB/s as indicated by tick/s in box/es

Issue	Project	Ref	Price	P/P
Dec 75	Sound-To-Light Display	DN0798	1·15+12	☐
Dec 75	Disco System, Amp. (2 required)	each AM0421	4·40+22	☐
Dec 75	Disco System, Light Modulator	AM0423	3·50+22	☐
Mar 76	CMOS Crystal Calibrator	AM0438	1·19+12	☐
Apr 76	Wobbulator	AM0443	1·08+12	☐
Apr 76	Auto. Slide Synchroniser	AM0441	2·33+15	☐
June 76	Dig. Freq. Meter (set of 5)	A015 and 4x A004	3·17+15	☐
July 76	Transistor Tester	A002	3·08+18	☐
July 76	Disco Preamplifier	A003	0·65+12	☐
Aug 76	Cassette Player Power Supply	A001	0·65+12	☐
Sep 76	Capacitance Meter	A009	2·59+14	☐
Oct 76	Digital Car Clock (set)	A001/2/3	2·58+12	☐
Oct 76	Interwipe	DN8JM	0·80+12	☐
Oct 76	Video-Writer (set)	D002/3/4/6 A007	21·44+50	☐
Oct 76	Hazard Flasher	D005	0·76+12	☐
Nov 76	Low Level Battery Indicator	A016	0·40+12	☐
Nov 76	Electronic Thermostat	A017	1·30+12	☐
Nov 76	Cirtest Probe	A018	0·48+12	☐
Nov 76	Burglar Alarm	A019	0·50+12	☐
Dec 76	Chromachase	A021	5·70+22	☐
Jan 77	Oscilloscope Calibrator	A023	1·25+12	☐
Jan 77	Icelert	A020	1·45+12	☐
Jan 77	Polyphon, motor and main boards	A025/4	7·90+20	☐
	Polyphon, tune disc, blank, SRBP	A008*	0·90+15	☐
Feb 77	Transistor Checker	A026	1·18+12	☐
Mar 77	FM Stereo Touch Tuner	D023/4/5	7·50+20	☐
Apr 77	Tug 'o' War (set)	A029/030	2·88+12	☐
Apr 77	Gas/Smoke Sensor Alarm	A028	0·65+12	☐
May 77	2-Way Intercom	D019	1·28+12	☐
May 77	Protected Battery Charger	A027	2·38+12	☐
May 77	Seekit Metal Locator	A031	3·38+12	☐
June 77	Reverberation Amplifier	A032	2·38+12	☐
June 77	Versatile AF Generator	A033	2·38+12	☐
June 77	Tele-Games	D029	3·22+18	☐
July 77	20W IC Amplifier	A034	1·38+12	☐
July 77	Radio 2 Tuner	A035	1·68+12	☐
July 77	Digital Clock Timer	A036	3·28+12	☐
Aug 77	Shoot (Telegames)	D035	1·55+15	☐
Aug 77	Atomic Time Receiver	D036	2·65+15	☐
Aug 77	Morse Code Tutor Cards (SRBP)	A037	1·75+15	☐
Sept 77	Jubilee Electronic Organ	A038	19·00+75	☐
Sept 77	Electronic Car Voltage Regulator	D037	1·25+12	☐

Post and packing is for one board or set of boards. Prices include VAT
Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required.

I enclose Postal Order/Cheque — ACCESS welcome.

No..... — Send card number only.

for £..... made payable to READERS PCB SERVICES LTD.

NAME.....

ADDRESS .....

.....

..... Post Code .....

Any correspondence concerning this service must be addressed to READERS PCB SERVICES and not to the Editorial offices.

electronic CAR VOLTAGE REGULATOR

C.GRAYSON B.Sc

In this age of sophisticated electronics in the car the traditional method of regulating the supply voltage by a pair of vibrating contacts with all the associated pitting, arcing and electrical noise, is, to put it mildly, outmoded. Therefore, this simple but reliable electronic regulator was designed.

The 'chopper' was originally designed to be a regulator for motorcycles but it can be calibrated for any DC field and armature, dynamo generating system. A CMOS integrated circuit was chosen for the heart of the circuit because of its high immunity to electrical noise, of which there is a great deal in car systems, and its ability to operate at a variety of supply voltages, of which there is precious little on a motorcycle.

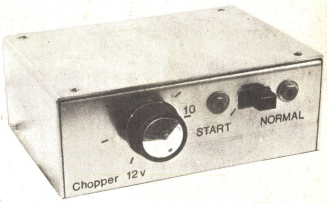

The one control on the Regulator adjusts the voltage while the slide switch enables the system to be started up if the car battery is flat.

IC Details

Some readers may be unfamiliar with the integrated circuit used in this project. It is the RCA CD4007A described as a 'dual complementary pair plus inverter' and its internal configuration is shown in **Fig. 1.** Basically the device consists of three CMOS inverters in various stages of dismemberment. Consider the inverter comprising p1 and n1. These are, respectively, a 'p' channel and an 'n' channel enhancement mode MOSFET. These may be considered as a resistive bar of 'p' or 'n' type silicon overlayed with an insulated metal electrode. The potential on the electrode (gate), controls the number of holes or electrons allowed to pass along the bar from source to drain. Thus, each MOSFET is basically a voltage controlled resistor with an R_{ds} on of about 500Ω and an R_{ds} off of greater than ten thousand megohms! Now if pins 13 and 8 are connected together on the CD4007A and a positive voltage is applied to pin 6 then the 'n' channel MOSFET is in the ON state and the 'p' channel is OFF. Thus, the output at pins 13 and 8 is the inverse of the input. In the 'chopper' two inverters are formed with the inputs at pins 6 and 10. The third 'p' channel device is not used but the 'n' channel is used in isolation as a voltage controlled resistor.

The Circuit

Now we can consider the circuit **Fig. 2,** of the 'chopper' in greater detail. Transistor Tr1, diodes D1 and D2, and resistors R1 and R2 form a constant current source of about 8mA which feeds D7 and C1 to give a regulated voltage of about 4V, which is fed to the supply pins of the IC. In the final analysis, this is the reference voltage for the whole system as the voltage-resistance characteristic of the feedback MOSFET is not absolute but relative to the substrate potentials.

The heart of the circuit is a CMOS oscillator with the halves of its cycle separately set in duration. The basic CHOS oscillator is shown in **Fig 3.** If, say, the output of N2 is high then C_{te} becomes charged positive, consequently the input to N2 is high and its output is low, thus C_{te} is discharged to ground through R_{te}. When the voltage on the input of N1 passes through its transfer point, the output goes high and

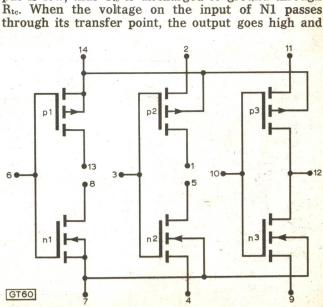

Fig. 1 : Basic circuit of the CD4007 IC used in this project as a 'chopper'.

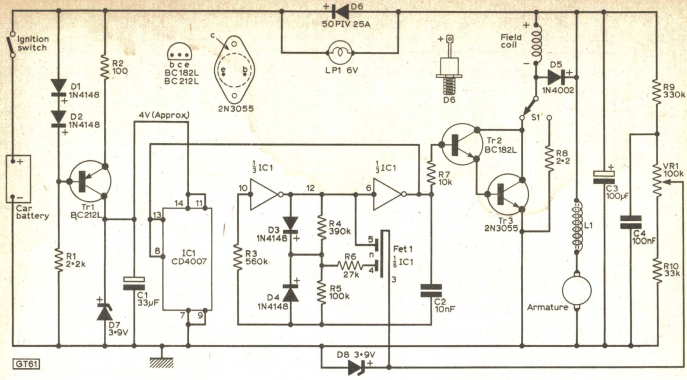

Fig. 2: The complete circuit of the Regulator. It is essential that the transistor Tr3 and Diode D6 are insulated from the metal case with the proper insulating kit or washers.

as a result the output of N2 goes low charging C_{tc}. Now R_{tc} provides a charging path for C_{tc} until the transfer point is again passed and the cycle repeats. For an ideal transfer point of 50% of the supply rails the time period of each half of the cycle is about $0{\cdot}7R_{tc}C_{tc}$ but this rises to around $1{\cdot}1R_{tc}C_{tc}$ when R_x is included to limit the current through the input protection diodes of N1 and to make the frequency of the oscillator relatively free from supply voltage variations.

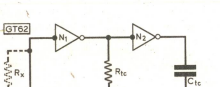

Fig. 3: Basic circuit of the CMOS oscillator, the operation of which is described in the text.

In the voltage regulator the oscillator is used to chop the supply to the field coil of the dynamo. Obviously, the longer the current is allowed to flow in the field coil via Darlington pair Tr2, Tr3, then the higher will be the armature voltage. Accordingly, the OFF period is set at 1·25ms by C2 charging through R5 when the output of N1 is high and the ON period is variable from 350μs to 5ms depending on the combination of R4, R6 and the D_{ss} of FET1.

The action of the circuit is as follows; when the machine is started up there is no voltage fed back by potential dividing chain R9, R10 and VR1. Hence, the R_{ss} of the FET is almost infinite and the field coil is energised with a 4:1 mark-space ON waveform and the armature voltage rises to feed the vehicle battery, light, etc through power diode D6 (which is necessary to prevent current feeding back from the battery into the armature winding). A proportion of this voltage is fed back to the gate of the 'n' channel FET to lower the total resistance presented to C_{tc} as an ON time discharge path. Thus, the field coil is excited for a lower proportion of the time and the voltage tends to fall. The converse is true, and a state of equilibrium is reached and the voltage is stabilised irrespective of engine speed or load. If VR1 is set to tap off less voltage then the regulated voltage at the anode of the power diode will rise to maintain the equilibrium thereby giving a wide range of control. The inductance of the field and armature coils combine to integrate the pulsed drive waveform to give a smooth output voltage.

★ components

Resistors

R1	2·2kΩ	R5	100kΩ	R9	330kΩ
R2	100Ω	R6	27kΩ	R10	33kΩ
R3	560kΩ	R7	10kΩ	VR1	100kΩ linear pot
R4	390kΩ	R8	2·2Ω 5W		

All resistors ¼W 5% except R8

Capacitors

C1	33µF 16V electrolytic	C3	100µF 25V electrolytic
C2	10nF paper foil	C4	100nF disc ceramic

Semiconductors

Tr1	BC212L	Tr3	2N3055
Tr2	BC182L	IC1	CD4007A
D1/4	1N4148	D6	50V PIV 25A
D5	1N4002	D7/8	Zener 3·9V (BZY88C3V9)

Miscellaneous

Insulating kit for 2N3055. Insulating washers for D6. Aluminium case approx 100 × 70 × 40mm or larger. S1, slide switch DPDT (connect contacts in parallel). LP1, lamp 6V 40mA. L1, 50 turns 26SWG insulated copper wire on 10mm dia. ferrite rod. PCB from PW Readers PCB Service.

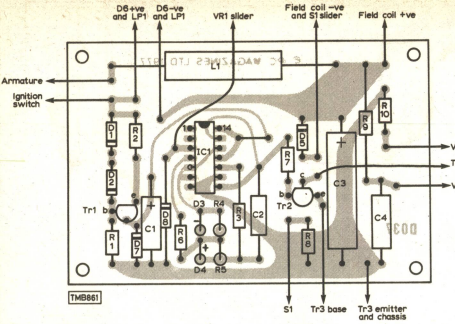

Fig. 5: The components mounted on the PCB are fitted as shown here. Check the lengths of the leads required for fitting the unit to a particular vehicle before soldering them to the board.

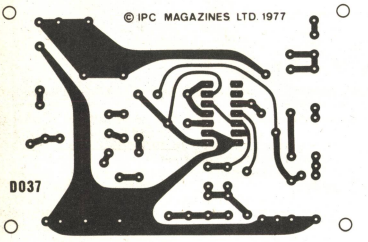

Fig. 4: Foil pattern of the printed circuit board, shown here actual size.

Anyone who has looked at the output of a car dynamo armature will attest to the apparent lunacy of connecting a delicate CMOS input directly to it. The 'chopper', however, incorporates a second order L-C low-pass filter comprising L1, C3 followed by a first order R-C low pass with R9, C4 to eliminate the hash from the output. Further protection is afforded by D8 which prevents any voltage greater than 4V appearing at the input which would forward bias the internal protection diodes and damage the integrated circuit. Finally, D5 protects the driving transistors from induced high reverse voltages. LP1 is the dashboard discharge lamp which glows when there is a reverse voltage across D6, and S1, R8 provides the facility to start the system up if the battery becomes very flat or disconnected.

Construction

Good solid construction is of the greatest importance where the circuit is to be exposed to the hot, dirty and vibrating environment of the road. Assembly is greatly eased by the use of the PCB shown in **Fig. 4.** Coil L1 is formed by winding about 50 turns of 26 SWG insulated wire on a 70mm length of 10mm diameter ferrite rod. The whole assembly may be conveniently secured to the board with epoxy resin. After L1, mount the passive components followed by the semiconductors and finally the integrated circuit. Care should, of course, be taken in handling CMOS. The supply pins should be soldered first with a well-earthed iron followed by the remaining pins. Component layout is shown in **Fig. 5.**

The board is mounted in a standard 100x70x40mm aluminium box. Tr3 and D6 are mounted on the rear face as shown in **Fig. 6.** S1 and VR1 are similarly mounted on the front face. As the power transistor operates in the switched mode very little power is dissipated and the aluminium serves more as a convenient mounting than a heatsink. The collector of the transistor is electrically isolated from the earthed chassis by a mica washer and bushes. The power diode is similarly mounted through a 10mm hole, again, under all but the most exceptional of circumstances, no heatsink is required. Wiring is quite straightforward but care should be taken to use heavy gauge copper wire in the high current section of the circuit.

Setting Up

The usual configuration in the electromechanical regulator situation is for one end of the field coil and one brush of the armature to be connected to the chassis while the other ends (usually marked F and D) go off to the regulator where they are joined by a resistor of some 3 to 4Ω. Now the earthy end of the field coil must be disconnected and wired into the circuit with the other two terminals as shown in **Fig. 2.** A little trial and error may be necessary with the values of R9, R10 and VR1 to give the correct range of adjustment and voltage.

As the characteristics of dynamos and CMOS devices vary so much a greater degree of control may be required. To achieve this the value of **R4** may be increased to 1MΩ while R6 is decreased to 10kΩ to give a 10:1 variation in mark-space. With

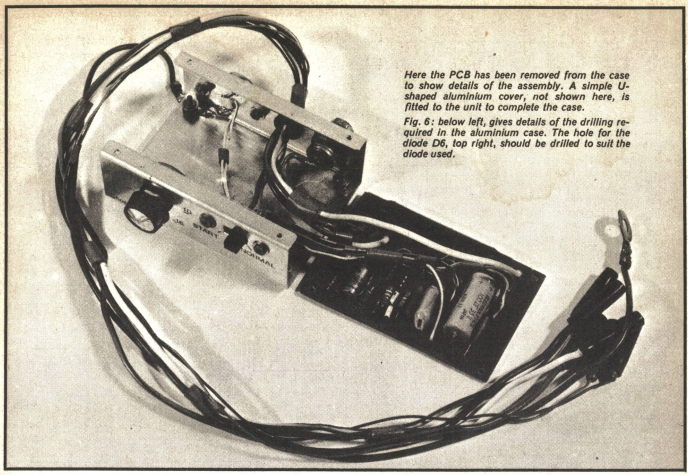

Here the PCB has been removed from the case to show details of the assembly. A simple U-shaped aluminium cover, not shown here, is fitted to the unit to complete the case.

Fig. 6: below left, gives details of the drilling required in the aluminium case. The hole for the diode D6, top right, should be drilled to suit the diode used.

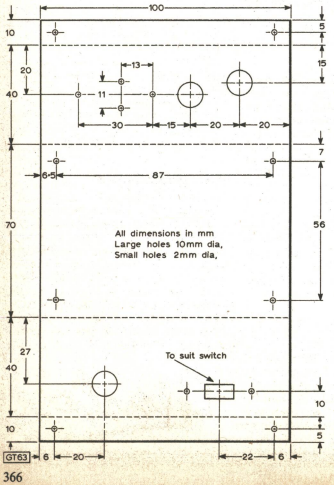

the values as shown the range of adjustment is from 10V to 16V on a Lucas type C40-1 generator. For a 6V system reducing R9 to 100kΩ and R10 to 10kΩ should prove to be about right.

When adjustments are complete the unit should be securely bolted to some convenient earthed part of the chassis with the leads to the dynamo, ignition switch and charging lamp taken out through a hole in the rear of the case and terminated in standard bullet connectors.

Positive Earth

Finally, it might be added that a positive earth version of the 'chopper' is quite possible and would merely involve reversing all polarised components except D3 and D4, together with transposing Tr1 and Tr2. A 2N2955 or similar pnp power transistor must be substituted for Tr3 and finally the track to the negative supply pin of the integrated circuit must be broken and the supply voltages transposed.

Now, the voltage feedback to the FET acts on the R_{ds} in the opposite sense, but the pnp transistors require the complementary logic level to turn them ON. Thus the two phase inversions cancel themselves out and the PCB layout given can still be used. However, with the advent of more electronics in the car many readers will probably wish to do as the author did and take the opportunity of fitting the 'chopper' to convert a positive earth system to the more convenient negative earth. This consists of removing both field and armature coils from the chassis and reconnecting both in the opposite sense, not forgetting to reverse the connections to the vehicle battery and any other polarity sensitive items already fitted. ●

HOTLINES

A REVIEW OF RECENT DEVELOPMENTS
In general, the author does not have any more information on products than appears in the article.

Measured charge

One or two items currently launched on the electronics market tend to remind us of the advances made in the field. Solid state relays, for example, have edged their way up the power-handling capability curve with almost monotonous regularity. I see that one of the very latest to appear (the GB15000 type) can handle a continuous current of 40A with a peak voltage rating of 600V.

Another item is a capacitance meter. Not much bigger than a small hand-held calculator it has a universal socket arrangement for the input(s), a push-to-read button, and a liquid crystal readout. To measure the value of your capacitor, you just poke its leads into the appropriate socket holes and press the button. The unit will give capacitance values from 0·1pF right up to 0·2 Farads. The meter is auto-ranging in that a LED illuminates to show that the reading is in pF, nF, µF or mF.

Viva la weed

It used to be said that the Chinese were "damned clever", but the French seem to be making a bid for this title: would you believe an electronic greenhouse?

Heart of this system is a thing called Firmin which is contained in an area less than 5 × 5 × 8in. Firmin carefully measures things like the soil conditions, the ambient light level, evaporation rates etc. It also computes just how thirsty each plant is and then supplies it with just the right amount of water. The system operates from solar cells as a power source.

Firmin has a calculator and a memory plus a section associated with a motor which controls a valve regulating the water flow. It is continually monitoring and comparing the plants' requirements with the environment so it's quite a precise system. It must be nice for the computer in Firmin to receive an order from hollyhock number five, "A large water—and leave the bottle!"

Open sesame!

Popular electronics construction journals have often published details of ultrasonic control systems. Those interested in this area will be pleased to hear that a German semiconductor manufacturer is to launch a set of three ICs which will allow hobbyists to make an infra red control system; useful for things like opening and closing garage doors, TV control, light dimmers etc.

The system employs pulse-code modulation and is initiated by simple push buttons. Up to 60 (sixty) command signals are possible from a hand-held, battery-operated transmitter. The receiver can be built into a space about 3 × 3 × 1in.

High hopes are held for the infra red system since it has certain advantages over its ultrasonic brother. For example, in the application of opening and closing garage doors the ultrasonic system could not work efficiently from a hand held device inside the car because the "sound" waves would not penetrate the car body etc. The infra red waves, however, can pass through glass and the IR system could be simply pointed through the cars' front windscreen.

Please note: these ICs are not available as yet.

Powerful FET

The arguments regarding semiconductor devices and valves at UHF still rages, with the semiconductor people edging a little closer each year. A new device just launched is a FET which can generate 1W at 8GHz with a 9·2dB gain. Impressive though this might be for a gallium-arsenide FET, it does have rather a long way to go to compete with the VTS-5753A1. This is a travelling wave tube which has a power gain of 47dB and a peak output at 3·3GHz of 120kW. I have to smile at the valve manufacturer who said of the semiconductor manufacturers of devices at these frequencies, "Ah yes, they make Watt-nots".

Get it taped

Video cassette recorders for the home haven't really taken off as yet in the UK, probably on account of the cost. But I am pleased to learn of sensible co-operation between two European manufacturers. Although individually developed, a close consultation between them during development has resulted in two systems that are compatible. Both will now record over two hours of colour TV programmes without a cassette change. In real terms this long recording time means that an entire football match could be recorded (or even a full length feature film) all on one cassette.

A useful (?) feature on one system is a highly accurate digital clock which allows its owner to select the turn-on and turn-off times of the equipment up to four days ahead of the time that recording is required.

Interesting to note that one manufacturer claims some 90,000 video recorders are in use in West Germany, and over 250,000 in the US.

Interested?

Good news for computer enthusiasts—cheaper items are on the way. One of the newer systems costs only $495 in the US and consists of a 73-key keyboard, 9in CRT, an 8-bit microprocessor, and 4,096 bits of random access memory which operates with Basic programme language. A built-in cassette player allows easy entry of recorded programmes.

Anyone interested in this area of electronics should drop a line to Mike Reeve. He is the secretary of the Amateur Computer Club and you can reach him at 6 Limes Avenue, North Finchley, London N12 8QN. Letters should be written in Basic English!

The write beam

Print-out devices are commonly offered on the electronics market, but one just mentioned in Japan seems to be something else. It uses a laser beam to do the "writing" on a photo-sensitive drum. The letters/characters are made up to a resolution of ten "dots" per millimetre. Printout is at six lines/inch but the twist in the tail is that this printer will printout 10,000 lines every minute! Perhaps it might be called "Print Sprint"?

Ginsberg

AMATEUR BANDS

by Eric Dowdeswell G4AR

The Torbay ARS let their hair down at their AGM with no less than eleven complaints on the current operation of the RSGB. Most are long-standing, such as too-technical articles in Radcom and nothing for the newcomer to amateur radio, late and varied posting of Radcom resulting in some readers not being able to take advantage of the 'For Sale' columns. The alleged delay on book orders etc. surprises me in view of the success of the new computer system. However the 1977 President's Committee may come up with some answers in due course, although I doubt it, as the reasons for the complaints are too deep-seated to admit of a simple solution. But one of TARS complaints, that the Society's AGM is always held in London instead of being allowed to 'go on tour', should not be difficult to solve!

First item this month must concern **Barry Harper** of Wednesbury, West Midlands, who was playing around with an old radiogram when he picked up a distress message from an Italian ship in trouble off Rome. Barry alerted his local police who contacted the coastguard authorities who passed a message to Rome. Their coastguards did in fact then locate the fishing vessel in distress. Barry's local press gave him a write-up but, not unusually, got most of the facts wrong! Apparently, Barry is going to rebuild the radiogram and adapt it for SW transmission! And study for a licence to broadcast! Actually, Barry has a No. 19 set that he has been playing with, mostly on 80m, but he's not too happy with the results on SSB.

Brian Harrison in Ore, Hastings continues to find plenty of daytime activity on 10m including KV4 and 8P6, while 20m turned up an HH which is not all that common on any band. In Dringhouses, York, **John Hague** continues to swot up the code so let's hope we shall be getting some interesting CW logs from you soon, John. Scottish reader **John Overton** BRS36909 of Glasgow has been lucky enough to enlist the help of two local amateurs GM4CNF and GM4EAW and now sports a BC348 receiver in place of his old CR100. John plans to sit the RAE in December and has not forgotten to keep up with the code. Talking of the code, I hope that the Morse Tutor in the August issue of PW proves of interest, especially in the clubs, where it would make an interesting project. This month sees the start of a series for those interested in studying for the RAE, which, I hope, includes most of the readers of this column!

John Reynolds, Bridgend, still plays around with his TRF in lieu of anything better. Being still at school limits the cash available. Well, John, be patient, stick to the 'A' level studies which are, by far, the most important item at the moment and perhaps everything will come right 'ere long.

Changes at the West of Scotland ARS where **Tom Wylie** GM4FDM is now the Hon. Sec. Write to him at 38 Rosedale Avenue, Paisley, if you'd like details of their summer programme. Another reminder of the North West Amateur Radio Convention to be held on 17 and 18 September and organised by the University of Lancaster ARS. Contact P. L. Jones c/o Dept of Physics, Univ. of Lancaster, Bailrigg, Lancaster for details.

Peter Page of Epping, Essex is yet another who has returned to the bands after a long break. He has an Eddystone 840 which still worked when the cobwebs were removed! A dipole for 20m suffices for the moment but plans are afoot to improve this situation. **John McFadden** keeps going in Belfast finding plenty of South Americans on 15m in the evenings. John mentioned W7ALD/MM. I normally refrain from commenting on these maritime mobile calls since by the time it appears in print the ship is thousands of miles away somewhere else or in dock and the operator paid off!

Once a reader of this column gets his/her own licence I don't normally expect to hear from him/her again! Quite understandable, of course, since the first flush of enthusiasm lasts quite a while and every spare moment is spent on the air, not writing letters but QSL's! So it was good to have a note from **Jeremy Hinton** who now signs G4EZE (was A8962 and G8LIZ) from Newcastle in Staffs. He used the GE special prefix during the Jubilee celebrations and generated a pile-up of Europeans, just for a change. Nice for the G's to get in the act at last! Jeremy uses an FT200 transceiver into a W3DZZ multi-band trap dipole. He's getting the knack of working the DX but sometimes feels he'd like a kW and a multi-element beam! Then where would the fun be, OM?? It would all be too easy, like working through repeaters!

Another pair of fellows enjoying the DX by sharing a KW201 receiver between them are **Paul Pasquet** A9105 and **Iain Christie** A9201, near Farnham, Surrey. They have another set, built by G4DPP, kept for the BC bands. Back on the amateur bands, they have amassed 160 countries so far this year. Another event on which a reminder would not be out of place

is the RTTY lecture and demonstration by G3MFJ and G3WWF on 16 August by the Wakefield and District Radio Society at Holmfield House. Ring Bob Firth G3WWF on Leeds 825519 for details.

Alan Doherty reports from Portrush, N. Ireland, that he had little response from his appeal for readers in his area to contact him with a view to forming a club. His success with stations in the Pacific has been mostly over the long path in the mornings. He reports poor returns from QSLs sent out but that is not an unusual situation. Personally speaking, I think the average listener to the amateur bands is wasting his time getting QSLs, not to mention the expense. Much better to spend the time studying for the RAE and then to get QSLs that represent much more of an achievement, a two-way QSO!

The Midland ARS is mourning the loss of Bob Palmer G5PP a past President and long established member of the club, giving lectures and organising constructional projects for other members. He was a great contest man and frequently combined holidays with a DX-pedition. This, of course, meant a great interest in mobile rallies which often meant a lot of hard work for him. After his retirement he was able to spend even more time on his hobby. I remember working him myself on many occasions in CW contests and so I know that the Midland ARS has lost a fine operator.

Good news from **Paul Barker** in Sunderland who says that he is intending to sit the RAE in December next. He is one of many studying at home so I sincerely hope that our news course on the RAE, starting in this issue, will be of some use to him. Paul, you may remember, is a very keen SSTV type and has not entirely deserted the DX bands in search of new countries to log. Just think, Paul, you will soon be able to answer back! Paul was third in his category in the 1st. Worldwide SSTV contest but still feels he did not do as well as he might have done due to QRM. Paul now has an 18AVT vertical multiband aerial which should have gone up by now.

An interesting letter arrived at the last moment from Harry Leeming G3LLL who tells me that, provided there is sufficient support, he will once again be running an RAE course, later in the year. Send your enquiries to the Principal, The College of Technology and Design, Feilden Street, Blackburn.

Late News, page 374.

Log extracts

P. Barker:— 20m AP5HQ C6ANO (Bahamas) KZ5JM TA1MB VP8SM YB6ACV **20m SSTV** DK2ZX LZ1MH OK1KO OZ3WP WA2PCY YU1CS 9G1JX

A. Doherty:— 20m JY25YJ KA6ML KP6AL KP6BD (Kingman Reef) KX6BU TU2EF VP8HZ VR1X YS1ESH 9M8HG **10m** A9XBC PY2HY ZP5SD

P. Pasquet:— 20m PJ3BW TT8SM 3D6BE 6W8LZ **15m** VP2GAH VP8PC TR8GB 9V1SW

J. Hinton:— worked 20m JY25MB KA6SS

J. McFadden:— 15m CP5AO EA8LD EP2RL HI8XBH HK1ZF KZ5KS LU5MBC PY2FMP PZ1DR VP2LL 6Y5GB

C. Page:— 20m CT3BO HR3JJR 6Y5KD

J. Overton:— 20m HC2CG HR1JAG KH6BTD KS6FL

B. Harrison:— 20m HH2MC OY5NS ZD8RR **15m** HM5HB YN7NI 6W8FZ **10m** KV4CI YV5ATX 8P6AJ

J. Hague:— 15m EP2RR JY4JW 9H4F

All reports are SSB unless indicated otherwise.

BROADCAST BANDS

MEDIUM WAVE DX

by Charles Molloy

Broadcasts from the Near East present quite a problem to the medium waxe DXer. The time zones of this part of the world are some two to four hours ahead of GMT which means that many of the medium wave stations there have already signed off for the night by the time European QRM starts to clear at 2300. There are a few exceptions. Bagdad is a regular on 760kHz sandwiched between West Germany on 755 and Switzerland on 764 and it can be heard throughout the evening. Another is Kuwait on 1345 which lies between the BBC on 1340 and France on 1349. Others than can be located in this way are Kermanshah, Iran on 895 just below Milan on 899, Ahwaz Iran on 1390 between European channels 1385 and 1394, Sharjah in the United Arab Emirates on 1575, between East Germany on 1570 and Norway on 1578.

An alternative is to listen between 0300 and sunrise when stations can be heard signing on for the day but the best time of all for DXing the Near East is during the month of Ramadan, the ninth month in the Moslem calendar which starts this year on the 16th August. During this period broadcasting goes on for most of the night, many stations staying on the air all night and presenting the listener with the opportunity of hearing DX that otherwise would be difficult or impossible to hear. Listen for Basra on 692; Damman, Saudi Arabia on 885; Antalya, Turkey on 890; Cairo 4 on 940; Damascus 944; Izmir, Turkey on 962; Taiz, Yemen on 1000; Istanbul 1016; Teheran 1088; Radio Oman 1240; Radio Afghanistan 1280; Aleppo, Syria 1313; Kirkuk, Iraq on 1360 and Hyderabad, Pakistan on 1010kHz. Broadcasts from the North African coast should be conspicuous during the late evening. Algeria is on 529, 548, 575 and 980; Tunisia on 584, 629, 719 and 962, Libya on 674, 827, 1124 and 1250 and Morocco on 593, 611, 701, 827 and 1232. On the long waves try for Istanbul on 182, Azilal, Morocco on 209 and Tebessa, Algeria on 251kHz.

"I was wondering if there is any publication available listing the addresses of the lower powered US stations, mainly the 5kW outlets, as I have logged a few" writes **Denis Taylor** from Preston in Lancashire. No need to worry about station addresses in North America. Use the station call letters and the location as announced over the air. For example Radio WEAN Providence, Rhode Island, USA will certainly find this 5kwatter. Denis uses a Realistic DX160 and MW loop and a few of his latest loggings are La Voz de Antioquia, Colombia on 750; WEAN on 790; All India Radio, Rajkot on 1070; Radio Tiempo, Caracas in Venezuela on 1200; Radio Coro, Venezuela 1210 and WVOJ Jacksonville, Florida on 1320.

A large souvenir QSL card issued by KDKA Pittsburg (1020) mentions that their signal has been heard at some time or other in every country in the world and Denis thinks this must confirm world-wide MW reception as mentioned recently in this column. Worldwide reception depends both on the location

of the listener and on the level of local QRM. In western Europe QRM is the main problem but it is unlikely, QRM permitting, that Hawaii and parts of the Pacific will be logged in the UK in other than freak conditions, as the Great Circle path between the UK and that part of the world passes over the north magnetic pole, a region of high absorption of medium wave signals.

"Freetown on 1205kHz is quite a good signal here around 2300, and I have just sent a report to them" says **Roy Patrick** whose QTH is in Mackworth near Derby. This station is the medium wave outlet of the Sierra Leone Broadcasting Service and it goes off the air at 2335 daily with a half hour extension on Saturday. Programming is largely in English. This station does QSL and the address is simply Radio Freetown, New England, Freetown, Sierra Leone.

Roy mentions that the long wave Algerian outlet on 251kHz has been off the air for a few weeks but is now back in service and transmits the French programme of RTA. Another item from Roy concerns MEKO 2 which is now testing from a harbour in Libya, presumably with the permission of the Libyan Government. It has been heard in Derby on 773kHz with announcements in English until it goes off at 2300 (0100 local time).

A letter from **Paul Griffith**, who lives at St James', in Barbados, refers to a MW loop he is constructing. "I ran into a snag in that I am unable to locate a 500pF tuning capacitor in Barbados and have had to order one from the UK" says Paul. This problem has faced some DXers in the UK as well since 500pF variables do not seem to be in demand, other than by constructors of a medium wave loop! Twin-gang capacitors of around 300pF per section are readily available though and one solution to the problem is to use a single section of a twin-gang to tune the HF end of the band and to switch-in the second section in parallel to cover the LF end. There will be some overlap but the additional capacitance when both sections are in use and the vanes closed, will extend the range by only a few kHz, perhaps to 500kHz instead of 540kHz.

The maximum value (vanes closed) of the tuning capacitor is not at all critical. It is the minimum value (vanes open) that is important as it is this amount plus the self-capacitance of the loop and wiring that will determine the highest frequency at which the loop will resonate. For this reason it is not a good idea to use a twin-gang with the two sections in parallel to cover the whole band. If the loop cannot be tuned to a low enough frequency with the vanes closed then the total capacitance is too low and will have to be increased by switching in additional capacitance. This can either be a fixed capacitor or the second section of a twin-gang variable. There is ample scope for the experimenter who can use a twin or triple-gang capacitor from an old radio or a single gang of lower value than 500pF. One design of loop seen by the writer used a 365pF variable, a switch and a 220pF fixed capacitor to cover the band in two sections, thus getting round the difficulty some DXers experience in constructing a loop that will cover the entire range from 540kHz to 1600 kHz.

My original article, 'Medium Wave DXing', which dealt with a practical loop aerial, appeared in PW for April 1970. Back numbers are not available but Eric Dowdeswell, Asst. Editor, is arranging for reprints to be made. Send an SAE **to me** if you are interested.

BROADCAST BANDS

SHORT WAVE BROADCASTS

by Derek Bell

It is with regret that these paragraphs that I write are the last. Over the many years, since December 1974, that I compiled the Short Wave News I have made many friends and, I trust, have helped and entertained many more. I started writing the column with the firm intention of serving all aspects of our hobby from aerials to QSL card collecting. It was never my intention to be a "Radio Times" section and I hope that the items of news and information that were put in helped to broaden my readers' horizons. Indeed it is to these very readers that I owe a debt of gratitude since, were it not for their letters, there would have been no column to write, so if anyone can employ a redundant typewriter jockey any offers will be gratefully received!

Having got that out of the way we will pass on to this month's letters and start with **Roy Patrick** from Derby who passes on the information that Radio Canada is now airing a short DX show on Sundays at 2043. Is this a sign that they are at last reinstating their formerly highly active DX section? Roy also tells me that Radio Nacional Brazilia is to cease its international service due to "technical reasons".

While on Latin Americans, **Alan Proctor** of Bristol has sent an interesting letter on the best verifiers on that continent. He nominates Radio Nacional Bogota and Radio Guaiba, and says that they replied in less than three weeks. Alan does say however that he enclosed two IRCs and, in one case, some Jubilee stamps. These seemed to attract the attention of a staff member who sent a personal reply and Alan is now a firm advocate of the personal touch.

My recent remarks concerning the oldest DXer prompted a reply from **Arthur Leir** of Belfast. While not, let me hasten to add, a candidate for that title, Arthur has been an addict since 1939 when he started with an Eddystone 504. He has QSL cards dating from pre-war which must be something to see. After a lull Arthur had the urge to re-enter the hobby and has purchased a VEP204, and asks about the various publications on the market. Well, Arthur, Short Wave Magazine is still extant but personally I would buy World Radio and TV Handbook from Argus Books, Station Road, Kings Langley, Herts.

It is one of life's ironies that DX strikes in the strangest places. **Andrew Brade**, aged 13, has an old domestic Ferguson 391T with a forty-foot long wire hung on the end. Added to this the cord drive to the dial has broken and so Andrew has to rely on verbal IDs but despite this he has two loggings that deserve a mention, Radio Grenada on 15105 at 2015 and this month's star prize for Voice of the Malayan Revolution on 15790 at 0940 and Andrew logged it for a week. It is reported in WRTVH as a 120kW from Hengyang, China, but I have never seen it reported before.

Recently this column arranged for the delivery of a number of spare speakers to a group of bedfast

Can YOUR Antenna do all this?

A SMALL SELECTION FROM OUR HUGE FILE OF TESTIMONIAL LETTERS ON THE JOYSTICK VARIABLE FREQUENCY ANTENNA (3-30MHz)

G4DJY's COPY LOG shows 68 North Americans worked in the ARRL W/VE contest.

W6TYP worked WA6JPR over hundreds of miles on 40m. using the JOYSTICK VFA and MICRO-WATTS "equivalent to 1,000,000 MILES PER WATT" —A WORLD RECORD—we can supply conclusive evidence!

"I have used Rhombics, 4 x ½ waves in phase, centre fed dipoles, etc., but the success I have had with the V.F.A. has been AMAZING . . . only 20ft high . . . in front of my mobile home, I NEVER RECEIVE LESS THAN R7 AND MOSTLY R9 ON CWDX WORKING —Bob Green, SUIKG/G3APH. W.B.E. W.A.C. Phone & C.W.

W7OE U.S.A. Government Electronics Engr. (retd.), claims "VFA 5ft below ground, same as dipole, elevated 15ft, on "S" point UP on dipole".

IN USE BY AMATEUR TRANSMITTING AND SWL STATIONS WORLD-WIDE AND IN GOVERNMENT COMMUNICATION

SYSTEM "A" £36·00

250 w. p.e.p. OR for the SWL.

SYSTEM "J" £42·60

500 w. p.e.p. (improved 'Q' on receive).

PARTRIDGE SUPER PACKAGES

COMPLETE RADIO STATIONS FOR ANY LOCATION

All Packages feature the World Record Joystick Aerial (System 'A'), with 8' feeder, all necessary cables, matching communication headphones. Deliv. Securicor our risk. Assembled in seconds! BIG CASH SAVINGS!

PACKAGE No. 1	As above with R.300RX SAVE £17·28 !	**£210·55**
PACKAGE No. 2	Is offered with the FRG7 RX. SAVE £12·21 !	**£193·11**
PACKAGE No. 3	New—low priced package.	**£154·86**

The all solid state SMC73 RX with all the Partridge extras. SAVE £17·28!

RECEIVERS ONLY, inclusive delivery, etc.

R.300 £184·50 FRG7 £162·00 SMC73 £128·81

All prices are correct at time of going to press inclusive of 12½% VAT and carriage.

BARCLAYCARD

Just telephone your card number Phone 0843 62535 (or 62839 after office hours)

Buy it with Access

or write for details, send 8½p stamp

G3CED PARTRIDGE ELECTRONIC Ltd. **G3VFA**

Box 5, Partridge House, Prospect Road, Broadstairs, CT10 1LD. (Callers by appointment).

Your free start to a rewarding new hobby.

Heathkit make the world's largest range of electronic kits.

Including amateur radio, test equipment, educational and general interest kits.

Every one of which comes to you absolutely complete–right down to the last nut and bolt.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

So, besides making an attractive, useful piece of equipment, you'll also have the makings of a satisfying, rewarding hobby.

To find out more, post the coupon and we'll send you our latest catalogue. Heath (Gloucester) Ltd., Dept. PW-97, Bristol Rd., Gloucester, GL2 6EE. Tel: Glos (0452) 29451.

HEATHKIT

BETTER BUILT BECAUSE YOU BUILD IT YOURSELF

The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Ltd., Dept. **PW-97,** Gloucester, GL2 6EE. Please send me my Heathkit catalogue.
I enclose an 11p stamp for postage.

HEATH Schlumberger

Name

Address

Postcode

ACCESS AND BARCLAYCARD WELCOMED

Showrooms at 233 Tottenham Court Road, London and Bristol Road, Gloucester.

LYNX ELECTRONICS (LONDON) LTD

92 BROAD STREET, CHESHAM, BUCKS Tel. (02405) 75154

Prices correct as at 30th June 1977

P. and P. 30p — Overseas 80p — Matching 20p per pair. ACCESS WELCOME

VAT 8% except for items * which are 12½% — No VAT Overseas.

IMPORTANT NOTICE

PLEASE NOTE ALL SCHOOLS, COLLEGES, UNIVERSITIES AND AMATEUR RADIO AND ELECTRONICS MAY DEDUCT 10% OFF PRE-VAT PRICES. THIS OFFER ONLY VALID FOR ORDERS OVER £20.

NEWS FLASH

Lynx will be holding a seminar this autumn on microprocessors, microcomputers and their applications. There will be a free competition for a system based on Z80. More details next month.

THYRISTORS

PIV	1A 3A (TO5)	3A (ST-UD)	4A (TO-106)	6A (TO-220)	8A (TO-220)	10A (TO-220)	16A (TO-220)
200	0-35	0-50	0-45	0-40	0-58	0-60	0-68 1-14
400	0-40	0-60	0-50	0-45	0-67	0-68	0-98 1-46
600	0-45	0-65	0-70	—	1-09	1-19	1-36 1-80

BT106 £1-06, BT107 £1-00, BT108 £1-80, BT109 £1-60, BT116 £1-00, BT118 £1-00, 2N3525 £2-50.

TRIACS—Plastic TO-220 Package Isolated Tab

	1A (a)	(b)	3A (a)	(b)	6A (a)	(b)	10A (a)	(b)	15A (a)	(b)
100V	0-60	0-60	0-70	0-70	0-78	0-78	0-83	0-83	1-01	1-01
200V	0-64	0-64	0-75	0-75	0-87	0-87	0-95	1-17	1-17	1-17
400V	0-77	0-78	0-80	0-83	0-97	1-01	1-13	1-19	1-70	1-74
600V	0-96	0-99	1-01	1-10	1-21	1-25	1-42	1-50	2-11	2-17

N.B.—(a) without internal diac. (b) with internal diac.

TTL7400 Series				Regulators		747	1-60	16 Pin	0-15
	7400	0-15	380	0-90*		748	1-80	24 Pin	0-45
7400	0-16	7448	0-35	381	1-68*			40 Pin	0-60
7401	0-16	7490AN	0-49	709	0-27				
7402	0-16	7491	0-65	710	0-28				
7403	0-16	7492	0-65	711	0-28				
7404	0-18	7493	0-45	NE555	0-60				
7405	0-18	7495	0-65	NE565	2-00*				
7406	0-18	7496	0-67	NE566	2-00*				
7409	0-18	7497	0-67	NE567	2-00*				
7410	0-16	7498	0-85	CA3045	3-00*				
7412	0-25	74100	1-07	CA3046	0-89*				
7413	0-40	74107	0-30	CA3052	2-50*				
7414	0-72	74121	0-34	MC1304P	1-66*				
7416	0-43	74122	0-40	MC1305P	1-66*				
7417	0-43	74123	0-60	MC1310P	1-66*				
7420	0-20	74141	0-80	MC1312P	1-66*				
7425	0-30	74145	0-58	MC1352P	0-75*				
7427	0-30	74150	1-20	MC1358P	0-75*				
7430	0-16	74154	0-93	MC1458P	0-77				
7432	0-30	74157	0-70	MC1496L	0-82*				
7437	0-80	74174	1-40	MC1496G	0-82*				
7441AN	0-78	74175	0-70	SAS560	2-25				
7442	0-65	74180	0-66	SAS570	2-25				
7445	0-96	74181	1-80	AA200	1-95				
7447AN	0-81	74191	1-33	TAA310A	1-98				
7448	0-81	74192	0-70	TAA320	0-95				
7470	0-30	74193	1-35	TAA611B12*	2-25*				
7472	0-26	74194	1-64	AAZ051	0-65				
7473	0-30			TBA530	1-95*				
7474	0-26			TBA540	1-95*				
7475	0-42	Linear I.C.s		TBA550	2-95*				
7476	0-36	3ΔA	0-48*	Medium Voltage, Fully unmarked. Similar to					
7485	0-85	307	0-55*	TCA270SQ*	0-95*				

SPECIAL OFFER SECTION

SG306K IATO3 5v...0-95 TIL209 Red Led...0-16

MM8314 ..... 3·25 MM8316 ..... 3·95

NPN 10 Watt Power Transistors. Fully tested but unmarked. Similar to 2N3055 except: BVCEO = 50+ VCE (sat) = 20 + at 3A, VCE SAT < 1·3V at 3A fT pcs 2MHz 25 pcs £4·00, 50 pcs £7·50, 100 pcs £13·00

TO-18 NPN Transistors. Medium Voltage, Fully unmarked. Similar to BC107/8/9, 25 pcs 1·20, 100 pcs 3·50 **Power Transistors.** 2N3055 Hardware. Mica, Washers, Solder tag. Nuts, Bolts, 50 sets for £1·00 **Rectifiers DO-4 Package.** 100 50V 6 Amp Pcs assorted 10A 100V 9·00 Polarity 10A 200V 1·20 Stud Cathode or 10A 400V 1·20 Stud Anode Ideal for Power Supplies, Inverters, etc.

Transistors									
AC126	BC148	0-09*	BD137	0-48*	BFX87	0-29	OC84	0-40	2N3702
AC127	BC149	0-09*	BD138	0-48*	BFX88	0-29	OC139	0-60	2N3703
AC128	BC157	0-09*	BD139	0-58*	BFX89	0-99	OC140	1-39	2N3704
AC128K	BC158	0-09*	BD140	0-58*	BFY10	0-99	TIP29A	0-64*	2N3705
AC128K	BC159	0-09*	BD157	0-60	BFY18	0-59	TIP29A	0-64*	2N3706
AC141	BC167	0-09*	BD158	0-60	BFY50	0-40	TIP30	0-64*	2N3707
AC141K	BC168	0-09*	BD182	0-92	BFY51	0-40	TIP41A	0-54	2N3708
AC142	BC169	0-09*	BD183	0-92	BFY52	0-40	TIP42A	0-64*	2N3709
AC142K	BC169	0-12*	BD184	1-20	BFY51	0-18	TIP41A	0-68	2N3710
AC176	BC170	0-09*	BD233	0-68	BFY52	0-18	TIP42A	0-68	2N3711
AC176K	BC182	0-11*	BD233	0-48	BFY53	0-18	TIP47	0-80	2N3715
AC187	BC182L	0-11*	BD234	0-48	BFY90	2-00	TIP48	1-20	2N3716
AC187K	BC183	0-10*	BD238	0-60	BSW20	0-99	TIP49	1-20	2N3771
AC188	BC183L	0-11*	BD410	0-80	BSX19	0-16	TIP50	1-20	2N3772
AC188K	BC184	0-11*	BDX32	2-30	BSX20	0-18	TIP120	0-99	2N3773
AD140	BC184L	0-11*	BDY10	1-50	BSY27	0-39	TIP121	1-20	2N3819
AD161	BC185	0-20*	BDY11	2-00	BSY53	0-39	TIP122	1-20	2N3820
AD162	BC212	0-09*	BDY20	0-90	BSY54	0-39	TIP125	0-80	2N3823
AF115	BC207B	0-11*	BDY38	0-90	BSY55	0-74	TIP126	0-80	2N3866
AF116	BC208	0-09*	BDY60	1-79	BSY56	0-74	TIP127	0-80	2N3903
AF117	BC212L	0-11*	BDY61	1-95	BSY75	0-39	TIP130	0-80	2N3904
AF118	BC213	0-09*	BDY90	2-14	BSY76	0-39	TIP131	0-80	2N3905
AF124	BC213L	0-14*	BDY92	2-14	BSY77	0-39	TIP132	0-80	2N3906
AF125	BC214	0-09*	BF115	0-49	BSY78	0-39	TIP135	0-80	2N3925
AF126	BC214L	0-11*	BF179	0-30	BSY79	0-39	TIP136	0-80	2N3926
AF139	BC238	0-09*	BF180	0-39	BSY95A	0-18	TIP137	0-80	2N3927
AF239	BC300	0-34	BF181	0-39	BU105	3-95*	TIP140	1-20	2N3928
AL100	BC301	0-36	BF182	0-39	BU106	3-95*	TIP141	1-20	2N3929
AL102	BC302	0-49	BF183	0-39	BU126	1-60*	TIP142	1-20	2N3954
AU107	BC303	0-90	BF184	0-30	BU204	1-50*	TIP145	1-20	2N4058
AU110	BC307	0-15	BF185	0-29	BU204	1-50*	TIP146	1-20	2N4059
AU113	BC308	0-15	BF194	0-15	BU205	1-95*	TIP147	1-20	2N4060
BC107	BC317	0-09*	BF195	0-12*	BU206	2-45*	TIP150	1-20	2N4061
BC107B	BC318	0-13*	BF196	0-12*	BU207	2-45*	TIP151	1-20	2N4062
BC108	BC319	0-13*	BF197	0-12*	BU208	2-45*	TIP152	1-20	2N4284
BC108B	BC327	0-13*	BF200	0-49*	BU208A	2-45*	TIP2955	0-80	2N4285
BC109	BC328	0-13*	BF224	0-15*	BU406	1-50*	TIP3055	0-80	2N4286
BC109B	BC337	0-13*	BF244	0-15*	BU407	1-50*	TIP3439	1-20	2N4287
BC109C	BC338	0-13*	BF257	0-39	BU408	1-50*	TIP3440	1-20	2N4288
BC117	BC547	0-15*	BF258	0-39	BU426	1-50*	TIP3441	1-20	2N4289
BC118	BC548	0-15*	BF259	0-39	BU427	1-50*	TIP3442	1-20	2N4290
BC119	BC549	0-15*	BF337	0-39	BU428	1-50*	TIP3772	1-20	2N4291
BC120	BC550	0-15*	BF338	0-49	BU500	2-95*	TIP3773	1-20	2N4292
BC125	BC557	0-15*	BF339	0-49	BU501	2-95*	TIP3792	1-20	2N4293
BC126	BC558	0-15*	BF344	0-49	BU502	2-95*	TIP3794	1-20	2N4294
BC127	BC559	0-15*	BF345	0-49	BU503	2-95*	TIP3795	1-20	2N4295
BC128	BC560	0-15*	BF457	0-49	BU504	2-95*	TIP3796	1-20	2N4296
BC129	BC635	0-15*	BF458	0-49	BU505	2-95*	TIP3797	1-20	2N4297
BC130	BC636	0-15*	BF459	0-49	BU506	2-95*	TIP3798	1-20	2N4298
BC131	BC637	0-15*	BF469	0-49	BU507	2-95*	TIP3799	1-20	2N4299
BC132	BC638	0-15*	BF470	0-49	BU508	2-95*	TIP3800	1-20	2N4300
BC133	BC639	0-15*	BF471	0-49	BU509	2-95*	TIP3801	1-20	2N4301
BC134	BC640	0-15*	BF472	0-49	BU510	2-95*	TIP3802	1-20	2N4302
BC135	BC807	0-15*	BF473	0-49	BU511	2-95*	TIP3803	1-20	2N4303
BC136	BC808	0-15*	BF494	0-15	BU512	2-95*	TIP3804	1-20	2N4304
BC137	BC809	0-15*	BF495	0-15	BU513	2-95*	TIP3805	1-20	2N4305
BC138	BCY30	0-49*	BF496	0-15	BU514	2-95*	TIP3806	1-20	2N4306
BC139	BCY31	0-49*	BF597	0-29	BU515	2-95*	TIP3807	1-20	2N4307
BC140	BCY32	0-49*	BF598	0-29	BU516	2-95*	TIP3808	1-20	2N4308
BC141	BCY33	0-49*	BF599	0-29	BU517	2-95*	TIP3809	1-20	2N4309
BC142	BCY34	0-49*	BF600	0-29	BU518	2-95*	TIP3810	1-20	2N4310
BC143	BCY39	0-49*	BF613	0-29	BU519	2-95*	TIP3811	1-20	2N4311
BC147	BCY42	0-09*	BF614	0-29	BU520	2-95*	TIP3812	1-20	2N4312
BC148	BCY70	0-12*	BF615	0-29	BU521	2-95*	TIP3813	1-20	2N4313
BC149	BCY71	0-18*	BF616	0-29	BU522	2-95*	TIP3814	1-20	2N4314
BC157	BCY72	0-12*	BF617	0-29	BU523	2-95*	TIP3815	1-20	2N4315
BC158	BCZ11	0-39*	BF618	0-29	BU524	2-95*	TIP3816	1-20	2N4316
BC159	BD131	0-39*	BF619	0-29	BU525	2-95*	TIP3817	1-20	2N4317
BC160	BD132	0-39*	BF620	0-29	BU526	2-95*	TIP3818	1-20	2N4318
BC167	BD135	0-39*	BF621	0-29	BU527	2-95*	TIP3819	1-20	2N4319
BC168	BD136	0-39*	BF622	0-29	BU528	2-95*	TIP3820	1-20	2N4320
BC169	BD137	0-48*	BFX87	0-29	OC84	0-40	2N3702	0-10*	
BC170	BD138	0-48*	BFX88	0-29	OC139	0-60	2N3703	0-10*	
BC171	BD139	0-58*	BFX89	0-99	OC140	1-39	2N3704	0-10*	
BC182	BD140	0-58*	BFY10	0-99	TIP29A	0-64*	2N3705	0-10*	
BC183	BD157	0-60	BFY18	0-59	TIP29A	0-64*	2N3706	0-10*	
BC184	BD158	0-60	BFY50	0-40	TIP30	0-64*	2N3707	0-10*	
BC212	BD182	0-92	BFY51	0-40	TIP41A	0-54	2N3708	0-09*	
BC213	BD183	0-92	BFY52	0-40	TIP42A	0-64*	2N3709	0-09*	
BC214	BD184	1-20	BFY51	0-18	TIP41A	0-68	2N3710	0-09*	
BC237	BD233	0-68	BFY52	0-18	TIP42A	0-68	2N3711	0-10*	
BC238	BD233	0-48	BFY53	0-18	TIP47	0-80	2N3715	1-80	
BC239	BD234	0-48	BFY90	2-00	TIP48	1-20	2N3716	1-80	
BC250	BD238	0-60	BSW20	0-99	TIP49	1-20	2N3771	1-80	
BC251	BDX32	2-30	BSX19	0-16	TIP50	1-20	2N3772	1-90	
BC252	BDY10	1-50	BSX20	0-18	TIP120	0-99	2N3773	2-50	
BC253	BDY11	2-00	BSY27	0-39	TIP121	1-20	2N3819	0-25*	
BC258	BDY20	0-90	BSY53	0-39	TIP122	1-20	2N3820	0-50	
BC259	BDY38	0-90	BSY54	0-39	TIP125	0-80	2N3823	1-10	
BC267	BDY60	1-79	BSY55	0-74	TIP126	0-80	2N3866	1-29	
BC268	BDY61	1-95	BSY56	0-74	TIP127	0-80	2N3903	0-10*	
BC269	BDY90	2-14	BSY75	0-39	TIP130	0-80	2N3904	0-10*	
BC270	BDY92	2-14	BSY76	0-39	TIP131	0-80	2N3905	0-10*	
BC286	BF115	0-49	BSY77	0-39	TIP132	0-80	2N3906	0-10*	
BC287	BF179	0-30	BSY78	0-39	TIP135	0-80	2N3925	0-80	
BC288	BF180	0-39	BSY79	0-39	TIP136	0-80	2N3926	0-80	
BC297	BF181	0-39	BSY95A	0-18	TIP137	0-80	2N3927	0-80	
BC300	BF182	0-39	BU105	3-95*	TIP140	1-20	2N3928	0-80	
BC301	BF183	0-39	BU106	3-95*	TIP141	1-20	2N3929	0-80	
BC302	BF184	0-30	BU126	1-60*	TIP142	1-20	2N3954	0-80	
BC303	BF185	0-29	BU204	1-50*	TIP145	1-20	2N4058	0-09*	
BC307	BF194	0-15	BU204	1-50*	TIP146	1-20	2N4059	0-09*	
BC308	BF195	0-12*	BU205	1-95*	TIP147	1-20	2N4060	0-09*	
BC317	BF196	0-12*	BU206	2-45*	TIP150	1-20	2N4061	0-09*	
BC318	BF197	0-12*	BU207	2-45*	TIP151	1-20	2N4062	0-09*	
BC319	BF200	0-49*	BU208	2-45*	TIP152	1-20	2N4284	0-12*	
BC327	BF224	0-15*	BU208A	2-45*	TIP2955	0-80	2N4285	0-12*	
BC328	BF244	0-15*	BU406	1-50*	TIP3055	0-80	2N4286	0-12*	
BC337	BF257	0-39	BU407	1-50*	TIP3439	1-20	2N4287	0-12*	
BC338	BF258	0-39	BU408	1-50*	TIP3440	1-20	2N4288	0-12*	
BC347	BF259	0-39	BU426	1-50*	TIP3441	1-20	2N4289	0-12*	
BC348	BF337	0-39	BU427	1-50*	TIP3442	1-20	2N4290	0-12*	
BC349	BF338	0-49	BU428	1-50*	TIP3772	1-20	2N4291	0-12*	
BC350	BF339	0-49	BU500	2-95*	TIP3773	1-20	2N4292	0-12*	
BC351	BF344	0-49	BU501	2-95*	TIP3792	1-20	2N4293	0-12*	
BC352	BF345	0-49	BU502	2-95*	TIP3794	1-20	2N4294	0-12*	
BC353	BF457	0-49	BU503	2-95*	TIP3795	1-20	2N4295	0-12*	
BC354	BF458	0-49	BU504	2-95*	TIP3796	1-20	2N4296	0-12*	
BC355	BF459	0-49	BU505	2-95*	TIP3797	1-20	2N4297	0-12*	
BC360	BF469	0-49	BU506	2-95*	TIP3798	1-20	2N4298	0-12*	
BC361	BF470	0-49	BU507	2-95*	TIP3799	1-20	2N4299	0-12*	
BC362	BF471	0-49	BU508	2-95*	TIP3800	1-20	2N4300	0-12*	
BC363	BF472	0-49	BU509	2-95*	TIP3801	1-20	2N4301	0-12*	
BC364	BF473	0-49	BU510	2-95*	TIP3802	1-20	2N4302	0-12*	
BC365	BF494	0-15	BU511	2-95*	TIP3803	1-20	2N4303	0-12*	
BC366	BF495	0-15	BU512	2-95*	TIP3804	1-20	2N4304	0-12*	
BC367	BF496	0-15	BU513	2-95*	TIP3805	1-20	2N4305	0-12*	
BC368	BF597	0-29	BU514	2-95*	TIP3806	1-20	2N4306	0-12*	
BC369	BF598	0-29	BU515	2-95*	TIP3807	1-20	2N4307	0-12*	
BC370	BF599	0-29	BU516	2-95*	TIP3808	1-20	2N4308	0-12*	
BC371	BF600	0-29	BU517	2-95*	TIP3809	1-20	2N4309	0-12*	
BC372	BF613	0-29	BU518	2-95*	TIP3810	1-20	2N4310	0-12*	
BC373	BF614	0-29	BU519	2-95*	TIP3811	1-20	2N4311	0-12*	
BC374	BF615	0-29	BU520	2-95*	TIP3812	1-20	2N4312	0-12*	
BC375	BF616	0-29	BU521	2-95*	TIP3813	1-20	2N4313	0-12*	
BC376	BF617	0-29	BU522	2-95*	TIP3814	1-20	2N4314	0-12*	
BC377	BF618	0-29	BU523	2-95*	TIP3815	1-20	2N4315	0-12*	
BC378	BF619	0-29	BU524	2-95*	TIP3816	1-20	2N4316	0-12*	
BC379	BF620	0-29	BU525	2-95*	TIP3817	1-20	2N4317	0-12*	
BC380	BF621	0-29	BU526	2-95*	TIP3818	1-20	2N4318	0-12*	
BC381	BF622	0-29	BU527	2-95*	TIP3819	1-20	2N4319	0-12*	
BC382	BFX87	0-29	BU528	2-95*	TIP3820	1-20	2N4320	0-12*	

MEMORIES

2102A-4	3-99
2112A-4	4-75
2102	2-99
2102	2-99
2102	2-99
2102	2-99

TO3 NPN 20 amp Triple-tons similar to 2N3771/2/3

Untested but no shorts or opens

5 Pcs	2-99
10 Pcs	5-00
25 Pcs	7-50

CMOS PLASTIC

4000BE	0-20	
4001BE	0-20	
4002BE	0-20	
4006BE	0-80	
4007BE	0-20	
4008BE	0-80	
4009BE	0-40	
4010BE	0-40	
4011BE	0-20	
4012BE	0-20	
4013BE	0-50	
4015BE	0-95	
4016BE	0-50	
4017BE	0-54	
4018BE	0-90	
4019BE	0-50	
4020BE	1-03	
4021BE	1-03	
4022BE	0-95	
4023BE	0-20	
4024BE	0-62	
4025BE	0-20	
4026BE	1-32	
4027BE	0-50	
4028BE	0-80	
4029BE	0-90	
4030BE	0-50	
4031BE	2-50	
4032BE	0-90	
4033BE	1-50	
4034BE	1-32	
4035BE	0-95	
4036BE	2-50	
4037BE	0-90	
4038BE	0-90	
4039BE	2-50	
4040BE	0-90	
4041BE	0-90	
4042BE	0-62	
4043BE	0-90	
4044BE	0-62	
4045BE	1-32	
4046BE	1-32	
4047BE	0-90	
4048BE	0-50	
4049BE	0-50	
4050BE	0-50	

Sonic

HI-FI DISCOUNT CENTRES

DISCOUNT SPEAKERS

Imp 8 or 15Ω as app.

Guarantees!
TITAN 5 years
FANE 3 years
OTHERS 1 year

ALL PRICES INC. VAT

Prices correct at 18.7.77

HI-FI TYPES

	List/Value	Sonic Price
5" FANE 501 Mid or Full range	Sp. Price	£4·95
5" FANE 15W Various makes	Sp. Price	£4·95
6" A.P. Model 80 Dual Cone	Sp. Price	£5·95
8" A.P. Model 83 Dual Cone	Sp. Price	£6·95
FANE 805	Sp. Price	£5·95
FANE 804	Sp. Price	£4·95
FANE 801 Dual Cone	Sp. Price	£7·50
FANE 8" 808T Dual Cone	Sp. Price	£3·95
FANE 8" 8NTTF	Sp. Price	£4·95
WH*FEDALE LYTON 3XP kit Pr.	£92·64	£37·95
10" GLENDALE 3XP KIT	£135	£59·95
10" GLENDALE 3XP KIT	£75·62	£33·95
8" FANE PEARLONE 8T Sp. Price	£12·49	£9·95
10" ELAC Model 10RM	Sp. Price	£3·95
12" FANE [12/15]LA 30w	Sp. Price	£9·95
12" FANE 12Q/10 35w	Sp. Price	£9·95

GROUP/DISCO TYPES

12" FANE POP 15	Sp. Price	£4·99
12" FANE POP 25T 25–30w	Sp. Price	£7·95
12" TITAN T12/45 45w	£13·80	£10·95
12" TITAN T12/60A 60w	£21·90	£14·95
12" TITAN T12/100A 100w	£36·00	£32·95
12" CELESTION G12H 30w	£22·00	£18·95
12" CELESTION G12H 30w	£22·00	£19·95
12" CELESTION G12/80 50w	£28·00	£17·95
12" CELESTION G12/50TC	£28·00	£17·95
12" GOODMANS 12 PM	Sp. Price	£17·95
12" GOODMANS 12 PM	Sp. Price	£17·95
12" FANE "SPECIAL" P.A. 80	Sp. Price	£14·95
12" FANE DISCO 50	£22·75	£16·95
12" " " GUITAR 80L	£23·75	£18·95
12" " " GUITAR 80L	£23·75	£18·95
12" FANE CRESCENDO 12A	£57·35	£39·95
12" FANE " 12 BASS	£57·35	£39·95
12" FANE " 12 BASS	£56·70	£39·95
15" TITAN T15/45 45w	£26·00	£19·95
15" TITAN T15/70 70w	£38·00	£19·95
15" TITAN T15/100 100w	£47·00	£33·95
15" FANE "SPECIALIST" BASS 85	£39·95	£39·95
15" " " BASS 100	£42·00	£39·95
15" GOODMANS 15P	Sp. Price	£33·95
15" GOODMANS 15P	Sp. Price	£36·00
15" FANE CRESCENDO 15/100A	£72·95	£49·95
15" FANE CRESCENDO 15/100A	£72·95	£49·95
15" " " 15/100LT	£74·69	£49·95
15" " " COLOSSUS 200w	£97·95	£69·95
18" TITAN T18/100 100w	£47·00	£33·95
18" GOODMANS 18P	Sp. Price	£39·95
18" CELESTION G18C	£53·00	£39·95
18" FANE CRESCENDO 18A	£89·95	£69·95
18" FANE CRESCENDO BASS	£89·95	£69·95
18" " " COLOSSUS 400w	£139·00	£99·95

HORN UNITS (Carr. 75p)

CELESTION MH1000 25w	£17·00	£13·75
FANE 910 HL 70w	£17·75	£13·75
" 920 100w	£59·95	£39·95
" 1[3] 50 50w	£7·95	£5·95
" 1[3] 50w	£11·75	£8·95
" 1[3] 70w	£16·95	£12·95

HIGH POWER 'CROSS-OVERS'

FANE HPX1 or HPX2 Carr. 35p £2·99 £1·99

ADD-ON HIGH FREQUENCY UNITS

F.A.L. Tweeter/ Carr. £1	£34·50	£28·95
TITAN TH 70w Carr. £1	Sp. Price	£25·95
TITAN T1000 100w Carr. £1	Sp. Price	£39·95

HI-FI SPEAKER SYSTEMS Carr. £1·50 Pair

LEAK 3020	Pair £128·56	£84·95
LEAK 3050	Pair £159·00	£104·95
LEAK 3050	Pair £245·80	£162·95
VINNACOMBE DENTON 2XP	Pair £65·45	£43·95
LINTON 2XP	Pair £91·07	£59·95
CHEVIN 2XP	Pair £42·55	£30·95
GLENDALE 3XP	Pair £135·00	£59·95
DOVEDALE 5P	Pair £217·44	£151·95

Also for personal shoppers only

AMPS, T'TABLES, JINGLE MACHINES, DISCO CONSOLES, LIGHTING, CABINETS, CREDIT TERMS AVAILABLE orders £20

Phone orders accepted from Access & Barclay card holders

403 SAUCHIENHALL STREET Tel: 141 332 0700 — Branches at GLASGOW

24 NEWGATE SHOPPING CENTRE Tel: 0632 25168 — NEWCASTLE

106 NEWPORT ROAD Tel: 0642 217402 — MIDDLESBROUGH

Mail Orders & Export enquiries to Middlesbrough Branch. Add 50p carr. on Hi-Fi speakers or kits. Otherwise add 85p (12" spkr.) £1·25 (15") £2 (18")

enthusiasts and it is a pleasant duty to thank Mr. and Mrs. Owen of Dollgellan who took the trouble to take these speakers and other components to Bedford.

J. Hilditch of Nantwich has sent the basic brass tacks letter asking "how do I start DXing"? The answer to this is in two parts. The first is decide which sort of DXing takes your fancy, Latin American, North American, Asian, etc. Then, secondly, the thing to do is to decide which of the technical aspects of DXing interests you, aerials, receivers or perhaps it might be propagation. Having decided we can then move on to study these. This can be done by getting hold of a good set of leaflets on your chosen themes. Many stations offer these, generally free of charge, or at worst for the cost of return postage or a few IRCs. The best I know are distributed by Radio Nederland, PO Box 222, Hilversum, Holland, and are free. These leaflets will lead you on to thinking and planning your DX rather than random listening and hoping to catch that elusive station. After all, a fisherman who goes for a particular fish arranges his tackle to suit. It is no good trying for a special station when the darkness path does not suit or your aerial is all wrong!

Some DXers concentrate on collecting QSL cards and in order to do this a knowledge of how to write a letter in a foreign tongue may help and this perhaps will lead to a visit to a reference library. So it can be seen that every aspect of our hobby has a spin-off into some other activity.

With that I fear that I must close down and thank you all for your support and to the readers in all the overseas countries that took the trouble to write, I wish you good DX and best 73s to you and yours.

Reports on SW BC bands should now be sent to Charles Molloy, see box for details.

VHF BANDS

by Ron Ham BRS15744

Members of the Brighton And District Radio Society were sporting their Jubilee callsigns at the Peacehaven Carnival on June 6th where they gave the visitors an insight to amateur radio. Their 2m station, an FT221 and a 10-element Sky-Beam, installed on the balcony of the Youth Centre was operated periodically by Brian Fenwick GE8BTC, Nigel Hewitt GE8JFT and Alan Baker, GE8LGQ. The Sky-Beam, mounted on a 15ft mast above the balcony, had a mechanical rotator and an electronic beam-heading indicator.

Among the stations worked during the afternoon were F1DZP and a YL operator F1CSW. The group used their own PA system so that visitors could hear the VHF traffic, which took on a special interest when Alan left the station to give a mobile demonstration. A specially prepared leaflet about amateur radio, listing four local clubs, was given to interested people.

During the early hours of the 4th, GE8LGQ took advantage of a lift and worked PE, ON and F on 2m SSB and at 0330 he contacted GE8DJR the station installed at Windsor Castle. Alan worked 36 stations on 2m and the last one was F6DGU/MM operating a hand-held set on board the Newhaven Ferry 'Vilandry'.

The major sporadic-E disturbances of the 1977 season began on May 25 when strong signals from east-European FM broadcast stations were received between 65 and 73MHz on a dipole feeding my R216 receiver. Similar events, lasting a few hours occurred on May 27 and periodically each day from June 8 to 15th inc., and each time strong vision pulses on Ch.R1 (49·75MHz), warned of the forthcoming event. The frequency range 40 to 75MHz was open all day on the 9th reaching a climax around 1800 when I counted 42 east-European broadcast signals between 65 and 73MHz. However, the most intense disturbance so far occurred around 1800 on the 14th when I heard 46 of these broadcast stations, and for about an hour the sporadic-E extended it's influence to 2m giving G4FUT, G8LIC and G8LZM the opportunity to work YU, YO, HB, LZ and I0SVS in Rome. Sporadic-E upset Band II during the evening of the 7th and 8th, according to **Ken Smith** BRS20001 Horsham, who heard several continental FM signals between 95 and 100MHz. Ken's report was soon followed by a postcard from "dampest Devon" where **John Wilson** G8KIS and **Richard Lambley** G8LAM were on holiday with their families. Richard wrote "We were listening to North Hessary Tor (R4) on my Beolit 600 portable about 1700GMT when the set started being 'captured' by German speaking stations. The whole band was alive with Austrian, Italian and Yugoslav stations until 1800 when it went flat again; all at ground level with a whip aerial and heavy local screening".

Almost every day from May 26th to June 19th there was activity on 10m. **Nigel Golds** BRS36910 West Chiltington, Sussex heard South-American stations on the 5th in addition to the short skip signals from Scandinavia to Africa which were predominant on most days. Like many of us, Nigel looked first for the International Beacon Project stations hearing 5B4CY on June 1st and 2nd and strong signals from DL0IGI for some period every day. **Alan Baker** G8LGQ Newhaven, heard the German beacon around midnight on several occasions and on the 8th he just heard the Canadian beacon VE3TEN.

To add to the fun, the sun went "active" on the 4th, **Cmdr. Henry Hatfield,** Sevenoaks, using his spectroheliioscope, found a sunspot group in the northern hemisphere, a bright plage in the southern hemisphere and a spray of gas on the east limb. Although overcast skies hampered visual observation, **Robert Mackenzie,** Dover, who projects the sun's image through his telescope, saw the sunspot group on the 8th. **John Smith,** Cranleigh, reported a marked increase in solar radio noise at 142MHz on the 5th and G8LGQ heard the "seashore" sound on both 2m and 10m indicating the wide frequency coverage of some of the solar bursts.

Both Henry and myself recorded several bursts and a mild solar noise storm at 136MHz on June 5th, 7th, 8th and 9th and the largest individual burst occurred on the 9th and lasted for six minutes. I hope to have reports soon from **Kelvin Lake,** Edgbaston, Birmingham, who, with the aid of a friend, has just completed a corner reflector interferometer, with a 25 wavelength baseline, operating at 143MHz, for radio astronomy work.

The prevailing high atmospheric pressure, 30·4″ began to fall on June 2nd and 3rd causing a tropo-opening toward the north; during this period I received a 569 signal from GB3SUT 432·890MHz, a picture from Lichfield on 189MHz, and several con-

tinental FM stations in Band II with a dipole feeding the receivers in each case. Another tropo-opening began during the evening of the 16th and **Barry Ainsworth** G8HYN Sompting, Sussex, worked PA0's, F's and GU4EON/M on 2m SSB and at 2330 he contacted G8HVY in Weymouth on 70cms. At the same time, I heard 8 continental FM stations in Band II and a PA0 working EI on 2m. GB5SUT came up at 2130 and was frequently heard in Sussex until the small hours of the 20th. During the afternoon of the 19th G8LGQ had a contact with G2BAR in Bristol and at 1816 he worked GW4FPX/P in Gwent. As if these were not enough to satisfy a VHF man's ego for one day, Alan heard a very weak GM pop up from the noise around 2000 and he stuck on that frequency until 2315 when, for the first time from his home in Newhaven, he worked GM6UW/P just north of Aberdeen, a distance of 560 miles which is not bad going on 2m!

Owing to the prevailing sporadic-E disturbance to the 4m band I was unable to make a satisfactory observation of the June Lyrid meteor shower which reached it's peak on the 15th. However, the next event to look out for are the Perseids which reach their maximum on August 12th. I would also like to remind you all about the 4m Open Contest on August 13th/14th and the 2m Open Contest on September 3rd/4th and in both events SWLs are welcome to take part.

Ivan Davies G3IZD took advantage of the good conditions and worked OZ1OQ and ON6AG on 2m SSB, from Arundel, Sussex during the evening mobile rally organised by Worthing and District ARC on June 21st. Among the visitors to the rally was Ernie Hoare G8BDJ from Brighton who learned recently that he was the winner of the 3cm section of the IARU Region 1 contest held last October. Ernie told me that he hopes to get going on 24GHz soon.

Thanks again to all of you who send me reports, I really do look forward to hearing from you and putting this feature together.

Reports on the various bands are welcome and should be sent direct, by the 15th of the month, to:-

AMATEUR BANDS Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashtead, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

MEDIUM and SW BANDS Charles Molloy G8BUS, 132 Segars Lane, Southport, PR8 3JG. Reports for both bands **must** be kept separate.

VHF BANDS Ron Ham BRS15744, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

Amateur Bands—continued

You won't be able to make the next meeting of the Wessex AR Group, on 5 August, because it's too late! But because it will be a very interesting talk perhaps G6MB and G4AMW might consider repeating it, if you ask them nicely! Title is 'Problems encountered in building and operating HF transceivers using the SL600 IC's. You will be able to make the following date on 19 August when Power Supply Units will be discussed followed by a talk on studying for the RAE. Details from Geoff Cole G4EMN, 6 St. Anthonys Road, Bournemouth (Tel: 20027).

Careers and Hobbies in Electronics.

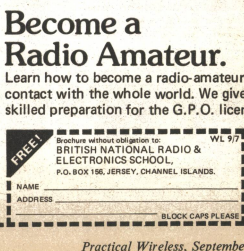

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

FREE! Brochure without obligation to: WL 9/7
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,
P.O. BOX 156, JERSEY, CHANNEL ISLANDS.

NAME _____

ADDRESS _____

_____ BLOCK CAPS PLEASE

RETURN OF POST MAIL-ORDER SERVICE

R.C.S. 100 watt MIXER/AMPLIFIER ALL VALVE CHASSIS

Four inputs. Four way mixing, master volume, treble and bass controls. Suits all purposes. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Send for details.

Suitable carrying cabinet £14. Price £85 carr. £2-50

ANOTHER R.C.S. BARGAIN !

ELAC 9 + 5in. HI-FI SPEAKER TYPE 59BM

This famous unit now available, 10 watts, 8 ohm.

Price £3-45 Post 40p

10" ELAC HI-FI SPEAKER

Large ceramic magnet.
Response: 50-10,000 cps.
Bass resonance 65 cps.
16 ohm impedance 10 watts. Post 50p £4-50

TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 × 13 × 12in. For 10in. dia. or 12in speaker. Illustrated. 14-50 Post £1-00

MODEL "B" BOOKSHELF. For 12 × 8in. speaker. 8-50 Post £1

R.C.S. BOOKSHELF SPEAKERS
Size 14in. × 9in. × 6in. approx. Response 50 to 14,000 cps. 8 watts 8 ohms. £16 pair Post £1-50

LOUDSPEAKER CABINET WADDING 1Min. wide, 50p yd.

GOODMANS CONE TWEETER

3in. diam. 18,000 C.P.S. 8S WATTS 8 Ω
Sin. Audax 15 watts 84-96. 3in. Sin. Mail order only. £3-25

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical bits/bights and sound effects to recordings. Use mic Microphone, records, tape and tuner with mains controls into mixer output. 9 volt battery operated. £6-75

TWO CHANNEL STEREO VERSION OF ABOVE £9-50

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated or Mains Supply £3-95.

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER
Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. Leaflet S.A.E. £4-95 Post 75p

WAFER T741M HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, workshop, warehouse, factory (available in manufacturing quantities). Approx. size 10½ × 8½ × ¼in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely safe providing safe Mains heat. Britain-made for use in photo-copiers and print drying equipment.

Ideal for home handyman and experimenters. Suitable for Heating Pads, Food Warmers, Incubators, Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc. etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1-50)

ALL POST PAID—Discount for quantity.

CASSETTE RECORDER MOTOR ONLY. 6 Volt. Will replace many types. Ideal for models. £1-25.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. Sin. sides 6 × 4in. 70p; 8 × 6in. 90p; 10 × 7in. £1-15; 14 × 9in. £1-60, 18 × 9in. £1-65; 18 × 5in. 97p; 18 × 10in. £1-70. All sizes in many sizes in stock.

DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in. 10in. or 7in. records
Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13½ × 11¼in. Above motor board 3½in. Below motor board 5½in. £17-50

With STEREO/MONO CARTRIDGE Single Player versions £13-50. All Post 75p
GARRARD MINICHANGER Size 13 × 9in. £9-95
BSR P126 with Ceramic Cartridge £19-50

BAKER MAJOR 12" £15-00

Post £1

90-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s rated 25 watts. NOTE: 4 or 9 or 16 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. Please state 4 or 9 or 16 ohms. Post £1 00 £19-00

BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups.
Useful response 30-13,000 cps.
Bass resonance 50 cps.

GROUP "25"
12in. 30 watt 4, 8 or 16 ohms. Post £1 £12-00

GROUP "35"
12in. 40 watt 4, 8 or 16 ohms. Post £1 £14-00

GROUP "50/12"
12in. 60 watt professional model. 3 ohms or 16 ohms. With aluminium presence dome. Post £1-00 £21-00

GROUP "50/15"
15in. 75 watt 8 or 16 ohms. Post £1-00 £26-00

Send for leaflets on Disco, P.A. and Group Gear.

BAKER 150 WATT QUALITY TRANSISTOR MIXER/AMPLIFIER

Professional amplifier using advanced circuit design. Ideal for disco, groups, P.A., or musical instruments. 4 inputs 4 way mixing. Master volume, bass and volume controls. 2 speaker output sockets to suit various combinations of speakers. 4-8-16 ohm. Slave output. A/C mains. Guard installed. Details S.A.E. 150w SLAVE VERSION £80.

Latest 50 watt Model £49 £72 Carr. £1-00

100 WATT DISCO AMPLIFIER CHASSIS

MADE BY JENNINGS MUSICAL INSTRUMENTS £52
4 speaker outputs, vol., treble, bass controls
CAN BE USED AS 100 WATT GUITAR AMP. Carr. £1

B.S.R. SINGLE PLAYER DECK

3 speed. Plays all size records, Stereo Ceramic. Cueing device. Ideal Disco Deck.

£13-50 Post 75p

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Will control up to 500 watts AC mains. Post 35p £2-25

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3½ watts for high medium or low gain per channel, with volume control and P.C. board. Can be ganged to make multi-way stereo mixers. Post 35p £7-95

P.W. SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three channels. 600 to 1,000 watts each.
As featured in Practical Wireless.
Cabinet extra £8. Price £14-00

8 inch PHILIPS LOUDSPEAKER

4 ohm, 6 watt ceramic magnet.
General purpose replacement unit. £1-95

MAINS TRANSFORMERS Post 50p

6 VOLT ½ AMP. £1-00 3 AMP. £1-40
12 VOLT 300 MA. £1-00 750 MA. £1-20
30 VOLT 5 AMP. 240 V. 34 VOLT 2 AMP. C.T. £3-45
20 VOLT 1 AMP. 42-0-42 3 AMP. £2-20 0-5-20 VOLT 1 AMP. £2-95
30 VOLT 1 AMP. 42-0-42 4 VOLT 2 AMP. £2-95 0-30-40-50 VOLT 1 AMP. £2-60 9 × 18 VOLT 6 AMP. £11.

PERIOD LOUDSPEAKER CABINETS

Two styles available, Regency and Queen Anne. Size approximately 34 × 19 × 16in. Then cabinets are slightly soiled and are priced from £19 each. Callers only.

R.C.S. BOOKSHELF SPEAKERS

12 × 10 × 6in.
50 to 14,000 cps.
8 watts rms. 8 ohms

£16 pair Post £1-50

BAKER DISCO SPEAKERS

HIGH QUALITY—BRITISH MADE

2 × 12" CABINETS

Tor Disco or PA all fitted with carrying handles and corners. Black vynide covered. Other cabinets in stock. SAE for leaflet

50 WATT R.M.S. £52 Carr. £3

70 WATT R.M.S. £56 Carr. £3

100 WATT R.M.S. £69 Carr. £4

1 × 15" + 1 × 12" 100 WATT CABINET
Size 36" × 24" × 15" £75-00. Carr. £5
Ideal for Disco, Organ or PA work.
High quality. Full range.

"SUPERB HI-FI" 12in 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance	35cps
Flux Density	16,500 gauss
Useful response	30-17,000cps

8 or 16 ohms models.

£22-00 Post £1-00

"AUDITORIUM" 12in. 35 watts

A full range reproducer for high power. Ideal for Hi-Fi and Discotheques. Electric Guitars, public address, multi-speaker systems, electric organs.

Bass Resonance	30cps
Flux Density	15,000 gauss
Useful response	28-16,000cps

8 or 16 ohms models.

£21-00 Post £1-00

"AUDITORIUM" 15in. 45 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home Hi-Fi.

Bass Resonance	35cps
Flux Density	15,000 gauss
Useful response	30-14,000cps

8 or 16 ohms models.

£26-00 Post £1-00

Loudspeaker Cabinet Wadding 1Min wide, 50p per ft.

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cube tables, 60p.

E.M.I. 13½ × 8in SPEAKER SALE!

With tweeter. And crossover. 15W. Rich 5 or 8 ohm. As illustrated. £7.95 Post 45p

15W model £10-50 8 ohms. Post 65p

20W model £11.50 4 or 8 or 15 ohms. Post 65p

RADIO COMPONENT SPECIALISTS

Minimum post 30p. Components List 10p. Cash price includes VAT. Access & Barclay cards welcome. Rail Saltburst. Tel. 01-684 1665

337 WHITEHORSE ROAD, CROYDON

Open 9—6 Wed. 9—1 Sat. 9—5 (Closed for lunch 1.15—2.30)

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. at 12½% **Telephone 6743**

OA2	-65	6AM8A	.70	6P38	-65	7B7	2-00	14H7	.75	80CD6G	
OB2	-60	6AN8	.70	6P54	.90	7Y7	2-00	14R7	1-00		
OC3	-60	6AQ5	.60	6P55	.90	7Z4	.60	50H8	.65		
OZ4	-45	6AQ8	.80	6P28	.90	7Z4	.60	19AQ8	.80		
1A5GT	-65	6AT6	1-00	6QF8A	.80	9D6	1-00	20D6G	.80		
1A6GT	-65	6AT6	1-00	6QF8	.80	9D6A	1-00	75	.70		
1A7GT	-65	6AT6	1-00	6QF8A	.80	9D6	1-00	75	.70		
1B3GT	-65	6AV6	.60	6QK5	.70	9U8	.95	19T8	.80		
1D5	1-00	6AW6	.64	6QR7	.70	9U11	.70	20P4	.70		
1G6GT	1-00	6AX4	.75	6H6GT	.90	10C12	.60	20D4	2-00		
1R5GT	-65	6BA6	.70	6J5	.60	10C1	.60	20L1	.80		
1L4	-65	6BA8	.60	6J6	.65	10D2	.60	20L1	1-00		
1L5G	-65	6BE6	.60	6J7G	.70	10F1	1-00	20P1	1-00		
1LN5	.70	6BE6	.60	6J7M	.65	10F9	.65	20P3	1-00		
1N5GT	.75	6BG6G	1-50	6J7GT	.65	10P13	.70	20P9	1-00		
1S5	-60	6BH6	.70	6K7G	.65	10L14	.65	20P5	1-00		
1S4	-65	6BJ6A	.60	6K8G	.75	10LD3	.65	20P9	1-00		
1S5	-65	6BK7A	.65	6K8GT	.65	10LD13	.65	20L6G	.70		
1T4	-60	6BN6	1-00	6K8M	.65	10LD20	.65	20L6	.70		
1U4	.70	6BQ5	.65	6L6GC	.85	10P13	.65	20T6G	.65		
1U5	.70	6BR7	.65	6L7	.65	10P14	.70	20T6	.65		
2D21	-65	6BR7	1-00	6L6	.85	12A5	.65	20Z5	.70		
5U4G	.75	6BZ6	1-00	6L6G	.85	12A6	.65	20Z6G	.70		
5X3	.70	6BZ7	2-00	6L19	2-00	12AD6	.60	20Z7	2-00		
5Y3	.60	6BW6	1-70	6L20	2-00	12AE6	.60	20A5	.75		
5Y3	-65	6BW7	.65	6LD20	.65	12AT6	.64	20C1	.65		
5Y4G	.60	6C4	.60	6P1	.65	12AT7	.75	20C1	.65		
5Z4	.60	6BT7	.80	6P9	.65	12AU6	.64	20C1	.65		
5Z4GT	.60	6BT7	.80	6P13	.65	12AU7	.75	20C1	.65		
6B4	.60	6C4	.60	6Q7G	.60	12AV6	.64	20C1	.65		
6B8	.70	6C6	.60	6Q7GT	.60	12AX7	.64	20C1	.65		
6C8G	.75	6C8	.80	6Q7GM	.60	12AY7	.64	20C1	.65		
6C9	.70	6C9	2-00	6R7G	.60	12BA6	.60	20C1	.65		
6C10	.70	6C10	.70	6R7GT	.60	12BE6	.60	20C1	.65		
6C6G	1-00	6C8GA	.60	6S7GT	.75	12BH7	.65	20C1	.65		
6F6	.60	6C8G	.60	6S8GT	.75	12BR7	.65	20C1	.65		
6F6A	1-00	6CD6G	1-00	6SH7	.65	13D1	2-00	20C1	.65		
6F6G	.60	6CH6	.60	6SJ7	.65	13D2	2-00	20C1	.65		
6F6GT	.60	6CL6	.75	6SK7GT	.65	13T7GT	.70	20C1	.65		
6F8	.65	6CM6	1-00	6SL7	.65	13T8GT	.70	20C1	.65		
6F8G	.65	6CM7	1-00	6U4GT	.65	15CW5	.70	20C1	.65		
6F8GT	.65	6CM8	.65	6U7G	.65	15CW8	.70	20C1	.65		
6J8G1	.70	6CU5	.90	6U8	.65	19Q2GT	.60	20C1	.65		
6A8G	1-00	6CU6	.60	6V6G	.60	19AE3	.70	20C1	.65		
6AC7	.65	6D3T	.90	6V6GT	1-00	19AQ5	.70	20C1	.65		
6AC7	.65	6D6G	.60	6V6M	.65	19BG6G	.80	20C1	.65		
6AG7	.60	6EW6	.65	6X5GT	.65	19H1	1-00	20C1	.65		
6AH6	.60	6F1	.65	6X8G	.65	19J6	.70	20C1	.65		
6AJ8	.70	6F2	.60	6Y7G	1-65	19K7	.60	20C1	.65		
6AK5	.65	6F12	.60	6Y7M	.65	19K8	.60	20C1	.65		
6AK5	.65	6F13	.60	7A6	.60	19T8	.78	35Z4GT	.70		
6AK5	.65	6F15	.60	7B6	.60	19TY4	.70	35Z5GT	.70		
6AK5	.65	6F15	.60	7D6	2-00	19BQ7G	.65	1-00			
6AK5	.65	6F15	.60	7D8	2-00		.65	1-00			
6AL5	.65	6F23	.75	7Y4	.60						
6AM5	.60	6F24	1-00	12BH7	.78	80CG	.70				

DAC32	-60	ECH3	1-00	EL37	3-00	KT71	1-00	PEN46B2D	UF85	-60	AAZ18 -91	HF178 -44
DAF91	-65	ECH4	1-00	EL41	-67	KT81	2-00	UF89	-60	AC107 -18	HF180 -60
DAF96	-60	ECH4	1-00	EL81	-70	KT88	2-00	PENDD-		AC113 -18	HF181 -44
DC90	-70	ECH35	-65	EL83	-70	KTW61	1-00	4050 1-00		AC126 -14	HF185 -47
DD4	-60	ECH35	-65	EL84	-65			PFL200	-70	UM80 -60	AC127 -18	HF186 -47
DF33	-75	ECH42	-65	EL86	-60	KTW62	1-00	PL33 1-00		UY41 -60	AC128 -18	HF187 -44
DF91	-60	EF37	-65	EL90	-60			PL36	-85	U10 -60	AC130 -18	HF188 -44
DF92	-65	ECC32	1-00	EL95	-67	KTW63	1-00	PL81	-60	U19 1-00	AC132 -18	HF189 -44
DH76	-60	ECC33	2-00	EL360	1-80			PL82	-57	U14 1-00	AC136 -28	HF114 -61
DH63	-60	ECC35	2-00	EL500	1-50	L63	-65	PL83	-67	U16 -60	AC137 -18	HF115 -61
DH77	-60	ECC81	-64	EM80	-65	LN119	-65	PL95	-67	U19 1-00	AC162 -30	HF117 -61
DH77	-60	ECC82	-64	EM81	-65	LN122	-65	PL504	-90	U25 -60	AC168 -44	HF211 -60
DK32	-60	ECC83	-64	EM84	-65	LN309	-65			U26 1-00	AC170 -44	HF212 -60
DK91	-60	ECC84	-64	EM85	-65	LN319	1-00	PL504/90	-90	U35 1-70	AC177 -60	HF213 -60
DK92	-60	ECC85	-64	EM87	1-00	MH4	1-00	PL508 1-00		U37 -60	AC178 -60	HF214 -60
DK96	-60	ECC86	1-00	EM88	1-00	MH4D	1-00	PL509 2-00		U81 -60	AC718 -23	HF241A 1-00
DL33	-60	ECC88	1-00	EM89	1-00	ML6	1-00	PL519 1-00		U191 -60	AC719 -23	HF242 -60
DL35	-60	ECF1	-85	EM91	-85	MS4B	1-00	PY80	-60	U281 1-00	ACT20 -30	OA47 -18
DL63	-70	ECH3	-58			MS/PEN	3-00	PY81	-60	U301 1-00	ACT22 -30	OA70 -18
DL64	-70	ECH4	1-00	EY51	-65	MXT4	1-00	PY82	-60	U403 -60	ACT23 -18	OA79 -18
DL92	-65	ECH21	1-00	EY86	-65	MYT4	1-35	PY83	-65	U404 -60	ACT25 -18	OA81 -18
DL94	-60	ECH35	-65	ECH81	-70	EY91	-65	PY88	-65	U801 -60	AD140 -60	OA85 -11
DL95	-60	ECH42	-65	ECH83	-70	EY500A	-75	PY500	-85	U4020 -60	AD149 -60	OA90 -11
DL96	-60	ECL80	-70	ECL82	-70	EZ40	-60	PY500A	-85	UF28 -65	AD162 -53	OA95 -60
DM70	-60	ECL82	-70	ECL83	-70	EZ41	-60	PY500A1	-85	UF41 -60	AF100 -60	OA200 -11
DM71	-60	ECL86	-70	ECL85	-70	EZ80	-60	PY800	-60	UF42 -60	AF114 -60	OA202 -11
DW2	-60	EF36	-65	ECL86	-70	EZ81	-60	PY801	-60	UF80 -60	AF115 -60	OA210 -11
DW4	-60	EF37A	-65	ECL86	-70	EZ90	-60	PY802	-60	UF85 -60	AF116 -60	OA211 -11
DY86	-60	EF39	-65	ECL86	-70	EZ91	-60	PY803	-60	UF89 -60	AF117 -60	OA212 -11
DY87	-60	EF40	-65	ECL86	-70	EZ92	-60	PY804	-60	UF92 -60	AF118 -60	OA214 -11
DY802	-60	EF41	-65	ECL86	-70	EZ93	-60	PY81/90	-60	UF93 -60	AF121 -60	OA215 -11
E88C	-60	EF42	-65	ECL86	-70	EZ94	-60	PY82/90	-60	UF94 -60	AF124 -60	OA216 -11
E88CC	-60	EF50	-65	ECL86	-70	EZ95	-60	PY83/90	-60	UF95 -60	AF125 -60	OA217 -11
E88CC	-60	EF50	-65	ECL86	-70	EZ96	-60	PY88/90	-60	UF96 -60	AF126 -60	OA218 -11
E90CC	-70	EF50	-65	ECL86	-70	EZ97	-60	PY500/90	-90	UF97 -60	AF127 -60	OA219 -11
E90CC	-70	EF50	-65	ECL86	-70	EZ98	-60	PY500A/90	-90	UF98 -60	AF128 -60	OA220 -11
E90CC	-70	EF50	-65	ECL86	-70	EZ99	-60	PY801/90	-60	UF183 -60	AF129 -60	OA221 -11
E90CC	-70	EF50	-65	ECL86	-70	EZ100	-60	PY802/90	-60	UF184 -60	AF130 -60	OA222 -11
E90CC	-70	EF50	-65	ECL86	-70	EZ101	-60	PY803/90	-60	UF185 -60

4½in × 3½in METER. 30μA, 50μA or 100μA, £4·78. P. & P. 19p.

42 × 42mm METERS
1mA, 10mA, 100mA, 500mA, £3·97, 11p P. & P.

60 × 45mm METERS
50μA, 100μA, 500μA and 1mA **VU METER** £4·13, 13p P. & P.

EDGEWISE METERS
90mm x 34mm, 1mA £3·40, 19p P. & P.

MICROPHONES FOR TAPE RECORDERS

DM228R 200 ohm with 3·5 & 2·5mm Jack Plugs £1·30
DM229R 50K with 3·5 & 2·5mm Jack Plugs £1·60
DH18ZD 200 ohm with 5 & 3 pin DIN plug £1·75
Postage on above microphones 11p.

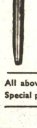

CARDIOID DYNAMIC MICROPHONES

Model UD-130. Frequency response 50–15,000c/s. Impedance Dual 50K and 600 ohms, £7·58. P. & P. 35p.

MULTI-METER

Model ITI-2
20,000 ohm/volt, £10·05.
P.&P. 33p.

TRANSFORMERS
Primary 240V

6–0–6V	100mA	£0·75
9–0–9V	75mA	£0·75
12–0–12V	50mA	£0·85
12–0–12V	100mA	£1·05

Post on above transformers 30p.

9–0–9V	1A	£1·80
12–0–12V	1A	£2·15
15–0–15V	1A	£2·34
30–0–30V	1A	£3·10
6·3V	1¼A	£1·80
6–0–6V	1¼A	£2·20

Post on above transformers 45p.

All above prices include V.A.T. LARGE S.A.E. for NEW LIST
Special prices for quantity quoted on request.

M. DZIUBAS
158 Bradshawgate · Bolton · Lancs. BL2 1BA

When you make your own PCB's, you need Seno Etch-Resist Transfer Symbols!

High definition, etch resist transfers that adhere perfectly to copper-clad board, offering a superb professional finish to the one-off PCB. Ten types of symbol, in strip form for greater accuracy. Packs of ten strips, mixed, or of any one symbol, for only 12!

From your usual component supplier or direct. Send in the coupon below for details of the Seno / 33 range of aids to PCB preparation

Decon Laboratories Ltd. Freepost, Portslade, Brighton BN4 1EQ (no stamp needed)

Name: _____

Address _____

Phone 0273-414371

Deteckknowledgey

Deteckknowledgey - the survey of metal locator theory and principles of operation. £1 post paid.

Bionic Ferret 4000 - the VCO system detector with Fe/NonFe discrimination, metej, loudspeaker, low power drain and high sensitivity. Price now reduced due to volume of demand to £34.26 (inc PP & VAT)
More details in catalogue - demonstrations available

TOKO MFL455 Sideband Mechanical Filter:
SSB filter with 2.1kHz 6dB BW. By popular demand, we now offer this superbly smooth sideband filter - designed for receiver or generator applications. With input/output matching transformers: only £9.95.
Convert our EF5801 to an ultra hi-gain 2m converter: Crystal locked oscillator - details SAE pl ease .

Radio Control and Short Wave Coils

Ambit is pleased to announce the addition of sets of specially designed TOKO coils for applications in model radio control and shortwave receivers, to our unique range of coils and filters.

7E High stability IFs for 455-470kHz, 1st, 2nd and 3rd IFs in three basic impedance ranges. 33p each unit or 75p per set of three. Full details in catalogue.
7KN High stability RF coils for 27MHz band. Spiral wound units with tap and secondary windings. 33p each.
10K Coils for short wave, new leaflet available, or see catalogue.

New modular Elektrick Wireless

7122 -A three stage tuned superhet AM radio module, with 80dB AGC, varicap tuning, ceramic IF filter, meter output. For LW, MW, and now short wave - with the correct coil pack. Not band switched, but using a separate module for each desired band. Better than 10uV sensitivity, and a new easy DIY approach to radio building. SAE for full info. Each module (inc. varicaps and coil pack) £9.00 +kit.
91198 -A three stage tuned AM/NBFM receiver module, being a refined version of above, with mechanical IF, MOSFET RF, NBFM discriminator (for afc), audio notch filter, separate oscillator, provision for 'pi' network input stu (with varicaps). Again, not bandswitchable, so as to optimize each module for its specific tuning range. Kit £15.75 each.

Components as previously advertized, including

CA3089	1.94	EF5800 6cct tunerhead FM	14.00
MC1310	2.20	EF5801 as 5800 with osc as	7.45
TBA120	0.75	EC3302 3cct varicap tunerhead	7.50
TBA120S	1.80	7030 linear phase IF system	10.95
UA753	1.80	91196 top spec decoder	12.99
HA1137	2.20	9310 1310 decoder & filter	5.95
HA1196	3.75	91197 varicap MW/LW tuner	13.35
uA720	1.40	7252 LARSHOLT FM tunerset for	
TBA651	1.81	mono with mosfet head	26.50
HA1197	1.40	7253 FET stereo tunerset	26.50
LM380	1.00		
LM381	1.81	**FAMOUS TOKO COILS/FILTERS**	
LM3900*	0.75	10mm IFTs 1st, 2nd or 3rd for	
TDA2020	2.99	455-470kHz	30p
TCA940	1.80	10mm IFTs for FM and detectors	
TBA810S	1.09	such as CA3089E	33p
ICL8038C	4.50	7mm IFTs for radio control	33p
NE561B*	3.50	CFU series ceramic 470kHz	55p
NE566V*	2.50	CFT series ceramic 455/470	55p
NE567*	2.50	MFHT series mechanical 455	1.95
uA723*	0.80	MFHK series mechanical filters for	
MEM616	0.57	455kHz now stocked	1.65
MEM680	*0.75	CFSE/SFE10.7 FM ceramics	0.50
BF256S	0.34	BR3132 FM linear phase	2.25
MVAM series		BLR3107N stereo 19/38kHz	1.90
2	1.35	SFE455 and SFD470	0.75
115	0.95	SFE6.0MA TV SiF	0.80
125	0.90	NEW comprehensive choke range	
BB104	0.45	1uH to 100mH see list in catalogue	

We would like to say more, but space has run out. Please remember p&p (25p) and VAT (12½% except where *) The catalogue has much new info since April. The new sheets will be sent on receipt of an A4 SAE. Or 40p for the complete catalogue and information package. SAE with ALL enquiries please. Callers welcome.

AMBIT INTERNATIONAL wireless specialists
37 High Street, Brentwood, Essex. CM14 4RH
telephone (0277) 216029

SUPER TOUCH—SENSITIVE PIANO

We have shown our special brand of skill and expertise in designing this piano, featuring:—
Wide range of touch-sensitive response ESU design. Free from breakthrough noise.
Choice of keyboard C-C or F-F.
Two models are available. Model TS50 is a touch-sensitive piano only. Model TS53 has extra effects of Honky-tonk, Harpsichord with fast and slow tremolo.

KIT SECTION PRICE LIST

ESU5 + 5 Keyer Units **£11·95** each, 5 required.
ESU5 + 6 Keyer Unit **£13·95**, 1 required.
Power Supply **£9·50**
Keyboard and Switches **£33·00**
Toneforming, Headphone and Voltage Regulator **£14·50**
Loud and Soft Pedal **£7·95**
Master Tone Generator **£15·00**
Tremolo Unit **£3·75**
Cabinet switches, etc. **£32·50**

SPECIAL OFFER
We will pay VAT and carriage on all orders received up to 31st October.

Can you afford £750 for an electronic piano? If the answer is NO why not visit our showroom and try our electronic pianos, discuss the technicalities in detail without obligation.

WE GUARANTEE TO SAVE YOU MONEY. IT IS SIMPLE ONCE YOU KNOW HOW.

Component shop: 40a Dalston Lane, Dalston Junction, E8 2AZ. Tel. 01-249 5624.

Parts for organ builders

4-Octave C-C keyboard	**£26·00**
5-Octave C-C keyboard	**£28·00**
5-Octave F-F keyboard	**£28·95**
13 note pedal board	**£25·00**
25 note pedal board	**£55·00**
32 note pedal board	**£115·00**
stop switches	**75p**

Tone Generator Units

GD500/5 with 73 outputs	**£39·95**
GD500/8 with 85 outputs	**£48·50**
GD500/12 with 96 outputs	**£52·50**

Diode Gate Sustain and Distribution Units

4-Octave with 3 pitches	**£32·00**
4-Octave with 4 pitches	**£38·00**
5-Octave with 3 pitches	**£33·00**
5-Octave with 5 pitches	**£60·00**
5-Octave with 6 pitches	**£65·00**
4-Octave with 9 pitches	**£88·00**
5-Octave with 9 pitches	**£96·00**

Toneforming Units

3 pitches with 10 voices	**£24·00**
4 pitches with 10 voices	**£26·00**
4 pitches with 15 voices	**£27·50**
5 pitches with 10 voices	**£38·40**
6 pitches with 19 voices	**£65·95**
9 pitches with 10 voices	**£40·50**

Rotating Speaker Units

Bass unit	**£68·00**
Mid Range	**£75·00**
Hi-Fi Horn	**£89·00**

Other useful components in stock for organ work.
Send 50p plus 20p p. & p. for the new monthly magazine 'Electronic Organ Review'.

Elwing

ELECTRONIC MUSICAL INSTRUMENTS
12 Brett Road, Hackney, London, E8 1JP. 01-986 8455/ 01-986 5063

FREE WITH SEPTEMBER'S PRACTICAL ELECTRONICS

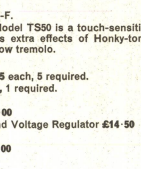

Britain's best-selling 64-page electronic kit and component catalogue from Doram with new products, new ideas!
Extra copies of catalogue available (send 20p to cover post and packing) from Doram Electronics Ltd, PO Box TR8, Wellington Road Estate, Wellington Bridge, Leeds LS12 2UF. Tel: 34222 (STD code 0532).

DORAM

BARGAIN PARCELS SAVE POUNDS

Huge quantities of electronic components must be cleared as space required. 1000's of Capacitors, Resistors, Transistors, etc. and ex equipment Panels, etc. Covered with valuable components. No time to sort, so must sell by weight. 7lb £3·95, 14lb £4·50, 28lb £10·50, 56lb £15·75, 112lb £25·50, inc. P & P.

BARGAIN PACKS

500 Mixed Resistors ¼ & ½ watt	£1	1lb Ferric Chloride	£1
100 Mixed Diodes, IN4148 etc.	£1	5lb Ferric Chloride	£4
100 Mixed Diodes including Zener and Power Types	£3	12 2TX010 Gen. Purp. PNP	£1
100 New and Marked Signal Transistors inc. 2TX212, BC148, BC168	£3	1 Dalo Pen, etch resist.	90p
500 New and Marked Transistors inc. AC128, 2N3055, 2TX212, BFY50, BD131	£8	40 OA91/95 type Glass Diodes	£1
		4 Aluminium Boxes 138 × 44 × 38mm. Ideal for Signal injectors etc.	£1

Add 30p P & P on all above items. Over £10 P & P FREE

DELUXE FIBRE GLASS BOARD P.C. KITS

INC. 150 sq in Copper Clad P/G Board, 1lb Ferric Chloride, A Dalo Pen, Abrasive Cleaner, 2 Mini Drill Bits, Etch Tray and Instructions. Only £5·99 inc. P & P. *Send cheque or P.O. with order to:*

SENTINEL SUPPLY, 20A Waddon Road, Croydon, Surrey.

TAPE HEADS

FIT A BRAND NEW HEAD
AND TRANSFORM THE QUALITY
OF YOUR TAPE PLAYER
AN EXTENSIVE RANGE ALWAYS IN STOCK
ASK FOR OUR SHORT FORM CATALOGUE

SPECIAL OFFER

STANDARD HEADS TO FIT MOST TAPE PLAYERS AT BULK DISCOUNT PRICES. ENCLOSE 15p P & P WITH ORDER

MONO CASSETTE	90p
STEREO CASSETTE	£2·00
STEREO 8 CARTRIDGES	£1·00
M/S CASSETTE ERASE	60p

MONOLITH Tel. Crewkerne 4321
THE MONOLITH ELECTRONICS CO. LTD.
5/7 Church Street, Crewkerne, Somerset, England

NEW MAZDA VALVES

All individually boxed, trade discounts to bonafide companies. Prices on application.

DM70 OFF EF83 OFF PCC85 OFF PL500 1-32
DY86/7 0-88 EF85 1-08 PCC88 1-65 PL504 2-16
DY802 0-72 EF86 1-65 PCF80 1-05 PL508 3-16
E92CC 1-72 EF89 OFF PCF82 1-05 PL509 OFF
EBC91 OFF EF91 1-32 PCF86 1-65 PY31/500 0-88
EBF80 OFF EF92 1-32 PCF801 1-65 PY81 0-88
EBF83 OFF EF93 0-88 PCF802 1-65 PY82 0-88
EBF89 0-85 EF183 0-84 PCF805 1-77 PY88 0-98
EC88 0-85 EF184 0-84 PCF806 1-77 PY500A 1-50
EC92 0-88 EH90 OFF PCF808 1-65 PY800 0-72
EC93 0-84 EL32 0-84 PCF809 1-65 PY801 0-72
EC95 OFF EL33 OFF PCF82 0-88 U25 1-10
EC97 1-84 EL34 0-98 PCH200 OFF U26 1-10
ECC32 0-88 EL36 1-84 PCL82 0-88 U191 OFF
ECC33 0-84 EL41 0-84 PCL83 1-05 U281 OFF
ECC34 1-90 EM81 OFF PCL84 0-79 UBF89 OFF
ECC35 1-90 EM84 0-85 PCL85 1-16 UCC85 1-16
ECC81 0-88 EY86/87 0-89 PCL805/ UCH81 1-24
ECF80 0-88 EZ35 0-88 850 0-89 UCL83 OFF
ECF82 0-88 EZ40 0-88 PD500 0-98 UF41 1-32
ECH35 OFF GY501 1-32 PL200 OFF UY85 0-80
ECH42 1-90 GZ32 1-84 PL81 1-08 Z77 1-08
ECH81 OFF KT33C 0-88 PL81A 1-08 ECC91OFF
ECH83 OFF OC3 0-88 PL82 1-08 6F8G/EF91 1-32
ECL80 0-88 PC86 1-08 PL83 1-08 PCL800 1-44
ECL82 0-72 PC88 0-88 PL84 0-88 30C1/PCF80 0-72
ECL83 OFF PC92 0-82 PL500 0-98 30C15/
ECL86 0-84 PC900 0-82 PL504 0-96 PCF801 1-58
EF80 0-84 PCC84 0-88 PL508 1-32 30P1/L15 1-44

MULLARD PRICES AVAILABLE ON REQUEST

NEW VALVES

Individually boxed and guaranteed but of European or other greatly reduced prices. Quotations for any valve not listed.

AZ1 1-58
AZ31 1-84
CBL31 1-58
CL33 1-90
CY31 1-90
DAF91 1-90
DAF96 1-90
DCC90 1-90
DF91 0-48
DF96 1-90
DK91 0-98
DK92 1-35
DK96 1-18
DL35 ELSM-DH/SUP
DL94 3-99
DY86 0-84
DY87 0-84
DY802 0-98
EABC80 0-84
EAF42 1-35
EB91 0-84
EBC33 1-78
EBC41 1-84
EBC81 1-18
EBF80 0-84
EBF83 1-25
EBF89 0-98
EBL31 2-99
EC52 0-98
EC92 0-85
EC93 0-84
EC94 0-90
EC95 0-90
EC96 0-98
ECC81 0-84
ECC82 0-84
ECC83 0-84
ECC84 0-90
ECC85 0-90
ECC86 0-98
ECC88 0-98
ECF80 0-84
ECF82 0-84
ECH35 0-98
ECH42 1-90
ECH81 0-84
ECH83 0-98
ECL80 0-90
ECL82 0-84
ECL83 1-90
ECL86 0-84
EF37A 1-90
EF39 0-84
EF50 0-65
EF80 0-84
EF85 0-84
EF86 USSR 0-48

EF89 Mullard
EF91 0-84
EF92 0-98
EF93 0-75
EF94 0-75
EF95 UK 1-65
EF96 1-90
EF183 0-90
EF184 0-90
EL32 1-90
EL33 OFF
EL34 0-85
EL34-CH/S(LOP
VACK 1-90
EL41 0-84
EL37 3-99
EL42 0-84
EL43 1-75
EL44 1-75
EL45 0-84
EL46 0-84
EL84 0-90
EL90 0-84
EM80 0-84
EM81 1-25
EM84 0-84
EM85 1-25
EV51 0-75
EY51 0-75
EY86 0-84
EY87 0-84
EY88 0-84
EZ40 1-25
EZ80 0-85
EZ81 0-85
FW4/500 1-90
GY501 1-32
GZ30 0-75
GZ32 0-75
HN309 2-00
KT61 1-84
KT66 2-00
KTW61/CR 1-84
KT88 4-75
KTW61 1-78
MU14 1-00
N78 7-00
OA2 0-45
OB2 0-45
PC86 0-85
PC88 0-85
PC92 0-82
PC97 0-88
PC900 0-75
PCC84 0-45
PCC85 0-85
PCC88 1-65
PCF80 1-05
PCF82 1-05
PCF86 1-65
PCF200 1-77
PCF801 1-65
PCF802 1-65
PCF805 1-77
PCF806 1-77
PCF808 OFF
PCH200 OFF
PCL82 0-88
PCL83 1-05
PCL84 0-79
PCL85 1-16
PCL86 0-88
PCL805/ 850 0-89
PD500 0-98
PEN45 1-29
PL36 0-85
PL81 1-08
PL82 1-08
PL83 1-08
PL84 0-88
PL500 0-98
PL504 0-96
PL508 1-32
PL509 OFF
PL802 1-65
PY31/500 0-72
PY81 0-72
PY82 0-85
PY88 0-98
PY500A 1-50
PY800/801 0-72
PY801 0-72
U14 0-85
U18 0-85
U191 OFF
U251 1-10
UABC80 0-90
UAF42 1-35
UBC41 0-84
UBF80 0-84
UBF89 0-98
UCC85 1-16
UCF80 1-24
UCH42 1-84
UCH81 0-84
UCL82 0-90
UCL83 1-90
UF41 1-32
UF42 1-32
UF80 0-84
UF85 0-84
UL41 0-75
UL84 0-90
UM80 0-84
UM84 0-84
UY41 0-75
UY85 0-80
VR150/30 0-48
VR150/30 0-84
1R5 0-85
1S5 0-85
1T4 0-48
1U4 0-85
3V4 1-00
5U4G 0-85
5U4G 1-00
5V4G 0-85
5Y3GT 0-85
6X4 0-85
6X5G 1-00
6Z4G 1-00
6X5GT 0-85
7B5 1-00
7B7 1-00
7C5 1-00
7C6 1-25
7H7 1-00
7R7 1-84
7S7 1-90
7Y4 0-75
9D2 0-75
10C1 0-72
10F1 0-72
10F9 0-72
12AT6 0-85
12AT7 0-85
12AU6 0-85
12AU7 0-85
12BA6 0-85
12BE6 0-85
12BH7 0-85
12K7GT 0-85
12Q7GT 0-85
20P1 1-58
20P3 1-58
20P4 1-58
30P4MR OFF
30PL1 1-44
30PL12 1-44
30PL13 1-44
30PL14 1-68
30PL15 1-44
30PL16 1-44
30C17 1-90
30C18 2-16
30C1/PCF805 1-28
30FL2/6116 1-90
30FL14/ PCL805 1-90
30FL2 1-90
30FL12 1-90
30P12 0-72
30P19 0-72
30PL1/ PCL82 0-72
30PL13/ PCL85 1-44
30PL14 1-68
30PL15 1-44
30PL16 1-44
30PL1/PCL86 1-44
30PL14/PCL805 1-32
30PL15/ PCL85 1-68
30PL16 1-44
30PL15 1-44

TRANSISTORS-INTEGRATED CIRCUITS

All transistors, I.C's offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, etc.

AA119 0-35
AAY30 0-12
AAY32 0-15
AAZ15 0-35
AAZ16 0-35
AAZ17 0-35
AC107 0-75
AC113 0-75
AC125 0-55
AC126 0-55
AC128 0-55
AC141 0-56
AC141K 0-90
AC142 0-60
AC142K 0-95
AC151 0-60
AC187 0-55
AC188 0-55
ACY17 0-65
ACY18 0-65
ACY19 0-65
ACY20 0-65
ACY21 0-65
ACY22 0-65
AD140 0-85
AD161 0-75
AD162 0-75
AD163 0-75
AF106 0-65
AF114 0-55
AF115 0-55
AF116 0-55
AF117 0-55
AF139 0-90
AF186 1-50
AF239 0-90
AFZ11 0-78
AFZ12 0-75
ASY26 0-45
ASY27 0-45
ASZ15 1-25
ASZ16 1-25
ASZ17 1-25
AU106 0-95
AU107 0-85
AU110 0-90
AU111 0-90
AU112 0-90
AU113 0-90
AUY10 0-85
AUY21 0-85
BA145 0-15
BA148 0-15
BA155 0-15
BA156 0-15
BAW62 0-15
BAX13 0-07
BAX16 0-12
BC107 0-12
BC108 0-12
BC109 0-13
*BC113 0-15
*BC114 0-15
*BC115 0-15
*BC116 0-19
*BC117 0-19
*BC118 0-16
*BC119 0-20
*BC120 0-25
*BC121 0-20
*BC122 0-20
*BC123 0-20
*BC124 0-20
*BC125 0-20
*BC126 0-20
*BC127 0-18
*BC128 0-18
*BC129 0-18
*BC130 0-19
*BC131 0-19
*BC132 0-19
*BC133 0-19
*BC134 0-19
*BC135 0-19
*BC136 0-19
*BC137 0-19
*BC138 0-19
*BC139 0-19
*BC140 0-19
*BC141 0-19
*BC142 0-19
*BC143 0-19
*BC144 0-19
*BC145 0-19
*BC146 0-19
*BC147 0-19
*BC148 0-19
*BC149 0-13
*BC157 0-13
*BC158 0-13
*BC159 0-13
*BC167 0-13
*BC168 0-13
*BC169 0-13
*BC170 0-13
*BC171 0-14
*BC172 0-14
*BC173 0-14
BC177 0-18
BC178 0-18
BC179 0-18
*BC182 0-11
*BC183 0-11
*BC184 0-11
*BC186 0-11
*BC187 0-11
*BC214 0-17
*BC237 0-15
*BC238 0-15
*BC239 0-15
BC300 0-99
BC301 0-99
*BC302 0-99
*BC303 0-99
*BC306 0-18
*BC307 0-18
BSW4 0-99
*BC308 0-18
*BC309 0-18
BC327 0-19
BC328 0-19
BC337 0-19
BC338 0-19
BCY30 1-60
BCY31 1-60
BCY32 1-60
BCY33 1-60
BCY34 1-60
BCY38 3-90
BCY39 3-90
BCY40 2-50
BCY42 0-18
BCY43 0-18
BCY70 0-18
BCY71 0-22
BCY72 0-17
BCZ11 1-50
BD115 0-90
BD121 0-90
BD123 1-90
BD124 1-60
BD131 0-84
BD132 0-84
*BD135 0-38
*BD136 0-38
*BD137 0-38
*BD138 0-38
*BD140 0-47
BD144 0-90
BD181 1-38
BD182 1-50
BD237 0-90
BD238 0-90
BDX10 0-75
BDX32 0-90
BDY20 1-42
BDY38 1-90
BF115 0-90
BF152 0-90
BF153 0-25
BF154 0-25
BF159 0-25
BF160 0-25
BF167 0-39
BF173 0-39
BF177 0-39
BF178 0-45
BF179 0-45
BF180 0-45
BF181 0-45
BF182 0-45
BF183 0-45
BF184 0-45
BF185 0-45
*BF194 0-12
*BF195 0-13
*BF196 0-13
*BF197 0-13
BF200 0-52
*BF224 0-25
*BF244 0-25
BF257 0-37
BF258 0-42
BF259 0-50
*BF336 0-50
*BF337 0-53
*BF338 0-55
BF361 1-38
BF529 1-38
*BF569 0-25
*BF598 0-25
BFW10 0-90
BFW11 0-90
BFW12 0-90
BFX85 0-61
BFX87 0-61
BFX88 0-32
BFY50 0-32
BFY51 0-32
BFY52 0-32
BFY90 0-32
BAX13 0-07
BAX16 0-12
BC107 0-12
BC108 0-12
BC109 0-13
*BC113 0-15
*BC114 0-15
*BC115 0-15
*BC116 0-19
*BC117 0-19
*BC118 0-16
*BC119 0-20
*BC120 0-25
*BC121 0-20
*BC122 0-20
*BC123 0-20
*BC124 0-20
*BC125 0-20
*BC126 0-20
*BC127 0-18
*BC128 0-18
*BC129 0-18
*BC130 0-19
*BC131 0-19
*BC132 0-19
*BC133 0-19
*BC134 0-19
*BC135 0-19
*BC136 0-19
*BC137 0-19
*BC138 0-19
*BC139 0-19
*BC140 0-19
*BC141 0-19
*BC142 0-19
*BC143 0-19
*BC144 0-19
*BC145 0-19
*BC146 0-19
*BC147 0-19
*BC148 0-19
*BC149 0-13
*BC157 0-13
*BC158 0-13
*BC159 0-13
*BC167 0-13
*BC168 0-13
*BC169 0-13
*BC170 0-13
*BC171 0-14
*BC172 0-14
*BC173 0-14
BC177 0-18
BC178 0-18
BC179 0-18
*BC182 0-11
*BC183 0-11
*BC184 0-11
*BC186 0-11
*BC187 0-11
*BC214 0-17
*BC237 0-15
*BC238 0-15
*BC239 0-15
BC300 0-99
BC301 0-99
*BC302 0-99
*BC303 0-99
*BC306 0-18
*BC307 0-18
BSW4 0-99
*BC308 0-18
*BC309 0-18
BC327 0-19
BC328 0-19
BC337 0-19
BC338 0-19
BCY30 1-60
BCY31 1-60
BCY32 1-60
BCY33 1-60
BCY34 1-60
BCY38 3-90
BCY39 3-90
BCY40 2-50
BCY42 0-18
BCY43 0-18
BCY70 0-18
BCY71 0-22
BCY72 0-17
BCZ11 1-50
BD115 0-90
BD121 0-90
BD123 1-90
BD124 1-60
BD131 0-84
BD132 0-84
*BD135 0-38
*BD136 0-38
*BD137 0-38
*BD138 0-38
*BD140 0-47
BD144 0-90
OC24 3-99
OC25 3-99
OC26 2-99
OC28 2-99
OC29 3-99
OC35 2-99
OC36 2-99
OC41 0-45
OC42 0-90
OC43 0-90
OC44 0-39
OC45 0-39
OC71 0-45
OC72 0-45
OC73 1-90
OC74 0-90
OC75 0-90
OC76 0-90
OC77 1-39
OC81 0-45
OC81Z 1-90
OC82 0-90
OC83 0-90
OC84 0-90
OC122 1-90
OC123 1-90
OC139 1-25
OC140 1-25
OC169 1-25
OC170 0-90
OC171 1-90
OC200 1-90
OC201 1-90
OC202 1-25
OC203 1-25
OC204 1-25
OC205 1-25
OC206 1-75
OCP71 1-25
OCP72 2-25
*R2006B 2-25
*R2006S 2-25
*R2010B 2-25
*R2010S 2-25
TIC206D 1-39
TIC206D 1-39
TIL309 0-90
*TIP29A 0-90
TIP30A 0-90
*TIP31A 0-62
*TIP32A 0-62
*TIP33A 1-99
*TIP34A 1-99
TIP41A 0-79
*TIP42A 0-79
SN141 0-85
SN142 0-85
SN143 0-85
SN144 0-85
SN145 1-00
SN146 1-00
SN147 1-00
SN148 1-00
SN149 1-00
SN150 1-00
SN151 0-85
SN152 0-85
7400 0-39
7401 0-39
7402 0-39
7403 0-39
7404 0-39
7405 0-39
7406 0-39
7407 0-39
7408 0-39
7409 0-39
7410 0-39
7411 0-39
7412 0-39
7413 0-39
7414 0-49
7416 0-49
7417 0-49
7420 0-39
7423 0-39
7425 0-39
7426 0-39
7427 0-39
7430 0-39
7432 0-39
7433 0-39
7437 0-42
7438 0-42
7440 0-39
7441AN 0-82
7442 0-78
7447AN 0-99
7450 0-39
7451 0-39
7453 0-39
7460 0-39
7470 0-42
7472 0-39
7473 0-39
7474 0-49
7475 0-49
7476 0-42
7480 0-78
7482 0-89
7483 0-89
7484 1-00
7485 1-00
7486 0-82
7489 1-99
7490 0-89
7491AN 0-89
7492 0-89
7493 0-89
7494 0-89
7495 0-89
7496 0-89
7497 1-99
74100 1-79
74107 0-89
74109 0-89
74110 0-57
74111 0-89
74116 0-89
74118 0-89
74119 0-89
74141 0-89
74121 0-45
74122 0-89
74123 1-99
74125 0-89
74126 0-89
74132 0-89
74136 0-89
74141 0-89
74142 0-89
74143 0-89
74144 0-89
74145 1-00
74147 1-99
74148 2-00
74150 1-99
74151 0-89
74153 0-89
74154 1-99
74155 0-89
74156 0-89
74157 0-89
74158 0-89
74170 0-89
74172 0-89
74173 0-89
74174 0-89
74175 0-89
74176 0-89
74177 0-89
74178 0-89
74179 0-89
74180 0-89
74181 1-99
74182 0-89
74184 2-99
74185 2-99
74186 2-99
74187 2-99
*74S138 1-75

● OSCILLOSCOPE TUBES
Types CV 1526,
VCR139A
All at £8·00 each,+ p & p 50p
8% VAT

EXPRESS POSTAGE
25p per order in UK

VAT To be added to all orders

VALVES 12½%
TRANSISTORS 8%
TRANSISTORS MARKED* 12½%

TERMS OF BUSINESS: C.W.O. A/c's available to approved companies. Open daily to callers 9 a.m.-5 p.m. Monday to Friday. Prices correct when going to press Prices on application for any types not listed.

RST

VALVE MAIL ORDER CO.
Climax House
Fallsbrook Road, London SW16 6ED
SPECIAL EXPRESS MAIL ORDER SERVICE

DIL SOCKETS 8 pin 15p
14 pin 15p
16 pin 17p

TELEPHONE No.
01-677-2424
TELEX: 946708

BEFORE ***YOU*** BUY AN AMPLIFIER MODULE—CHECK:

DOES IT HAVE ★ 30A POWER TRANSISTORS ★ 3A DRIVERS (100 W UNIT) ★ 2 YEAR GUARANTEE ★ INTEGRAL OUTPUT CAPACITOR

THEN COMPARE WITH THE TAMBA RANGE—EXCELLENT VALUE—25, 50 & 100 W RMS

TAM1000 100W 4 OHMS 65V	£9·80
TAM500 50W 4 OHMS 45V	£7·50
TAM250 25W 8 OHMS 45V	£4·75
POWER SUPPLIES	
For 1 or 2 TAM250/500	£7·50
For 1 or 2 TAM1000	£9·80
(Carr. 50p on supplies)	

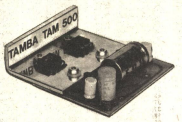

NEW

ALL PURPOSE MIXER/PREAMP

(WITH 60 mm SLIDER VOLUME)

- Anodised & printed facia
- Suitable for multiple input systems
- High & low impedance inputs
- High sensitivity
- Built in supply smoothing
- 20-20,000 hz ±1dB
- 80dB Noise level
- Accepts a wide variety of inputs
- Wide range bass & treble controls Use up to 10 preamps with 1 power

COMPLETE & TESTED assembly with Treble & Bass controls plus slider Volume Control. **£6·50**

- Suits loads 4-16 ohms
- 20-20,000 hz ±1dB
- Silicon circuitry throughout
- Glass fibre P.C.B.
- High sensitivity (100mV 10k)
- Low distortion (0·1%)
- Low profile (1" High 3½" x 3")
- 75% efficient
- Accepts most mixer/preamps
- Four simple connections

High Grade Components used throughout: Texas, Mullard, R.C.A., Plessey, etc.

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s, etc.) C.O.D. (60p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50-100W units and at 12½% for 25W units

Hours, 9.30 a.m.–5 p.m. Monday—Saturday. Callers welcome. Tel: (01) 684 0098

TAMBA ELECTRONICS

BENSHAM MANOR ROAD PASSAGE, BENSHAM MANOR ROAD, THORNTON HEATH, SURREY

PHILIPS

PHILIPS

YOU & PHILIPS HI-FI KITS

The top sellers for home assembly in Europe—now available in the U.K.

Now – read all about the Philips range of quality kits for home assembly – mixers, amplifiers, speakers, etc, etc. Send today to S.S.T. Distributors (Electronic Components) Ltd., West Road, Tottenham, London N17 0RN

Please send me, quickly, the new colour catalogue.

Name PW 9.1

Address

PHILIPS

Postcode

free SEND TODAY!

S.S.T. Distributors is a member of the Philips Group of Companies.

Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WAA

Free! Brochure, without obligation to: WK 977

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O.Box 156, Jersey, Channel Islands.

NAME

ADDRESS (Block caps please)

TV GAMES CHIP
AY-3-8500 **£9·95**. Printed circuit and kit of extra parts black and white version **£10·95**. Colour model **£24·95**. Rifle kit **£4·95**. Send sae for data.

NEW COMPONENT SERVICE
Resistors 5%, carbon E12 1Ω to 10MΩW 1p. 1W 3p. **Preset** pots subminiature 0·1W 100Ω to 4M7 9p. **Potentiometers** 2W 4K7 to 2M2 log or lin. Single 30p. Dual 90p. **Polystyrene** capacitors E12 63V 22pF to 8200pF 3p. **Ceramic** Capacitors 50V 6·8pF to 47000pF 3p. **Mylar** Capacitors 100V ·001, ·002, ·005 4p. ·01, ·02, ·025 4p. **Polyester** Capacitors 250V ·001, ·002, ·005, ·01 5p. ·02, ·033 6p. ·047 7p. **Electrolytic** 50V ·47, 1, 2mF 5p. 25V 5, 10mF 5p. 16V 22, 33, 47mF 5p. 100mF 7p. 220, 330mF 9p. 470mF 11p. 1000mF 18p. **Zener** Diodes 400mW E24 3V3 to 33V 9p.

MAINS TRANSFORMERS
6-0-6V 100mA **75p**. 9V 75mA **94p**. 0/12/15/20/24/30V 1A **£3·85**. 12-0-12V 50mA **96p**. 0/12/15/20/24/30V 2A **£5·15**. 6·3V 1·5A **£3·30**. 6-0-6V, 12A **£3·75**. 9-0-9V 1A **£3·39**. 12-0-12V 1A **£3·69**. 15-0-15V 1A **£3·89**. 30-0-30V 1A **£3·99**.

PRINTED CIRCUIT KITS, ETC.*
Contains 1 sq ft copper clad, 1 tin of pc board, 1lb ferric chloride, etch resist pen, drill bit and laminate cutter **£3·85**. 100 sq ins pc board **89p**. 1lb FeCl **£1·05**. Etch resist pen **75p**.

S-DECS and T-DECS*
S-Dec **£1·99**. T-Dec **£3 ·61**.
C-Dec **£3 ·97**. 1-C-Dec **£4·97**.
IC carriers with sockets:
16 dil **£1·91**. 10TO5 **£1·79**.

SINCLAIR CALCULATORS AND POCKET TV
Sinclair pocket TV **£165**. Cambridge Scientific Programmable **£13·95**. Cambridge library **£4·95**. Cambridge Scientific **£8·45**. Oxford Scientific **£10·60**. Mains adaptors **£3·00**.

BATTERY ELIMINATOR BARGAINS
3-WAY MODELS
With switched output and 4-way multi-jack connector. Type 1—3/4½/9V 1A model **£3·30**. Type 2—4½/7½/9V 300mA **£2·90**.
1000mA RADIO MODELS
With press-stud connectors. 9V **£3·45**, 6V **£3·45**, 9V + 9V **£3·45**, 6V + 6V **£3·45**, 4½V + 4½V **£3·45**.
CASSETTE MAINS UNIT
7½V with 5 pin din plug 150mA **£3·65**.
FULL-WAVE RECTIFIER MODEL £6·40.
Switched output of 3/6/7½/9V 400mA stabilised.
CAR CONVERTORS 12V INPUT
Output 9V 300mA **£1·80**. Output 7½V 300mA **£1·80**.

BATTERY ELIMINATOR KITS
Send s.a.e. for free leaflet on range.
100mA radio types with press stud battery terminals. 4½V 3D, 10, 6V **£2·10**, 9V **£2·10**. 4½V+4½V 3D, 6V+6V **£2·50**. 9V+9V **£2·50**.
Cassette type 7½V 100mA with din plug **£2·10**.
Transistor stabilised 8-way type for low hum. 3/4½/6/7½/9/12/15V 100mA. **£3·35**. Amp **£4·40**.
Heavy duty 13-way types 4½/6/7½/9/11/13/14/17/21/25/28/34/42V. 1 Amp **£4·95**. 3 Amp **£7·95**.
Car conversion 12V DC. Output 6/7½/9V DC 1A transistor stabilised **£1·95**.
Stabilised laboratory power kit Switched 1 to 30V in 0·1V steps. 1 Amp **£12·45**. 2 Amp **£14·95**.

SINCLAIR PROJECT 80 AUDIO MODULES
PZ5 **£4·95**. Z40 **£5·75**.
BI-PAK AUDIO MODULES
5450 tuner **£31·95**. AL60 **£4·86**. PA100 **£14·95**. MK60 audio kit **£36·48**. Stereo 30 **£17·95**. SPM80 **£3·78**. TBTR **£3·78**. Send sae for free data.

SINCLAIR IC30
IC30 10W-10W stereo integrated circuit amp kit with printed circuit and data **£6·99**.
PZ30 Power supply kit for above **£5·65**
VP20 Volume, tone control and preamp kit **£8·95**.
Send sae for free leaflet on the whole system.

JC12 AND JC40 AMPLIFIERS
JC12 6V integrated circuit amp with free data and printed circuit **£1·95**.
Also new JC40 20W model with pcb **£3·95**.
Send sae for free leaflet on both models and associated power supply and preamp kits.

FERRANTI ZN414
IC radio chip **£1·44**. Extra parts and pcb for radio **£3·85**. Case **£1**. Send sae for free data.

SWANLEY ELECTRONICS
DEPT. PW, PO BOX 68,
32 GOLDSEL RD., SWANLEY, KENT

Send sae for free data on kits. Post 30p. Prices include VAT. Official orders welcome. Overseas customers deduct 7% on items marked * and 11% on others.

TTLs by TEXAS

7400	15p	74111	75p
7401	15p	74112	85p
7402	18p	74116	218p
7403	18p	74118	180p
7404	36p	74120	139p
7405	36p	74121	75p
7406	43p	74122	52p
7407	43p	74123	90p
7408	22p	74125	79p
7409	22p	74126	79p
7410	18p	74128	82p
7411	29p	74132	98p
7412	35p	74136	81p
7413	45p	74141	139p
7414	85p	74142	399p
7416	40p	74145	139p
7417	49p	74147	295p
7420	18p	74148	139p
7423	40p	74150	139p
7425	36p	74151	81p
7426	36p	74153	81p
7427	36p	74154	139p
7428	43p	74155	97p
7430	18p	74156	97p
7432	29p	74157	97p
7437	36p	74159	199p
7438	36p	74160	139p
7440	37p	74161	139p
7441	85p	74162	139p
7442	79p	74163	139p
7443	133p	74164	139p
7444	133p	74165	139p
7445	133p	74166	139p
7446	108p	74174	139p
7447	89p	74175	97p
7448	89p	74176	139p
7450	18p	74177	139p
7451	18p	74180	139p
7453	18p	74181	295p
7454	18p	74182	199p
7460	18p	74184	199p
7470	38p	74186	899p
7472	38p	74190	199p
7473	38p	74191	199p
7474	38p	74192	199p
7475	48p	74193	139p
7476	48p	74194	199p
7480	64p	74195	199p
7481	198p	74196	199p
7482	99p	74197	139p
7483	99p	74198	299p
7484	129p	74199	279p
7485	129p	74200	1·99
7486	39p	74251	159p
7489	399p	74273	299p
7490	48p	74278	329p
7491	99p	74279	119p
7492	58p	74283	299p
7493	58p	74284	899p
7494	99p	74285	475p
7495	79p	74290	199p
7496	99p	74293	199p
74100	148p	74365	168p
74100	148p	74365	168p
74105	79p	74367	199p
74107	79p	74390	299p
74109	89p	74393	249p
74110	89p	74490	299p

CMOS ICs			
4000	21p	4040	159p
4001	21p	4042	97p
4002	21p	4043	99p
4006	127p	4045	199p
4007	21p	4047	199p
4009	21p	4049	84p
4010	21p	4050	84p
4012	23p	4054	129p
4013	59p	4055	199p
4014	99p	4056	149p
4015	99p	4060	139p
4016	54p	4069	39p
4017	159p	4071	21p
4018	119p	4072	39p
4019	59p	4081	39p
4020	139p	4082	39p
4021	99p	4085	39p
4022	99p	4510	149p
4023	21p	4511	149p
4025	23p	4518	139p
4026	299p	4520	139p
4027	64p	4528	149p
4028	99p	14433	614
4029	129p	14533	546p
4030	87p	14563	£1

LOW PROFILE DIL SOCKETS BY TEXAS

8 pin 12p	32 pin 38p
14 pin 15p	24 pin 40p
16 pin 16p	28 pin 48p
18 pin 36p	40 pin 69p

MEMORY I.Cs
1702A EPROM **1000p**
2102-2 RAM **210p**
2107 RAM **450p**
2112-2 RAM **470p**
AY-5-1013X UART **795p**
CB080A CPU **1495p**
IK05-2013 ROM **899p**

OP. AMPS

LM300/A	49p	741	25p
LM318N	225p	748	49p
LM324N	139p	787	£5·95
LM339N	175p	MC1458	75p
NE531V	149p	CA3130	195p
709	38p	CA3140	168p
733	199p	LM3900	79p

LINEAR I.Cs

AY-1-270	699p	NE555	109p
CA3028A	112p	NE556	199p
CA3045	199p	NE560	499p
CA3046	99p	NE561	499p
CA3053	79p	NE567V	299p
CA3065	99p	SN76003N	299p
CA3080E	97p	SN76003N	275p
CA3080A	139p	SN76013N	275p
CA3094AQ	425p	SN76013N	175p
CA3083CC	499p	SN76013ND	199p
LM377N	399p	SN76018	288p
LM380N	112p	SN76023N	75p
LM381N	199p	SN76033ND	199p
LM389N	99p	SN76033N	275p
M252AA	899p	SP8615	119p
MC1310P	199p	TAA661A	199p
MC1351P	119p	TAA661B	159p
MC1455	89p	TBA120	97p
MC1466P/P	112p	TBA641B	369p
MC1496P	139p	TBA651	295p
MC3360P	199p	TBA800	112p
MC4000B	199p	TBA810S	139p
MFC8040	299p	TBA820	109p
NE540	199p	TBA920	449p
NE545L	199p	ZN414	149p
NE555V	89p		

VOLTAGE REGULATORS—Fixed

Plastic—TO220—3 Terminals			
1 Amp	+ ve	− ve	
5V	7805	7905	215p
8V	7808	7908	215p
12V	7812	7912	215p
15V	7815	7915	215p
18V	7818	7918	215p
24V	7824	7924	215p
100mA—TO92			
5V	78L05	79L05	85p
6V	78L06	79L06	85p
12V	78L12	79L12	85p
15V	78L15	79L15	85p
LM309K TO3	1A 5V	150p	396p
LM323K TO3	3A 5V	299p	599p
LM387N (16 DIL) 100mA +5 —12V			275p
LM1469 (16 DIL) 100mA 15V			399p
(Adj. by Re from ±8V to ±30V)			
TBA465B (TO3) 0·5A 12V			199p
7800 (TO3) 1A 5V			199p

VARIABLE

LM 14 pin DIL 2V-37V 150mA	45p
LM317T TO220 1A—2V-37V	325p
TL430 TO92 100mA 2V-30V	149p
78MGTIC 4 pin DIL 5V-30V 500mA	199p

OPTO-ELECTRONICS

ORP 21	139p	LEDS: TIL209	Red	16p
ORP 12	79p	TIL211	Green	16p
ORP 60	89p	TIL212	Infrared	81p
ORP 61	89p	TIL220	5 mm	18p
TIL177	49p		Green	38p
			Yellow	38p

DISPLAYS

3015F	Miniltron	175p	FND500	Red 139p
DL704	Red/Green	169p	FND507	Red 139p
DL707	Red/Green	169p	TIL321	Red 139p
DL747	Red/Green	299p	TIL322	Green 139p

DRIVERS:	75491	84p	9368PC	216p
	75492	104p		

SCR-THYRISTORS

1A 50V TO5	65p	C106D 70p
1A 400V TO5	99p	2N3525 130p
1A 400V stud	139p	2N4444 269p
7A 400V TO5	199p	
12A 400V TO220	199p	
16A 400V TO220	229p	**DIODES**
16A 800V TO220	299p	BY127 12p
BT 106 stud	159p	OA47 9p
		OA81 9p
		OA85 15p
TRIACS	**BRIDGE**	OA90 9p
Plastic	**RECTI-**	OA91 9p
PEAK	**FIERS**	OA95 9p
1A 50V 125p		OA200 9p
8A 400V 197p	1A 50V 25p	OA202 15p
8A 400V 197p	1A 100V 27p	IN914 7p
10A 400V 149p	1A 400V 31p	IN916 7p
10A 500V 169p	1A 600V 39p	M1201 29p
15A 400V 299p	2A 100V 45p	M1448 7p
15A 500V 299p	2A 400V 49p	IN4001/2 6p
	3A 600V 89p	IN4004/5 8p
40430 139p	4A 100V 89p	IN4007 8p
40669 139p	4A 400V 99p	IN4148 5p
T2 202D 139p	6A 100V 109p	IN5404 29p
BR100 32p	6A 400V 129p	IN5406 39p
	10A 400V 279p	
HEAT SINK	25A 400V 499p	**ZENERS**
For plastic		2·7V-33V
TO220	**FM TUNER**	400mW 11p
TRS. or VR	LP1186 £9·50	1W 25p

PW "JUBILEE" ELECTRONIC ORGAN

AY-1-0212	699p	VM16	
AY-1-0213	699p	14 DIL Bridge	45p
AY-1-1313	775p	7812	199p
AY-5-1015	699p	LM320-12	
AY-5-1017A	699p	-12V Regulator	215p

DIL SKTS to suit available. App prices VAT inc.

VAT INCLUSIVE PRICES

Please add 20p P. & P.

MAIL ORDER ONLY

TECHNOMATIC LTD.
54 SANDHURST ROAD, LONDON, NW9
Tel. 01-204 4333 Telex 922800

TRANSISTORS

AC125	29p
AC126	39p
AC127	29p
AC128	29p
AC176	29p
AC187	39p
AC188	39p
AD149	69p
AD161	49p
AD162	49p
AF114	22p
AF115	22p
AF116	22p
AF117	22p
AF124	34p
AF125	34p
AF126	34p
AF127	34p
AF139	68p
AF178	68p
AF180	68p
AF181	68p
AF186	68p
AF239	68p
BC107/B	15p
BC108/B	15p
BC114C	15p
BC109C	15p
BC147	9p
BC148	9p
BC149	10p
BC157	15p
BC158	13p
BC159	13p
BC169C	15p
BC177	25p
BC172	11p
BC178	25p
BC179	17p
BC182	12p
BC182L	12p
BC184	14p
BC212	12p
BC212L	14p
BC214	17p
BC214L	20p
BC237	12p
BC239	12p
BC307	12p
BC308	12p
BC309	14p
BC327	14p
BC328	14p
BC337	14p
BC338	14p
BC347	17p
BC348	17p
BC349	17p
BC350	17p
BC477	39p
BC478	39p
BC479	39p
BC547	12p
BC548	12p
BC549	12p
BC550	12p
BC557	12p
BC558	12p
BC559	12p
BC560	12p
BCY70	25p
BCY71	35p
BD131	65p
BD132	65p
BD135	55p
BD136	55p
BD137	55p
BD138	55p
BD139	55p
BD140	69p
BD175	79p
BF115	24p
BF167	29p
BF170	25p
BF173	25p
BF177	28p
BF178	28p
BF179	35p
BF180	39p
BF181	35p
BF182	39p
BF183	39p
BF184	34p
BF185	34p
BF194	11p
BF195	11p
BF196	17p
BF197	17p
BF200	49p
BF244B	49p
BF256B	69p
BF257	39p
BF258	39p
BF259	39p
BF337	32p
BF338	32p
BFR40	34p
BFR41	34p
BFR79	34p
BFR80	34p
BFR81	34p
BFW10	90p
BFW10	90p
BFX29	39p
BFX84	39p
BFX85	39p
BFY50	22p
BFY51	22p
BFY52	22p
BFY90	99p
BRY39	49p
BSX20	39p
BSX30	39p
BU105	312p
BU108	312p
BU340	79p
MJ481	175p
MJ491	199p
MJ2501	299p
MJ2955	199p
MJE2055	139p
MJE3055	99p
MJE5731	299p
MPF102	49p
MPF104	49p
MPF105	49p
MPS706	37p
MPSA06	37p
MPSA12	49p
MPSA55	49p
MPSA56	49p
MPSU05	79p
MPSU06	79p
MPSU55	99p
MPSU56	99p
OC28	99p
OC35	99p
OC36	99p
OC45	28p
OC71	40p
OC72	40p
OC81	40p
OC81D	40p
OC82	40p
OC82D	40p
OC83	40p
OC84	40p
OC139	99p
OC140	99p
OC170	39p
OC171	39p
OC200	99p
OC201	99p
OC202	99p
OC203	99p
OC204	99p
OC205	99p
OC206	99p
R2008B	225p
R2010B	225p
TIP29A	39p
TIP30A	49p
TIP30A	69p
TIP30C	72p
TIP31A	39p
TIP31C	49p
TIP32A	49p
TIP32C	69p
TIP33A	87p
TIP33C	99p
TIP34A	124p
TIP34C	149p
TIP35A	342p
TIP36A	399p
TIP36C	387p
TIP41A	69p
TIP41C	89p
TIP42A	89p
TIP42C	99p
TIP2955	99p
TIP3055	69p
TIS43	39p
TIS83	39p
TIS90	39p
2N696	43p
2N697	43p
2N698	99p
2N706	22p
2N708	22p
2N914	39p
2N929	19p
2N930	19p
2N1132	25p
2N1302	39p
2N1305	79p
2N1306	79p
2N1307	79p
2N2160	199p
2N2192	99p
2N2222	22p
2N2369	22p
2N3442	199p
2N3502	39p
2N3702	14p
2N3703	14p
2N3704	14p
2N3705	14p
2N3706	14p
2N3707	14p
2N3708	14p
2N3773	329p
2N3819	49p
2N3820	99p
2N3823	99p
2N3866	61p
2N3903	14p
2N3904	22p
2N3905	22p
2N4036	99p
2N4037	99p
2N4058	14p
2N4059	14p
2N4061	14p
2N4062	19p
2N4123/4	22p
2N4125/6	22p
2N4284	39p
2N4401	34p
2N4402	34p
2N4427	99p
2N4871	49p
2N5087	39p
2N5179	79p
2N5401	42p
2N5401	42p
2N5457	49p
2N5458	49p
2N5459	49p
2N5485	49p
2N5457	49p
2N6027	99p
2N6340	79p
2N6254	149p
2N6027	99p
2N109	89p
2N141	99p
2N3055	69p
40360	49p
40361	49p
40362	49p
40485	49p
40410	35p
40411	325p
40594	49p
40595	87p
40602	99p
40636	149p
40673	99p

Soldercon Pins
100 for 49p

TV GAME IC AY-3-8500
775p

Receivers and Components

ELECTRONIC DEVICES and Semiconductors. Components for this month's projects. SAE lists. NKM, 32 Seaside, Eastbourne, Sussex. Tel: 33921.

LEDs. Mixed bags of 4 different sizes and 4 different colours, 50 at £5·25, 100 at £9·25, including VAT and post and packing. CWO. Michael Williams Electronics, 47 Vicarage Avenue, Cheadle Hulme, Cheshire SK8 7JP.

BRAND NEW COMPONENTS BY RETURN.

Electrolytic capacitors 16V, 25V, 50V.—0·47, 1·0, 2·2, 4·7 & 10mfd.—2p. 22, 47—3p. (50V—4p). 100—7p. (50V—8p) 220—8p. (50V—10p) 470—11p. (50V—16p) 1000/16V—15p. 1000/25V—18p. 1000/50V—22p.

Subminature bead tantalum electrolytics—0·1, 0·22, 0·47, 1·0, 2·2 @ 35V, 4·7/25V—11p. 10/25V—13p. 22/16V, 47/6V, & 100/3V—15p.

Mullard miniature ceramic E12 series 2% 63V. 10pf. to 47pf.—3p. 56pf. to 330pf.—4p.

Vertical mounting ceramic plate 50V.
E12 series 22pf-1000pf. E6 series 1500pf-47000pf.—2p.

Polystyrene E12 series 5V hotspot mounting. 10pf to 1000pf—3p. 1200pf. to 10000pf.—4p.

Mullard polyester 250V vertical mounting E6 series.
0·01 to 0·1—4p. 0·15, 0·22—5p. 0·33, 0·47—6p. 0·68—11p. 1·0—13p. 1·5—16p. 2·2—22p.

Mylar (Polyester) Film 100V vertical mounting. 0·001, 0·002, 0·005—3p. 0·01, 0·02—4p. 0·04, 0·05—4p.

Miniature resistors Highstab E12 series 2%. Carbon Film 0·25W 1Ω to 10MΩ. (10% over 1MΩ)—3p. Metal Film 0·125W, 0·25W & 0·5W 1Ω to 10MΩ.—4p. Metal Film 1W.2Ω to 10MΩ.—7p ea.

1N4148—4p. 1N4000—5p. 1N4000—7p. 1N4007—8p. BC107/8/9, BC147/8/9, BF157/8/9 & BF194 & 197—8p. BC177/8/9 & 307 class B—11p. 2" ceramic—21p. Post 10p. (Free over £4·00). Prices inclusive of VAT.

THE C. R. SUPPLY CO.
127, Chesterfield Rd., Sheffield S8.

SEMICONDUCTORS:— 1N914E 3p each £1·80/100, £13/1,000. 800v 1 amp (IN4000 equiv). 5p each, £4/100, £35/1,000. Zeners:— 2·2-36v 5p each, £4/100 (no mix), £4·50/100 (mix). C.P. Silicon Diodes:— 2p each, £1·30/100, £10/1,000, OA90/91 etc 4p each, £5/100. Ltd Qty. Branded Transistors:— BC212L 9p each, ZT 212 10p each, 2N2955 £1 each, 2N3054 40·40 each, 2N3710 £1·60 each, CZ11 Thermistor 20p each, 10 for £1·50. S.A.E. for lists. P+P 20p. Bale Electronics, "Wanock," Dalton, Lockerbie, Dumfriesshire.

TRANSISTORS, capacitors, resistors, diodes, pots, plugs and sockets etc. All top quality at 65 Railway Road, Leigh.

NOSTALGIA — COLLECTING

VINTAGE RADIO

1920 to 1950

Receivers, valves, components, service data, historical research, books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet. Full 1977 catalogue, 70p post paid.

TUDOR REED (Vintage Radio Services), 64, Broad Street, Staple Hill, Bristol, BS16 5NL. Tel. Bristol 565472.

SMALL ADS

The prepaid rate for classified advertisements is 17 pence per word (minimum 12 words), box number 40p extra. Semi-display setting £14·00 per single column inch (2·5cm). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.

2. The publishers reserve the right to refuse or withdraw any advertisement.

3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

VALVES

Radio – T.V. – Industrial – Transmitting
We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 2700 Types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves.

COX RADIO (SUSSEX) LTD.
Dept. P.W. The Parade, East Wittering, Sussex PO20 8BN
West Wittering 3023 (STD Code 024366)

SURPLUS TRANSISTOR Amplifier Modules 75p each. Mains transformers 20,000Ω/V DC, with leads and leather case, £8·00, plus 50p P&P. Ex GPO Cutters and Pliers, 75p each. Archer, 9 Pine Grove, Maidstone, Kent.

TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting via mains rewiring. Insulated Touch Plates. All with full instructions.
NEW! TSD300K—TOUCH ON/SWITCH and DIMMER combined. ONE touch plate to switch light on or off. Touch and hold to dim. Size 70x70x20—£4·95
TSB300K—TOUCHSWITCH. TWO touchplates. £3·67
TSA300K—AUTOMATIC TOUCHSWITCH
Stays on for preset time. £3·67

LD300K—LIGHTDIMMER KIT. £2·45

AY-5-1230 4-digit CLOCK/APPLIANCE Timer £4·99

LOW PRICES!		CMOS (Motorola)	
4000 18p	4013	55p	4040 87p
4001 18p	4015	91p	4049 48p
4002 18p	4016	37p	4050 48p
4007 18p	4017	91p	4501 28p
4011 18p	4023	37p	4510 58p
4012 17p	4025	17p	4585 135p

TRIACS 400V TO220 10A 50p 6A 40p 3A 30p 10A + 20p
Case Isolated tab: 74T 5 pin dil 30p
8·5A 70p Diac 25p 2N6027 (PUT) 34p
6·5A with trigger 80p 2N3055 36p

QUANTITY DISCOUNTS ON REQUEST
Add 8% VAT plus 25p P & P. Mail Order only to:

T. K. ELECTRONICS (PW)
196 Shudley Grange Road, London, W7 3LX.

ORCHARD ELECTRONICS

I.C.s TTL. C/Mos. Linear. Capacitors. Resistors. (E12) Sil./Rectifiers. Diodes. LED. Thyristors. Zeners. Voltage Reg. DIL Sockets. Bridge Rectifiers. Potentiometers. Presets. Triacs. Diac. Plugs. Sockets. Cable. Vero. Carefully selected range, excellent despatch service. Same day turn round. S.A.E. List. Suppliers to A.E.R.E. U.K.A.E.A. Governments Depts. Schools. Universities. Manufacturers. Export. Trade and enquiry. Join the professionals. Phone by 4 p.m. Goods out 1st class by 6 p.m. Try us and prove it!

ORCHARD ELECTRONICS
Flint House, High Street, Wallingford, Oxon. Telephone 0491-35329

Books and Publications

RADIO BOOK SERVICE

World Radio TV Handbook 1977	£5·75
The Cathode Ray Oscilloscope and its Uses	£3·50
T.V. & Radio Spot Faults Equiv. & Substitutes (Set)	£1·35
Radio Valve & Transistor Data (Set)	£1·35
Radio Antenna Manual for Long Dist. Reasons	£5·75
TV Electronic Novelty Circuits	£3·50
Radio Enthusiasts Handbook	£5·75
The Complete CB Radio Handbook	£5·95
Pop Group Organ Projects Handbook	£5·95
R.S.G Transistor Substitutes Handbook	£3·50
Integrated Circuits Equiv & Substitutes Handbook	£5·95
Manual of Electronic Circuits for the Hobbyist	£5·75
Postage 50p per book	

PRICES INCL. P&P. SEND S.A.E. FOR FULL LIST **NOTE NEW ADDRESS**
4 CHILCHESTER COURT, WICKHAM RD. BECKENHAM KENT. BR3 2DW

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £4·50, request free circuit diagram. Stamp brings details unique TV Publications (Ausepw), 76 Church Street, Larkhall, Lanarkshire.

YOU CAN'T HELP BUT MAKE MONEY. If you follow the planned and detailed information on how to start your own business rewinding ARMATURES, set out in the new manual which is profusely illustrated and leads you through easily understood stages of fault diagnosis, taking data, test procedures, laying down and rewinding, where to obtain work, how to cost jobs, etc. NO PREVIOUS ELECTRICAL KNOWLEDGE REQUIRED. Complete instruction manual, £4·00 plus P&P. CWO. Copper Supplies, 102 Parrswood Road, Withington, Manchester 20. DEPT. PWB.

Aerials

G2DYM SWL AERIALS

All aerials custom built by G2DYM, Ex-B.B.C. Transmitter and Aerial Engineer. CONSULT US for DESIGN & ADVISORY SERVICE, send large S.A.E., 3 9p stamps. We will quote you for Custom building aerials to your requirements, enclosing free a large aerial article.

LAMBDA ANTENNA STUD FARM
Whitebail, Wellington, Somerset

Ladders

LADDERS. Varnished. 20ft 9in extd. £25·33. Carr. £3·90. Aluminium alloy ext. up to $62\frac{1}{2}$ft. The Ladder Centre (WLS), Halesfield (1), Telford, Salop. Tel: 586644. Callers welcome.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Courses

BE A SUCCESSFUL TV ENGINEER. Join our Full-time Two-year College Diploma Course, specially designed to cover the examinations of the City and Guilds Radio, Television and Electronic Technician's Certificate. Full theoretical and practical instruction on all types of modern receivers including the latest colour sets. Enrolments are now under way for September 1977. Minimum entrance requirements are Senior Cambridge or 'O' level or equivalent in Mathematics and English. September includes a specialised Colour TV and FM Stereo servicing course, plus a 2nd year Technicians' Course. Contact us for free prospectus, THE PEMBRIDGE COLLEGE OF ELECTRONICS, Dept. PW, 34a Hereford Road, London W2 5AJ. Tel: 01-229 9117.

Business Available

SHREWSBURY. Thriving electronics and electrical trade business. Excellent trading position in this busy market town. Previous experience in the trade not essential. Easily run by husband and wife. Premises to be let on lease, £11,000 for goodwill, fixtures and fittings. S.A.V. FULL INFORMATION FROM COOPER AND GREEN, 3, Barker Street, Shrewsbury, Tel. 50081.

LARGE SUPPLIERS OF SERVICE SHEETS AND COLOUR MANUALS

TV, RADIO, TUNERS, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS.

ALL AT 75p EACH EXCEPT COLOUR TV & CAR RADIOS.

PLEASE STATE IF CIRCUIT WILL DO, IF SERVICE SHEET NOT IN STOCK. LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS OTHERWISE CANNOT BE ATTENDED TO. UNCROSSED P.O.'s OR CROSSED P.O.'s RETURNED IF SERVICE SHEETS ARE NOT AVAILABLE. ALL SERVICE MEN, PLEASE NOTE, WE OPERATE A SAME DAY RETURN SERVICE. ALL CLAIMS OF NON-DELIVERY MUST BE MADE WITHIN SEVEN DAYS. NO OVERSEAS MAIL PLEASE. MAIL ORDER ONLY OR 'PHONE 01-459 4892. FREE TV FAULT TRACING CHART OR TV LIST ON REQUEST WITH ORDER.

C. CARANNA, 71 BEAUFORT PARK, LONDON, NW11 6BX. NO CALLERS PLEASE

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc., 75p plus SAE. Colour TV Service Manuals on request. SAE, with enquiries to BTS, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

SERVICE SHEETS, radio, TV etc. 10,000 models. Catalogue 24p plus SAE with orders, enquiries. Telray, 154 Brook Street, Preston PR1 7HP.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc, With free fault-finding guide, from 50p and SAE. Catalogue 25p and SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

For Sale

BARGAIN PACK 1,000 assorted nuts and bolts, 2, 4 and 6 BA. NEW, Cadmium plated. Value at least £12. Only £4 inc. P&P. CWO. (UK only). Refund if not delighted. A.P., 171 Great Brays, Harlow, Essex CM18 6DT.

NEW ISSUES of "Practical Wireless" available from April 1974 edition up to date. Price 65p post free.—Bell's Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel (0423) 55885.

MAIL ORDER PROTECTION SCHEME

The Publishers of *Practical Wireless* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Practical Wireless* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as:—

'Direct response advertisements, displays or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.

SERVICE SHEETS — COLOUR TV SERVICE MANUALS

Service Sheets for Mono TV, Radios, Record Players and Tape Recorders 75p. Please send large Stamped Addressed Envelope.We can supply manuals for most makes of Colour Television Receivers including:

B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA FERGUSON H.M.V. MARCONI AND MANY MORE

Let us quote you. Please send a Stamped Addressed Envelope for a prompt reply. Also comprehensive T.V. repair manuals by J. M. Court. S.A.E. for details. MAIL ORDER ONLY.

G. T. TECHNICAL INFORMATION SERVICE

19 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA

Wanted

SURPLUS??? Turn it into cash. Phone: 0491 35529 (Oxon).

WANTED NEW Valves, transistors, I.Cs, amplifiers, receivers, televisions (Anything Useful) any quantity. Stan Willets, 37 High Street, West Bromwich. Tel: 021-553 0186.

WANTED—NEW VALVES, TRANSISTORS. TOP PRICES, popular types. Kensington Supplies (C), 367 Kensington Street, Bradford 8, Yorkshire.

Electrical

STYLI CARTRIDGES & AUDIO LEADS etc. For the best at keenest prices send S.A.E. for free illustrated list to: Pelstead Electronics (PW) Longley Lane, Gatley, Cheadle, Cheshire SK8 4EE.

Miscellaneous

AERIAL WIRE. High quality p.v.c. covered multi-strand copper, 50ft, 85p (15p); 75ft, £1·28 (17p); 100ft, £1·67 (25p); 150ft, £2·51 (34p); 200ft, £3·36 (39p); 250ft, £4·19 (46p); 300ft, £4·97 (49p): P&P in brackets. A.1 Radio Components, 19 The Borough, Canterbury, Kent CT1 2DR.

ARMATURE & COIL WINDING ENAMELLED COPPER WIRE
Only top quality materials supplied.
All orders dispatched within 24 hrs.

S.W.G.	1 lb reel	½ lb reel
10 to 19	£2·95	£1·60
20 to 29	£3·10	£1·70
30 to 34	£3·45	£1·90
35 to 40	£3·60	£2·10

All prices are inclusive of P. & P. in U.K.

COPPER SUPPLIES, 102 Parnewood Road, Withington, Manchester 20. Tel: 061-445 5752

CIRCOSOL. Solder-Through Coating prevents oxidation and fingerprint formation on printed circuit boards. Greatly eases Soldering of components by increasing "wetability". Gives a lasting professional finish. 99p per pack/P&P 20p. Audio Services, 13 Hale Street, Warrington WA2 7BU.

Bargain Boards

New equipment PCB's with 100% re-usable components.

1. Invertor 12 & 24V DC in 240V AC out untested new equipment £1·00
2. Boards with min. of 800V thyristor plastic transistor caps etc. All long leads. 50p
3. Boards with min. 2 × high speed plastic power TIP41A type good for Hi Fi O.P. 50p
4. Ex. equip. TO3 2N3055 type. 30p

Add 10p p & p. 20p overseas.

R. JONES SUPPLIES.
3, Centre Vale Close, Littleborough, Lancs. OL15 9EZ.

Miscellaneous

OUTSTANDING HI-FI FM TUNER, comprises 7 transistor superhet design with Varicap tuning, AFC. Latest silicon circuitry, full coverage 88-102MHz. Supplied built and tested with metal front, panel and instruction sheet. Only £9·95 plus 30p P&P. Gregg Electronics, 86-88 Parchmore Road, Thornton Heath, Surrey.

ENAMELLED COPPER WIRE

SWG	1 lb	½ lb	2oz
14-20	2·48	1·29	·68
21-29	2·68	1·39	·72
30-34	2·78	1·49	·76
35-40	2·98	1·59	·78

Inclusive of p&p and VAT.
SAE brings Catalogue of copper and resistance wires in all coverings.

THE SCIENTIFIC WIRE COMPANY
PO Box 30, London E4 9BW
Rep. Offices: 57 Conlingsby Gardens,

1 mm 9v P.C. POWER DRILL uses p.p. 9 Safe Reliable Guaranteed. 2-1 mm drills supplied. £3·95. c.w.o. P. E. LTD., Coedaben, Wrexham, Clwyd.

THE BRITISH RADIO TECHNICAL ADVISORY SERVICE and The British Telecommunication Equipment Servicing Centre for all makes of modern Transceivers, Receivers, details. s.a.e. GDZVM Projects, Yaesu Agents, Lambda, Whitebali, Wellington, Somerset.

SUPERB INSTRUMENTS CASES by Bazelli, manufactured from heavy duty 20 G. faced steel. Used hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 85p. Examples: width, depth, height, 8in × 5in × 3in, £1·70. 10in x 6in x 3in £2·42, 10in x 8in x 3in £3·02. 12in x 10in x 3in £3·68. 14in × 4in × 4in £2·98. 14in x 6in x 4in £2·97. 12in x 8 in x 4in £3·96. 7in x 7in x 6in £2·91. 8in x 10in x 6in £3·96. 12in x 8in x 7in £4·40. 12in x 12in x 7in £4·84. Plus 85p carriage and 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated). Bazelli, Dept. No. 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

RECHARGEABLE BATTERIES. 'AA' pencell (HP7), £1·26; Sub 'C', £1·29; 'C' (PH11), £2·38; 'D' (HP2), 201 Monmouth Drive, Sutton Coldfield, West Midlands. Tel: 021-354 9764. Callers to TLC, 32 Craven Street, Charing Cross, London WC2.

H. M. ELECTRONICS
27a FULWOOD ROAD, BROOMHILL, SHEFFIELD S10, S10.

BSC. CABINETS (illus'd).

METAL CASES
DRY TRANSFER LETTERING
Send 18p for leaflets (Refundable)
Trade enquiries invited

ALARM BUZZERS 3-12 VOLT Solid State Type ABT — £1·00 ea

MORSE PRACTICE OSCILLATORS Built-in Key M.P.O. 1 — £2·00 ea

MINIATURE PLUG-IN RELAYS (VARLEY) 12 or 24 v. d.c. 4A, c/o, dust covers — 40p ea

SPECIAL OFFER: 3 Relays for £1·00

VAT inclusive prices—please add 20p per Item p & p.

BB SUPPLIES (Dept. D), 67 Westcliff Road, Ramsgate, Kent, CT11 9NP

MAKE YOUR OWN PRINTED CIRCUITS

RUB-ON TRANSFERS—Starter pack (5 sheets, lines, pads, i.c. pads) £1·30. Spare sheets 27p.

FERRIC CHLORIDE—1 lb bag 70p (p.&p. 30p)*

SOLDERCON SOCKETS—100 65p. Quantity rates.

PLASTIC SUPPORTS—7 or 8 hole. 6p/pair.

TRANSISTOR TESTER—67 (p.&p. 30p)*

SAE lists, samples. P.&p. 15p/order except *.

P.K.G. ELECTRONICS

OAK LODGE, TANSLEY, DERBYSHIRE

100 RESISTORS 75p

1w 5% C/Film E 12—2·2M £1 (E12)

10 each of any value

C60 CASSETTES 30p	All Cassettes in Plastic	
C90 CASSETTES 45p	Case with Index and Screwed Assembly.	

All prices include VAT. Add Postage 10p in £1.

Send stamp envelope for free sample.

Quantity Discounts.	SALOP ELECTRONICS
10 Units 5%	23 WYLE COP
50 Units 7½	SHREWSBURY
100 Units 10%	Tel. 53286

SINTEL — FREE CATALOGUE BY RETURN

FOR BY RETURN DELIVERY

PHONE OXFORD

0865 49791

OR WRITE TO

SINTEL

P.O. BOX 75F

209 Cowley Road

OXFORD

BUILD THE TREASURE TRACER MK III Metal Locator

- Various tuning
- British's best selling metal locator kit
- Fitted with Faraday shield.
- Speaker and earphone operation
- 4,000 already sold
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete Kit £15·95 Post £1·20 + £1·31 VAT

Built & tested £20·95 Post £1·20 + £1·71 VAT

MINIKITS ELECTRONICS, 8a CLEVELAND ROAD, LONDON, E18 2AN (Mail order only)

£23 TYPE AO113

HIGH QUALITY AUDIO SIG GENERATOR

(A JOHN LINSLEY HOOD DESIGN)

IDEAL FOR HI FI TESTING.

Range 10Hz-100Khz. Sine/Square. Output 1V attenuated. Distortion below ·02%. 9V battery. Kit of parts £19·50. *Tax extra 8% P.P. & INS £1.

Other Instruments: T.H.D. Analyser, Milli V/mtr, F.M. Sig gen. P.S.V.O.-60V 1 amp. etc. SAE FOR LEAFLETS.

TELERADIO ELECTRONICS

325 Fore St. London. N.9. 01-807 3719

HOW'S THE QRM?

FREE DX from tiring whistles and CW interference, FAST, with a Tunable Audio Notch Filter. Easy kit includes ALL parts, case, printed circuit, screws etc, postage, instructions, money back assurance. MORE RARE DX for only £7·99. SEND TODAY.

CAMBRIDGE KITS

45 (PW) Old School Lane, Milton, Cambs.

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual designs. Prompt service. Send 25p for catalogue. From:

Ramar Constructor Services,
Masons Road, Stratford on Aven, Warwicka. Tel. 4878

NOTICE TO READERS

When replying to Classified Advertisements please ensure:

(A) That you have clearly stated your requirements.

(B) That you have enclosed the right remittance.

(C) That your name and address is written in block capitals, and

(D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

ELECTRONIC BROKERS

ELECTRONIC BROKERS LTD
49/53 Pancras Road
London NW1 2QB
Tel: 01-837 7781

Computer parts for hobby, experimental, educational and professional use.

FRESH STOCKS OF THE POPULAR CLARE-PENDAR ASCII KEYBOARD TYPE KB6 NOW TO HAND

ASCII-Coded TTL-compatible 4-bank alphanumeric keyboards with ROM encoder chip, strobed output, two-key rollover and debounce. Standard 7-bit ASCII code (no parity) Supplied complete with circuit diagrams and code chart.

SPECIFICATIONS

Power Supply: +5VDC +/− 5%, 150mA; −12VDC +/− 10% 10mA. *Output Logic Levels:* Data Bits 1 through 7 0v "0" 45V; 3·6v "1" 5·25V. *Fan Out* One standard TTL load. *Strobe:* 2·6v "1" 5·25V; 0v "0" 46V. *Fan Out:* 10 standard TTL loads. Strobe signal delay 10 milliseconds nominal to allow data to stabilise.

KB6: 56-station standard Teletype layout, AS RECOMMENDED FOR PRACTICAL WIRELESS VIDEO-WRITER PROJECT. *Price £39·50 + £1 P&P + 8% VAT (send £43·74).*

NEW ARRIVALS

FABULOUS NEW 96-STATION CRT DISPLAY KEYBOARDS. 8-bit ASCII code, upper and lower case output PLUS separate numeric pad. TTL Logic. Delayed strobe signal and two-key rollover feature. Mounted in attractive box, overall dimensions 20¼ × 7¼ × 3¼". *Price £65·00 + £3 carriage + 8% VAT (send £73·44).*

BCD-CODED 56-STATION KEYBOARD, brand new, upper and lower case outputs. Mounted on double PCB and set in attractive metal inset complete 8 indicator lamps and on/off switch. Dimensions 15¾ × 3¼ × 2¼". *Price £39·50 + £2 P&P + 8% VAT (send £44·42).* Also available, A few only of the above model WITHOUT ENCODING PCB PANEL. *Price £25·00 + £1·50 P&P + VAT (send £28·42).*

18-KEY CALCULATOR KEYBOARDS (0-9, CK + − × ÷ =). Make/break switches mounted on PCB. Overall dimensions 150 × 110 × 40mm. *Price £4 plus 50p P&P + VAT (Send £4·86p).*

JUST RECEIVED — SPECIAL PURCHASE OF DATA DYNAMICS MODEL 390 TELETYPE TERMINALS IN BRAND NEW CONDITION

TERMINALS — LARGE STOCKS AVAILABLE. ASR33 Teletype from £625·00. KSR33 Teletype from £435·00. ASR35 Teletype from £750·00. IBM731/8 Golfball Typewriter from £275·00.

SPECIAL OFFER

Cossor DIDS 401.2A Visual Display Units. 13 lines × 80 characters (8); × 45° screen 64 character repertoire with detachable ASCII keyboard (Control device required). **Bargain Price: £145·00.** Also available Cossor DIDS 402.2A, as above but incorporating control logic. **Price £395·00.**

FOR IBM 360 USERS. Sanders 720 Data Display System consisting of six VDUs, control unit and communications buffer. Complete with connecting cables and technical documentation. **Price £2,750·00.**

MINIATURE MATRIX PROGRAMME BOARDS: Brand new X-Y Matrix boards, with 3mm grating, 3 × 10 positions (1⅜" × 1") £4·00. P&P 40p.

MAGNETIC TAPES. Manufacturers surplus stocks, brand new in original sealed packing. ½" × 2400' £4·00 per reel. P&P extra.

NAB-centre metal 1" tape spools (10½" dia), in plastic canister. Min. order quantity 5 for £6·25 + £2·50 P&P + 8% VAT (Send £9·45).

"SUPER SPARK" Mk5

NEW ELECTRONIC IGNITION UNIT THAT SAVES MONEY AND IMPROVES PERFORMANCE

DIRECT FROM THE MAKERS

- ADAPTABLE TO + OR – EARTH AS REQUIRED
- REV. LIMITING CONTROL
- INSTANT REVERT SWITCH TO NORMAL IGNITION
- ON-OFF SWITCH TO IMMOBILIZE ENGINE
- EASY TO INSTALL
- FULLY GUARANTEED

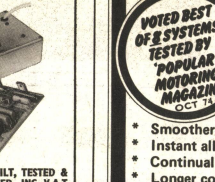

VALUE SUPREME!

Nothing extra to pay for

With Super Spark Mk. 5 you get all the advantages of electronic ignition for your car—year-round easier starting, fuel economy, better working life from the engine PLUS essential features which come as extras in other makes. Built from heavy duty components on improved circuit board, now in heavy gauge aluminium case 60° × 40° × 2°F with neon indicator and colour coded leads (approx. 27"). OVER 14,000 SUPER SPARK UNITS HAVE ALREADY BEEN SOLD. FOR DELIVERY BY RETURN. S.A.E. brings leaflet.

Made in U.K. by

STIRLING SOUND (Dept. PW97)

37 VANGUARD WAY, SHOEBURYNESS, ESSEX

Phone (03702) 5543

Shop—220-224 West Rd., Westcliff-on-Sea, Essex SS0 9DF

READY BUILT, TESTED & GUARANTEED, INC. V.A.T

£12.75

POST FREE IN U.K.

COMPLETE KIT GUARANTEED INC. V.A.T.

£10.50

POST FREE IN U.K.

J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln LN2 1JF **Tel: 20767**

100-A-100UA TUNING METER 1½ × 1¼in square, **90p.**
20 ASSORTED VARI-CAP DIODES, untested, **45p.**
MINIATURE 3-POLE 4-WAY SWITCHES, 20p each.
1in DIA. LUMINOUS DOME BUTTON, 75p each.
UNIJUNCTIONS, TIS43 type **20p**, MEU21 **22p**, MV4894 **22p**, GE4|D5E29 **22p.**
HEAVY DUTY DPDT TOGGLE SWITCHES, 40p each.
TEXAS SCR's, TIC47 200PIV 300mA. **18p** each.
PHONO SOCKETS, single **5p**, double **10p**, triple **15p**, quad **20p.**
200 ASSORTED RESISTORS ¼W, ⅓W **75p.**
100 ASSORTED POLYSTYRENE CAPACITORS, 57p.
100 MULLARD C280 CAPACITORS, assorted, **57p.**
PLASTIC BC108 OR BC212 TYPE BRANDED TRANSISTORS, 10 for 60p.
SILICON SOLAR CELLS 0·5V 5mA, **35p.**
ZN414 RADIO I.C., with data, **£1.**
TRANSFORMERS 240V A.C. input, type / 22V 1 amp **88p** (20p P. & P.); type 2 22V 300mA, 7V 1 amp, **99p** (20p P. & P.); type 2 12V 300mA, **88p** (15p P. & P.); type 4 9V 500mA, **88p** (20p P. & P.); type 5 50V 2 amp, 50V 500mA, **£3·50** (75p P. & P.) type 6 10V 1½ amp twice, 20V 1½ amp twice, **£4·50** (85p P. & P.).
TWO-PIN DIN SPEAKER SOCKETS, 10p, bank of 2 **18p.**
MINIATURE 8uF 350V.W. ELECTROLYTICS, 10 for 57p.
500YD REEL OF PVC 14-0048 CABLE, £3.
AUDIBLE ALARM SYSTEM, with transistors and I.C., 12V, **75p.**
TANTALUM BEAD CAPACITORS 0·1uF 35V.W., 0·33uF 35V.W., 1uF 35V.W., 2·2uF 35V.W., 4·7uF 35V.W., 5uF 25V.W., 6·8uF 25V.W., 6·8uF 35V.W., 10uF 25V.W., 15uF 20V.W., 20uF 6V.W., 22uF 16V.W., 33uF 25V.W, 47uF 6V.W., all **9p** each.
TOKO 5SH.H. ADJUSTABLE COILS FOR FILTERS, 18p each.
FERRANTI ZTX108 BRANDED TRANSISTORS, 6 for 50p.
POWER TRANSISTORS, OC25 **50p**, AD149 **60p**, BD112 **25p**, BD187 **35p**, BD207 **55p.**
WIDE BAND RADAR AMPLIFIERS, 10-100MHz untested with data, 5 for **57p.**
50 ASSORTED BC107-8-9 TRANSISTORS, untested, for **57p.**
OPTO ISOLATOR LINTRONIX IL-74, with data, **50p** each.
0·1uF 160 V.W. POLYESTOR CAPACITORS, 20p doz.
CA3089E I.F. I.C., £1·49 each.
FM FRONT END 88 TO 108MHz with details for conversion to aircraft band or 2 metres, **£3.**
10 ASSORTED MULTI-TURN TRIM-POTS for **60p.**
20 ASSORTED PHOTO AND DARLINGTON TRANSISTORS, untested for **£1.**
50 AC128 TRANSISTORS, branded but untested for **57p.**
Please add 20p for post and packing on orders under £2, unless otherwise stated. Overseas orders at cost.

Sparkrite mk2

Capacitive discharge electronic ignition kit

- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch.
Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as an anti-theft device. Includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service – 'phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.
IMPROVE PERFORMANCE & ECONOMY NOW
Note—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit, **£3·35** inc. V.A.T., p.& p.
E.D.A. 82 BATH STREET, WALSALL, WS1 3DE.

POST TODAY!

Quick installation
No engine modification required

Electronics Design Associates, Dept., P.W.9
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name .....

Address .....

	QUANTITY NEEDED
Mk. 2 DIY Ass. Kit @ £11.80	
Mk. 2 Ready Built Negative Earth @ £14.97	
Mk. 2 Ready Built Positive Earth @ £14.97	
Ignition Changeover switches @ £4.30	
R.P.M. Limit systems in above units @ £2.42	

I enclose cheque/PO's for £

Cheque No.

Send SAE if brochure only required.

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 37774

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS CASH/CHEQUE/P.O.s OR ACCREDITED BRANCH OF WORTH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. MINIMUM EXPORT ENQUIRIES WELCOME. ADD 25p TO ALL ORDERS UNDER £10-00. OVERSEAS ORDERS POSTAGE AT COST.

VAT Export orders are VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the end user.

We stock over 3000 items. It is not possible to list them all. Situated behind Watford Football Ground. Nearest Underground/Br. Rail Station Watford High Street. Open Monday to Saturday. Ample free car parking space available.

POLYESTER CAPACITORS: Axial lead type. (Values are in *pF*).
250V: 0·001, 0·002, 0·003, 0·005, 0·01, 0·02, 0·03, 0·04, 0·05, 0·06, 0·07, 0·08, 0·1p; 0·12, 0·15, 0·18, 0·2, 0·22, 0·25, 0·3, 0·33, 0·39, 0·4, 0·47, 0·5, 0·56, 0·6, 0·68, 0·7, 0·8, 0·82, 0·9, 1·0, 1·2, 1·5, 1·8, 2·0, 2·2, 2·5, 2·7, 3·0, 3·3, 3·9, 4·0, 4·7, 5·0, 5·6, 6·0, 6·8, 7·0, 8·2, 9·0, 10·0, 12·0, 15·0, 18·0, 20·0, 22·0, 25·0, 27·0, 30·0, 33·0, 39·0, 40·0, 47·0, 50·0, 56·0, 60·0, 68·0, 70·0, 82·0, 90·0, 100·0, 120·0, 150·0, 180·0, 200·0, 220·0, 250·0, 270·0, 300·0, 330·0, 390·0, 400·0, 470·0, 500·0, 560·0, 600·0, 680·0, 700·0, 820·0, 900·0, 1000·0, 1200·0, 1500·0, 1800·0, 2000·0, 2200·0, 2500·0, 2700·0, 3000·0, 3300·0, 3900·0, 4000·0, 4700·0, 5000·0, 5600·0, 6000·0, 6800·0, 7000·0, 8200·0, 9000·0, 10000·0, 12000·0, 15000·0, 18000·0, 20000·0, 22000·0, 25000·0, 27000·0, 30000·0, 33000·0, 39000·0, 40000·0, 47000·0, 50000·0, 56000·0, 60000·0, 68000·0, 70000·0, 82000·0, 90000·0, 100000·0, 120000·0, 150000·0, 180000·0, 200000·0, 220000·0, 250000·0, 270000·0, 300000·0, 330000·0, 390000·0, 400000·0, 470000·0, 500000·0, 560000·0, 600000·0, 680000·0, 700000·0, 820000·0, 900000·0, 1000000·0, 1200000·0, 1500000·0, 1800000·0, 2000000·0, 2200000·0, 2500000·0, 2700000·0, 3000000·0, 3300000·0, 3900000·0, 4000000·0, 4700000·0, 5000000·0, 5600000·0, 6000000·0, 6800000·0, 7000000·0, 8200000·0, 9000000·0, 10000000·0, 12000000·0, 15000000·0, 18000000·0, 20000000·0, 22000000·0, 25000000·0, 27000000·0, 30000000·0, 33000000·0, 39000000·0, 40000000·0, 47000000·0, 50000000·0, 56000000·0, 60000000·0, 68000000·0, 70000000·0, 82000000·0, 90000000·0, 100000000·0, 120000000·0, 150000000·0, 180000000·0, 200000000·0, 220000000·0, 250000000·0, 270000000·0, 300000000·0, 330000000·0, 390000000·0, 400000000·0, 470000000·0, 500000000·0, 560000000·0, 600000000·0, 680000000·0, 700000000·0, 820000000·0, 900000000·0, 1000000000·0, 1200000000·0, 1500000000·0, 1800000000·0, 2000000000·0, 2200000000·0, 2500000000·0, 2700000000·0, 3000000000·0, 3300000000·0, 3900000000·0, 4000000000·0, 4700000000·0, 5000000000·0, 5600000000·0, 6000000000·0, 6800000000·0, 7000000000·0, 8200000000·0, 9000000000·0, 10000000000·0, 12000000000·0, 15000000000·0, 18000000000·0, 20000000000·0, 22000000000·0, 25000000000·0, 27000000000·0, 30000000000·0, 33000000000·0, 39000000000·0, 40000000000·0, 47000000000·0, 50000000000·0, 56000000000·0, 60000000000·0, 68000000000·0, 70000000000·0, 82000000000·0, 90000000000·0, 100000000000·0, 120000000000·0, 150000000000·0, 180000000000·0, 200000000000·0, 220000000000·0, 250000000000·0, 270000000000·0, 300000000000·0, 330000000000·0, 390000000000·0, 400000000000·0, 470000000000·0, 500000000000·0, 560000000000·0, 600000000000·0, 680000000000·0, 700000000000·0, 820000000000·0, 900000000000·0, 1000000000000·0, 1200000000000·0, 1500000000000·0, 1800000000000·0, 2000000000000·0, 2200000000000·0, 2500000000000·0, 2700000000000·0, 3000000000000·0, 3300000000000·0, 3900000000000·0, 4000000000000·0, 4700000000000·0, 5000000000000·0, 5600000000000·0, 6000000000000·0, 6800000000000·0, 7000000000000·0, 8200000000000·0, 9000000000000·0, 10000000000000·0, 12000000000000·0, 15000000000000·0, 18000000000000·0, 20000000000000·0, 22000000000000·0, 25000000000000·0, 27000000000000·0, 30000000000000·0, 33000000000000·0, 39000000000000·0, 40000000000000·0, 47000000000000·0, 50000000000000·0, 56000000000000·0, 60000000000000·0, 68000000000000·0, 70000000000000·0, 82000000000000·0, 90000000000000·0, 100000000000000·0, 120000000000000·0, 150000000000000·0, 180000000000000·0, 200000000000000·0, 220000000000000·0, 250000000000000·0, 270000000000000·0, 300000000000000·0, 330000000000000·0, 390000000000000·0, 400000000000000·0, 470000000000000·0, 500000000000000·0, 560000000000000·0, 600000000000000·0, 680000000000000·0, 700000000000000·0, 820000000000000·0, 900000000000000·0, 1000000000000000·0, 1200000000000000·0, 1500000000000000·0, 1800000000000000·0, 2000000000000000·0, 2200000000000000·0, 2500000000000000·0, 2700000000000000·0, 3000000000000000·0, 3300000000000000·0, 3900000000000000·0, 4000000000000000·0, 4700000000000000·0, 5000000000000000·0, 5600000000000000·0, 6000000000000000·0, 6800000000000000·0, 7000000000000000·0, 8200000000000000·0, 9000000000000000·0, 10000000000000000·0, 12000000000000000·0, 15000000000000000·0, 18000000000000000·0, 20000000000000000·0, 22000000000000000·0, 25000000000000000·0, 27000000000000000·0, 30000000000000000·0, 33000000000000000·0, 39000000000000000·0, 40000000000000000·0, 47000000000000000·0, 50000000000000000·0, 56000000000000000·0, 60000000000000000·0, 68000000000000000·0, 70000000000000000·0, 82000000000000000·0, 90000000000000000·0, 100000000000000000·0, 120000000000000000·0, 150000000000000000·0, 180000000000000000·0, 200000000000000000·0, 220000000000000000·0, 250000000000000000·0, 270000000000000000·0, 300000000000000000·0, 330000000000000000·0, 390000000000000000·0, 400000000000000000·0, 470000000000000000·0, 500000000000000000·0, 560000000000000000·0, 600000000000000000·0, 680000000000000000·0, 700000000000000000·0, 820000000000000000·0, 900000000000000000·0, 1000000000000000000·0, 1200000000000000000·0, 1500000000000000000·0, 1800000000000000000·0, 2000000000000000000·0, 2200000000000000000·0, 2500000000000000000·0, 2700000000000000000·0, 3000000000000000000·0, 3300000000000000000·0, 3900000000000000000·0, 4000000000000000000·0, 4700000000000000000·0, 5000000000000000000·0, 5600000000000000000·0, 6000000000000000000·0, 6800000000000000000·0, 7000000000000000000·0, 8200000000000000000·0, 9000000000000000000·0, 10000000000000000000·0, 12000000000000000000·0, 15000000000000000000·0, 18000000000000000000·0, 20000000000000000000·0, 22000000000000000000·0, 25000000000000000000·0, 27000000000000000000·0, 30000000000000000000·0, 33000000000000000000·0, 39000000000000000000·0, 40000000000000000000·0, 47000000000000000000·0, 50000000000000000000·0, 56000000000000000000·0, 60000000000000000000·0, 68000000000000000000·0, 70000000000000000000·0, 82000000000000000000·0, 90000000000000000000·0, 100000000000000000000·0, 120000000000000000000·0, 150000000000000000000·0, 180000000000000000000·0, 200000000000000000000·0, 220000000000000000000·0, 250000000000000000000·0, 270000000000000000000·0, 300000000000000000000·0, 330000000000000000000·0, 390000000000000000000·0, 400000000000000000000·0, 470000000000000000000·0, 500000000000000000000·0, 560000000000000000000·0, 600000000000000000000·0, 680000000000000000000·0, 700000000000000000000·0, 820000000000000000000·0, 900000000000000000000·0, 1000000000000000000000·0, 1200000000000000000000·0, 1500000000000000000000·0, 1800000000000000000000·0, 2000000000000000000000·0, 2200000000000000000000·0, 2500000000000000000000·0, 2700000000000000000000·0, 3000000000000000000000·0, 3300000000000000000000·0, 3900000000000000000000·0, 4000000000000000000000·0, 4700000000000000000000·0, 5000000000000000000000·0, 5600000000000000000000·0, 6000000000000000000000·0, 6800000000000000000000·0, 7000000000000000000000·0, 8200000000000000000000·0, 9000000000000000000000·0, 10000000000000000000000·0, 12000000000000000000000·0, 15000000000000000000000·0, 18000000000000000000000·0, 20000000000000000000000·0, 22000000000000000000000·0, 25000000000000000000000·0, 27000000000000000000000·0, 30000000000000000000000·0, 33000000000000000000000·0, 39000000000000000000000·0, 40000000000000000000000·0, 47000000000000000000000·0, 50000000000000000000000·0, 56000000000000000000000·0, 60000000000000000000000·0, 68000000000000000000000·0, 70000000000000000000000·0, 82000000000000000000000·0, 90000000000000000000000·0, 100000000000000000000000·0, 120000000000000000000000·0, 150000000000000000000000·0, 180000000000000000000000·0, 200000000000000000000000·0, 220000000000000000000000·0, 250000000000000000000000·0, 270000000000000000000000·0, 300000000000000000000000·0, 330000000000000000000000·0, 390000000000000000000000·0, 400000000000000000000000·0, 470000000000000000000000·0, 500000000000000000000000·0, 560000000000000000000000·0, 600000000000000000000000·0, 680000000000000000000000·0, 700000000000000000000000·0, 820000000000000000000000·0, 900000000000000000000000·0, 1000000000000000000000000·0, 1200000000000000000000000·0, 1500000000000000000000000·0, 1800000000000000000000000·0, 2000000000000000000000000·0, 2200000000000000000000000·0, 2500000000000000000000000·0, 2700000000000000000000000·0, 3000000000000000000000000·0, 3300000000000000000000000·0, 3900000000000000000000000·0, 4000000000000000000000000·0, 4700000000000000000000000·0, 5000000000000000000000000·0, 5600000000000000000000000·0, 6000000000000000000000000·0, 6800000000000000000000000·0, 7000000000000000000000000·0, 8200000000000000000000000·0, 9000000000000000000000000·0, 10000000000000000000000000·0, 12000000000000000000000000·0, 15000000000000000000000000·0, 18000000000000000000000000·0, 20000000000000000000000000·0, 22000000000000000000000000·0, 25000000000000000000000000·0, 27000000000000000000000000·0, 30000000000000000000000000·0, 33000000000000000000000000·0, 39000000000000000000000000·0, 40000000000000000000000000·0, 47000000000000000000000000·0, 50000000000000000000000000·0, 56000000000000000000000000·0, 60000000000000000000000000·0, 68000000000000000000000000·0, 70000000000000000000000000·0, 82000000000000000000000000·0, 90000000000000000000000000·0, 100000000000000000000000000·0, 120000000000000000000000000·0, 150000000000000000000000000·0, 180000000000000000000000000·0, 200000000000000000000000000·0, 220000000000000000000000000·0, 250000000000000000000000000·0, 270000000000000000000000000·0, 300000000000000000000000000·0, 330000000000000000000000000·0, 390000000000000000000000000·0, 400000000000000000000000000·0, 470000000000000000000000000·0, 500000000000000000000000000·0, 560000000000000000000000000·0, 600000000000000000000000000·0, 680000000000000000000000000·0, 700000000000000000000000000·0, 820000000000000000000000000·0, 900000000000000000000000000·0, 1000000000000000000000000000·0, 1200000000000000000000000000·0, 1500000000000000000000000000·0, 1800000000000000000000000000·0, 2000000000000000000000000000·0, 2200000000000000000000000000·0, 2500000000000000000000000000·0, 2700000000000000000000000000·0, 3000000000000000000000000000·0, 3300000000000000000000000000·0, 3900000000000000000000000000·0, 4000000000000000000000000000·0, 4700000000000000000000000000·0, 5000000000000000000000000000·0, 5600000000000000000000000000·0, 6000000000000000000000000000·0, 6800000000000000000000000000·0, 7000000000000000000000000000·0, 8200000000000000000000000000·0, 9000000000000000000000000000·0, 10000000000000000000000000000·0, 12000000000000000000000000000·0, 15000000000000000000000000000·0, 18000000000000000000000000000·0, 20000000000000000000000000000·0, 22000000000000000000000000000·0, 25000000000000000000000000000·0, 27000000000000000000000000000·0, 30000000000000000000000000000·0, 33000000000000000000000000000·0, 39000000000000000000000000000·0, 40000000000000000000000000000·0, 47000000000000000000000000000·0, 50000000000000000000000000000·0, 56000000000000000000000000000·0, 60000000000000000000000000000·0, 68000000000000000000000000000·0, 70000000000000000000000000000·0, 82000000000000000000000000000·0, 90000000000000000000000000000·0, 100000000000000000000000000000·0, 120000000000000000000000000000·0, 150000000000000000000000000000·0, 180000000000000000000000000000·0, 200000000000000000000000000000·0, 220000000000000000000000000000·0, 250000000000000000000000000000·0, 270000000000000000000000000000·0, 300000000000000000000000000000·0, 330000000000000000000000000000·0, 390000000000000000000000000000·0, 400000000000000000000000000000·0, 470000000000000000000000000000·0, 500000000000000000000000000000·0, 560000000000000000000000000000·0, 600000000000000000000000000000·0, 680000000000000000000000000000·0, 700000000000000000000000000000·0, 820000000000000000000000000000·0, 900000000000000000000000000000·0, 1000000000000000000000000000000·0, 1200000000000000000000000000000·0, 1500000000000000000000000000000·0, 1800000000000000000000000000000·0, 2000000000000000000000000000000·0, 2200000000000000000000000000000·0, 2500000000000000000000000000000·0, 2700000000000000000000000000000·0, 3000000000000000000000000000000·0, 3300000000000000000000000000000·0, 3900000000000000000000000000000·0, 4000000000000000000000000000000·0, 4700000000000000000000000000000·0, 5000000000000000000000000000000·0, 5600000000000000000000000000000·0, 6000000000000000000000000000000·0, 6800000000000000000000000000000·0, 7000000000000000000000000000000·0, 8200000000000000000000000000000·0, 9000000000000000000000000000000·0, 10000000000000000000000000000000·0, 12000000000000000000000000000000·0, 15000000000000000000000000000000·0, 18000000000000000000000000000000·0, 20000000000000000000000000000000·0, 22000000000000000000000000000000·0, 25000000000000000000000000000000·0, 27000000000000000000000000000000·0, 30000000000000000000000000000000·0, 33000000000000000000000000000000·0, 39000000000000000000000000000000·0, 40000000000000000000000000000000·0, 47000000000000000000000000000000·0, 50000000000000000000000000000000·0, 56000000000000000000000000000000·0, 60000000000000000000000000000000·0, 68000000000000000000000000000000·0, 70000000000000000000000000000000·0, 82000000000000000000000000000000·0, 90000000000000000000000000000000·0, 100000000000000000000000000000000·0, 120000000000000000000000000000000·0, 150000000000000000000000000000000·0, 180000000000000000000000000000000·0, 200000000000000000000000000000000·0, 220000000000000000000000000000000·0, 250000000000000000000000000000000·0, 270000000000000000000000000000000·0, 300000000000000000000000000000000·0, 330000000000000000000000000000000·0, 390000000000000000000000000000000·0, 400000000000000000000000000000000·0, 470000000000000000000000000000000·0, 500000000000000000000000000000000·0, 560000000000000000000000000000000·0, 600000000000000000000000000000000·0, 680000000000000000000000000000000·0, 700000000000000000000000000000000·0, 820000000000000000000000000000000·0, 900000000000000000000000000000000·0, 1000000000000000000000000000000000·0, 1200000000000000000000000000000000·0, 1500000000000000000000000000000000·0, 1800000000000000000000000000000000·0, 2000000000000000000000000000000000·0, 2200000000000000000000000000000000·0, 2500000000000000000000000000000000·0, 2700000000000000000000000000000000·0, 3000000000000000000000000000000000·0, 3300000000000000000000000000000000·0, 3900000000000000000000000000000000·0, 4000000000000000000000000000000000·0, 4700000000000000000000000000000000·0, 5000000000000000000000000000000000·0, 5600000000000000000000000000000000·0, 6000000000000000000000000000000000·0, 6800000000000000000000000000000000·0, 7000000000000000000000000000000000·0, 8200000000000000000000000000000000·0, 9000000000000000000000000000000000·0, 10000000000000000000000000000000000·0, 12000000000000000000000000000000000·0, 15000000000000000000000000000000000·0, 18000000000000000000000000000000000·0, 20000000000000000000000000000000000·0, 22000000000000000000000000000000000·0, 25000000000000000000000000000000000·0, 27000000000000000000000000000000000·0, 30000000000000000000000000000000000·0, 33000000000000000000000000000000000·0, 39000000000000000000000000000000000·0, 40000000000000000000000000000000000·0, 47000000000000000000000000000000000·0, 50000000000000000000000000000000000·0, 56000000000000000000000000000000000·0, 60000000000000000000000000000000000·0, 68000000000000000000000000000000000·0, 70000000000000000000000000000000000·0, 82000000000000000000000000000000000·0, 90000000000000000000000000000000000·0, 100000000000000000000000000000000000·0, 120000000000000000000000000000000000·0, 150000000000000000000000000000000000·0, 180000000000000000000000000000000000·0, 200000000000000000000000000000000000·0, 220000000000000000000000000000000000·0, 250000000000000000000000000000000000·0, 270000000000000000000000000000000000·0, 300000000000000000000000000000000000·0, 330000000000000000000000000000000000·0, 390000000000000000000000000000000000·0, 400000000000000000000000000000000000·0, 470000000000000000000000000000000000·0, 500000000000000000000000000000000000·0, 560000000000000000000000000000000000·0, 600000000000000000000000000000000000·0, 680000000000000000000000000000000000·0, 700000000000000000000000000000000000·0, 820000000000000000000000000000000000·0, 900000000000000000000000000000000000·0, 1000000000000000000000000000000000000·0, 1200000000000000000000000000000000000·0, 1500000000000000000000000000000000000·0, 1800000000000000000000000000000000000·0, 2000000000000000000000000000000000000·0, 2200000000000000000000000000000000000·0, 2500000000000000000000000000000000000·0, 2700000000000000000000000000000000000·0, 3000000000000000000000000000000000000·0, 3300000000000000000000000000000000000·0, 3900000000000000000000000000000000000·0, 4000000000000000000000000000000000000·0, 4700000000000000000000000000000000000·0, 5000000000000000000000000000000000000·0, 5600000000000000000000000000000000000·0, 6000000000000000000000000000000000000·0, 6800000000000000000000000000000000000·0, 7000000000000000000000000000000000000·0, 8200000000000000000000000000000000000·0, 9000000000000000000000000000000000000·0, 10000000000000000000000000000000000000·0, 12000000000000000000000000000000000000·0, 15000000000000000000000000000000000000·0, 18000000000000000000000000000000000000·0, 20000000000000000000000000000000000000·0, 22000000000000000000000000000000000000·0, 25000000000000000000000000000000000000·0, 27000000000000000000000000000000000000·0, 30000000000000000000000000000000000000·0, 33000000000000000000000000000000000000·0, 39000000000000000000000000000000000000·0, 40000000000000000000000000000000000000·0, 47000000000000000000000000000000000000·0, 50000000000000000000000000000000000000·0, 56000000000000000000000000000000000000·0, 60000000000000000000000000000000000000·0, 68000000000000000000000000000000000000·0, 70000000000000000000000000000000000000·0, 82000000000000000000000000000000000000·0, 90000000000000000000000000000000000000·0, 100000000000000000000000000000000000000·0, 120000000000000000000000000000000000000·0, 150000000000000000000000000000000000000·0, 180000000000000000000000000000000000000·0, 200000000000000000000000000000000000000·0, 220000000000000000000000000000000000000·0, 250000000000000000000000000000000000000·0, 270000000000000000000000000000000000000·0, 300000000000000000000000000000000000000·0, 330000000000000000000000000000000000000·0, 390000000000000000000000000000000000000·0, 400000000000000000000000000000000000000·0, 470000000000000000000000000000000000000·0, 500000000000000000000000000000000000000·0, 560000000000000000000000000000000000000·0, 600000000000000000000000000000000000000·0, 680000000000000000000000000000000000000·0, 700000000000000000000000000000000000000·0, 820000000000000000000000000000000000000·0, 900000000000000000000000000000000000000·0, 1000000000000000000000000000000000000000·0, 1200000000000000000000000000000000000000·0, 1500000000000000000000000000000000000000·0, 1800000000000000000000000000000000000000·0, 2000000000000000000000000000000000000000·0, 2200000000000000000000000000000000000000·0, 2500000000000000000000000000000000000000·0, 2700000000000000000000000000000000000000·0, 3000000000000000000000000000000000000000·0, 3300000000000000000000000000000000000000·0, 3900000000000000000000000000000000000000·0, 4000000000000000000000000000000000000000·0, 4700000000000000000000000000000000000000·0, 5000000000000000000000000000000000000000·0, 5600000000000000000000000000000000000000·0, 6000000000000000000000000000000000000000·0, 6800000000000000000000000000000000000000·0, 7000000000000000000000000000000000000000·0, 8200000000000000000000000000000000000000·0, 9000000000000000000000000000000000000000·0, 10000000000000000000000000000000000000000·0, 12000000000000000000000000000000000000000·0, 15000000000000000000000000000000000000000·0, 18000000000000000000000000000000000000000·0, 20000000000000000000000000000000000000000·0, 22000000000000000000000000000000000000000·0, 25000000000000000000000000000000000000000·0, 27000000000000000000000000000000000000000·0, 30000000000000000000000000000000000000000·0, 33000000000000000000000000000000000000000·0, 39000000000000000000000000000000000000000·0, 40000000000000000000000000000000000000000·0, 47000000000000000000000000000000000000000·0, 50000000000000000000000000000000000000000·0, 56000000000000000000000000000000000000000·0, 60000000000000000000000000000000000000000·0, 68000000000000000000000000000000000000000·0, 70000000000000000000000000000000000000000·0, 82000000000000000000000000000000000000000·0, 90000000000000000000000000000000000000000·0, 100000000000000000000000000000000000000000·0, 120000000000000000000000000000000000000000·0, 150000000000000000000000000000000000000000·0, 180000000000000000000000000000000000000000·0, 200000000000000000000000000000000000000000·0, 220000000000000000000000000000000000000000·0, 250000000000000000000000000000000000000000·0, 270000000000000000000000000000000000000000·0, 300000000000000000000000000000000000000000·0, 330000000000000000000000000000000000000000·0, 390000000000000000000000000000000000000000·0, 400000000000000000000000000000000000000000·0, 470000000000000000000000000000000000000000·0, 500000000000000000000000000000000000000000·0, 560000000000000000000000000000000000000000·0, 600000000000000000000000000000000000000000·0, 680000000000000000000000000000000000000000·0, 700000000000000000000000000000000000000000·0, 820000000000000000000000000000000000000000·0, 900000000000000000000000000000000000000000·0, 1000000000000000000000000000000000000000000·0, 1200000000000000000000000000000000000000000·0, 1500000000000000000000000000000000000000000·0, 1800000000000000000000000000000000000000000·0, 2000000000000000000000000000000000000000000·0, 2200000000000000000000000000000000000000000·0, 2500000000000000000000000000000000000000000·0, 2700000000000000000000000000000000000000000·0, 3000000000000000000000000000000000000000000·0, 3300000000000000000000000000000000000000000·0, 3900000000000000000000000000000000000000000·0, 4000000000000000000000000000000000000000000·0, 4700000000000000000000000000000000000000000·0, 5000000000000000000000000000000000000000000·0, 5600000000000000000000000000000000000000000·0, 6000000000000000000000000000000000000000000·0, 6800000000000000000000000000000000000000000·0, 7000000000000000000000000000000000000000000·0, 8200000000000000000000000000000000000000000·0, 9000000000000000000000000000000000000000000·0, 10000000000000000000000000000000000000000000·0, 12000000000000000000000000000000000000000000·0, 15000000000000000000000000000000000000000000·0, 18000000000000000000000000000000000000000000·0, 20000000000000000000000000000000000000000000·0, 22000000000000000000000000000000000000000000·0, 25000000000000000000000000000000000000000000·0, 27000000000000000000000000000000000000000000·0, 30000000000000000000000000000000000000000000·0, 33000000000000000000000000000000000000000000·0, 39000000000000000000000000000000000000000000·0, 40000000000000000000000000000000000000000000·0, 47000000000000000000000000000000000000000000·0, 50000000000000000000000000000000000000000000·0, 56000000000000000000000000000000000000000000·0, 60000000000000000000000000000000000000000000·0, 68000000000000000000000000000000000000000000·0, 70000000000000000000000000000000000000000000·0, 82000000000000000000000000000000000000000000·0, 90000000000000000000000000000000000000000000·0, 100000000000000000000000000000000000000000000·0, 120000000000000000000000000000000000000000000·0, 150000000000000000000000000000000000000000000·0, 180000000000000000000000000000000000000000000·0, 200000000000000000000000000000000000000000000·0, 220000000000000000000000000000000000000000000·0, 250000000000000000000000000000000000000000000·0, 270000000000000000000000000000000000000000000·0, 300000000000000000000000000000000000000000000·0, 330000000000000000000000000000000000000000000·0, 390000000000000000000000000000000000000000000·0, 400000000000000000000000000000000000000000000·0, 470000000000000000000000000000000000000000000·0, 500000000000000000000000000000000000000000000·0, 560000000000000000000000000000000000000000000·0, 600000000000000000000000000000000000000000000·0, 680000000000000000000000000000000000000000000·0, 700000000000000000000000000000000000000000000·0, 820000000000000000000000000000000000000000000·0, 900000000000000000000000000000000000000000000·0, 1000000000000000000000000000000000000000000000·0, 1200000000000000000000000000000000000000000000·0, 1500000000000000000000000000000000000000000000·0, 1800000000000000000000000000000000000000000000·0, 2000000000000000000000000000000000000000000000·0, 2200000000000000000000000000000000000000000000·0, 2500000000000000000000000000000000000000000000·0, 2700000000000000000000000000000000000000000000·0, 3000000000000000000000000000000000000000000000·0, 3300000000000000000000000000000000000000000000·0, 3900000000000000000000000000000000000000000000·0, 4000000000000000000000000000000000000000000000·0, 4700000000000000000000000000000000000000000000·0, 5000000000000000000000000000000000000000000000·0, 5600000000000000000000000000000000000000000000·0, 6000000000000000000000000000000000000000000000·0, 6800000000000000000000000000000000000000000000·0, 7000000000000000000000000000000000000000000000·0, 8200000000000000000000000000000000000000000000·0, 9000000000000000000000000000000000000000000000·0, 10000000000000000000000000000000000000000000000·0, 12000000000000000000000000000000000000000000000·0, 15000000000000000000000000000000000000000000000·0, 18000000000000000000000000000000000000000000000·0, 20000000000000000000000000000000000000000000000·0, 22000000000000000000000000000000000000000000000·0, 25000000000000000000000000000000000000000000000·0, 27000000000000000000000000000000000000000000000·0, 30000000000000000000000000000000000000000000000·0, 33000000000000000000000000000000000000000000000·0, 39000000000000000000000000000000000000000000000·0, 40000000000000000000000000000000000000000000000·0, 47000000000000000000000000000000000000000000000·0, 50000000000000000000000000000000000000000000000·0, 56000000000000000000000000000000000000000000000·0, 60000000000000000000000000000000000000000000000·0, 68000000000000000000000000000000000000000000000·0, 70000000000000000000000000000000000000000000000·0, 82000000000000000000000000000000000000000000000·0, 90000000000000000000000000000000000000000000000·0, 100000000000000000000000000000000000000000000000·0, 120000000000000000000000000000000000000000000000·0, 150000000000000000000000000000000000000000000000·0, 180000000000000000000000000000000000000000000000·0, 200000000000000000000000000000000000000000000000·0, 220000000000000000000000000000000000000000000000·0, 250000000000000000000000000000000000000000000000·0, 270000000000000000000000000000000000000000000000·0, 300000000000000000000000000000000000000000000000·0, 330000000000000000000000000000000000000000000000·0, 390000000000000000000000000000000000000000000000·0, 400000000000000000000000000000000000000000000000·0, 470000000000000000000000000000000000000000000000·0, 500000000000000000000000000000000000000000000000·0, 560000000000000000000000000000000000000000000000·0, 600000000000000000000000000000000000000000000000·0, 680000000000000000000000000000000000000000000000·0, 700000000000000000000000000000000000000000000000·0, 820000000000000000000000000000000000000000000000·0, 900000000000000000000000000000000000000000000000·0, 1000000000000000000000000000000000000000000000000·0, 1200000000000000000000000000000000000000000000000·0, 1500000000000000000000000000000000000000000000000·0, 1800000000000000000000000000000000000000000000000·0, 2000000000000000000000000000000000000000000000000·0, 2200000000000000000000000000000000000000000000000·0, 2500000000000000000000000000000000000000000000000·0, 2700000000000000000000000000000000000000000000000·0, 3000000000000000000000000000000000000000000000000·0, 3300000000000000000000000000000000000000000000000·0, 3900000000000000000000000000000000000000000000000·0, 4000000000000000000000000000000000000000000000000·0, 4700000000000000000000000000000000000000000000000·0, 5000000000000000000000000000000000000000000000000·0, 5600000000000000000000000000000000000000000000000·0, 6000000000000000000000000000000000000000000000000·0, 6800000000000000000000000000000000000000000000000·0, 7000000000000000000000000000000000000000000000000·0, 8200000000000000000000000000000000000000000000000·0, 9000000000000000000000000000000000000000000000000·0, 10000000000000000000000000000000000000000000000000·0, 12000000000000000000000000000000000000000000000000·0, 15000000000000000000000000000000000000000000000000·0, 18000000000000000000000000000000000000000000000000·0, 20000000000000000000000000000000000000000000000000·0, 22000000000000000000000000000000000000000000000000·0, 25000000000000000000000000000000000000000000000000·0, 27000000000000000000000000000000000000000000000000·0, 30000000000000000000000000000000000000000000000000·0, 33000000000000000000000000000000000000000000000000·0, 39000000000000000000000000000000000000000000000000·0, 40000000000000000000000000000000000000000000000000·0, 47000000000000000000000000000000000000000000000000·0, 50000000000000000000000000000000000000000000000000·0, 56000000000000000000000000000000000000000000000000·0, 60000000000000000000000000000000000000000000000000·0, 68000000000000000000000000000000000000000000000000·0, 70000000000000000000000000000000000000000000000000·0, 82000000000000000000000000000000000000000000000000·0, 90000000000000000000000000000000000000000000000000·0, 100000000000000000000000000000000000000000000000000·0, 120000000000000000000000000000000000000000000000000·0, 150000000000000000000000000000000000000000000000000·0, 180000000000000000000000000000000000000000000000000·0, 200000000000000000000000000000000000000000000000000·0, 220000000000000000000000000000000000000000000000000·0, 250000000000000000000000000000000000000000000000000·0, 270000000000000000000000000000000000000000000000000·0, 300000000000000000000000000000000000000000000000000·0, 330000000000000000000000000000000000000000000000000·0, 390000000000000000000000000000000000000000000000000·0, 400000000000000000000000000000000000000000000000000·0, 470000000000000000000000000000000000000000000000000·0, 500000000000000000000000000000000000000000000000000·0, 560000000000000000000000000000000000000000000000000·0, 600000000000000000000000000000000000000000000000000·0, 680000000000000000000000000000000000000000000000000·0, 700000000000000000000000000000000000000000000000000·0, 820000000000000000000000000000000000000000000000000·0, 900000000000000000000000000000000000000000000000000·0, 1000000000000000000000000000000000000000000000000000·0, 1200000000000000000000000000000000000000000000000000·0, 1500000000000000000000000000000000000000000000000000·0, 1800000000000000000000000000000000000000000000000000·0, 2000000000000000000000000000000000000000000000000000·0, 2200000000000000000000000000000000000000000000000000·0, 2500000000000000000000000000000000000000000000000000·0, 2700000000000000000000000000000000000000000000000000·0, 3000000000000000000000000000000000000000000000000000·0, 3300000000000000000000000000000000000000000000000000·0, 3900000000000000000000000000000000000000000000000000·0, 4000000000000000000000000000000000000000000000000000·0, 4700000000000000000000000000000000000000000000000000·0, 5000000000000000000000000000000000000000000000000000·0, 5600000000000000000000000000000000000000000000000000·0, 6000000000000000000000000000000000000000000000000000·0, 6800000000000000000000000000000000000000000000000000·0, 7000000000000000000000000000000000000000000000000000·0, 8200000000000000000000000000000000000000000000000000·0, 9000000000000000000000000000000000000000000000000000·0, 10000000000000000000000000000000000000000000000000000·0, 12000000000000000000000000000000000000000000000000000·0, 15000000000000000000000000000000000000000000000000000·0, 18000000000000000000000000000000000000000000000000000·0, 20000000000000000000000000000000000000000000000000000·0, 22000000000000000000000000000000000000000000000000000·0, 25000000000000000000000000000000000000000000000000000·0, 27000000000000000000000000000000000000000000000000000·0, 30000000000000000000000000000000000000000000000000000·0, 33000000000000000000000000000000000000000000000000000·0, 39000000000000000000000000000000000000000000000000000·0, 40000000000000000000000000000000000000000000000000000·0, 47000000000000000000000000000000000000000000000000000·0, 50000000000000000000000000000000000000000000000000000·0, 56000000000000000000000000000000000000000000000000000·0, 60000000000000000000000000000000000000000000000000000·0, 68000000000000000000000000000000000000000000000000000·0, 70000000000000000000000000000000000000000000000000000·0, 82000000000000000000000000000000000000000000000000000·0, 90000000000000000000000000000000000000000000000000000·0, 100000000000000000000000000000000000000000000000000000·0, 120000000000000000000000000000000000000000000000000000·0, 150000000000000000000000000000000000000000000000000000·0, 180000000000000000000000000000000000000000000000000000·0, 200000000000000000000000000000000000000000000000000000·0, 220000000000000000000000000000000000000000000000000000·0, 250000000000000000000000000000000000000000000000000000·0, 270000000000000000000000000000000000000000000000000000·0, 300000000000000000000000000000000000000000000000000000·0, 330000000000000000000000000000000000000000000000000000·0, 390000000000000000000000000000000000000000000000000000·0, 400000000000000000000000000000000000000000000000000000·0, 470000000000000000000000000000000000000000000000000000·0, 500000000000000000000000000000000000000000000000000000·0, 560000000000000000000000000000000000000000000000000000·0, 600000000000000000000000000000000000000000000000000000·0, 680000000000000000000000000000000000000000000000000000·0, 700000000000000000000000000000000000000000000000000000·0, 820000000000000000000000000000000000000000000000000000·0, 900000000000000000000000000000000000000000000000000000·0, 1000000000000000000000000000000000000000000000000000000·0, 1200000000000000000000000000000000000000000000000000000·0, 1500000000000000000000000000000000000000000000000000000·0, 1800000000000000000000000000000000000000000000000000000·0, 2000000000000000000000000000000000000000000000000000000·0, 2200000000000000000000000000000000000000000000000000000·0, 2500000000000000000000000000000000000000000000000000000·0, 2700000000000000000000000000000000000000000000000000000·0, 3000000000000000000000000000000000000000000000000000000·0, 3300000000000000000000000000000000000000000000000000000·0, 3900000000000000000000000000000000000000000000000000000·0, 4000000000000000000000000000000000000000000000000000000·0, 4700000000000000000000000000000000000000000000000000000·0, 5000000000000000000000000000000000000000000000000000000·0, 5600000000000000000000000000000000000000000000000000000·0, 6000000000000000000000000000000000000000000000000000000·0, 6800000000000000000000000000000000000000000000000000000·0, 7000000000000000000000000000000000000000000000000000000·0, 8200000000000000000000000000000000000000000000000000000·0, 9000000000000000000000000000000000000000000000000000000·0, 10000000000000000000000000000000000000000000000000000000·0, 12000000000000000000000000000000000000000000000000000000·0, 15000000000000000000000000000000000000000000000000000000·0, 18000000000000000000000000000000000000000000000000000000·0, 20000000000000000000000000000000000000000000000000000000·0, 22000000000000000000000000000000000000000000000000000000·0, 25000000000000000000000000000000000000000000000000000000·0, 27000000000000000000000000000000000000000000000000000000·0, 30000000000000000000000000000000000000000000000000000000·0, 33000000000000000000000000000000000000000000000000000000·0, 39000000000000000000000000000000000000000000000000000000·0, 40000000000000000000000000000000000000000000000000000000·0, 47000000000

WATFORD ELECTRONICS

(tinued from opposite side)

s	15p
60p	18p
80p	18p
10p	20p
20p	20p
14p	24p
16p	24p
8p	24p
5p	24p
8p	24p
10p	24p
8p	24p
5p	24p
5p	24p
5

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 6403
Open all day Saturday

AC/DC TAUT SUSPENSION MULTIMETERS (Made in USSR)

TYPE	U4312	U4313	U4315
Sensitivity D.C.	667 o.p.v.	20,000 o.p.v.	20,000 o.p.v.
Sensitivity A.C.	667 o.p.v.	2,000 o.p.v.	2,000 o.p.v.
D.C. Current	300 μA-6A	50μA-2·5A	50μA-2·5A
A.C. Current	1·5mA-6A	0·6mA-1·5A	0·5mA-2·5A
D.C. Volts	75mV-600V	75mV-600V	75mV-1000V
A.C. Volts	300mV-600V	15V-600V	1V-1000V
Resistance	0·02-3kΩ	1K-1M	300Ω-500kΩ
Capacity	—	0·5μF	0·5μF
Accuracy	1½ D.C., 1·5% A.C.	1·5% D.C., 2·5% A.C.	2·5% D.C., 4% A.C.

Price complete with pressed steel carrying case and test leads. **£14·50** **£17·50** **£14·95**

TYPES U4313 & U4313 PROVIDED WITH ANTI-PARALLAX MIRROR SCALES

TYPE U4324

Sensitivity:	20,000Ω/V D.C. 4,000Ω/V A.C.
D.C. Current:	0·06-0·6-60-600mA-3A
A.C. Current:	0·3-3-30-300mA-3A
D.C. Voltage:	0·6-1·2-3-12-30-60-120-600-1200V
A.C. Voltage:	3-6-15-60-150-300-600-900V
Resistance:	500Ω-5-50-500kΩ
Accuracy:	D.C. 2·5%; A.C. 4% (of F.S.D.)

PRICE complete with test leads and fibreboard storage case **£14·50**

TYPE U4341

Sensitivity:
16700Ω/V D.C.,
3300V A.C.

Ranges:
D.C. current: 0·06-0·6-6-60-600mA.

A.C. current 0·3-3-30-300mA

D.C. Voltage: 0·3-1·5-6-30-60-150-300-600V

Resistance: 2-20-200kΩ-2MΩ

Transistor collector cut-off current 60μA

Transistor D.C. current gain in two ranges 10-250

Accuracy: 2·5% D.C. 4·5% A.C. 5% D.C. current gain

Power supplies: 4·5V battery (Eveready 1289)

Complete with steel carrying case, test lead, battery and instruction manual **£14·50**

NO OVERLOAD PROTECTION IS INCORPORATED IN THESE INSTRUMENTS

THE ABOVE PRICES ARE EXCLUSIVE OF VAT (at present 8%) HANDLING AND POSTAGE CHARGES £1·25 PER INSTRUMENT

OUR NEW 1976/1977 **CATALOGUE** IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR £0·30

TECHNICAL TRAINING IN ELECTRONICS TELEVISION AND RADIO SERVICING

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained person. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City & Guilds Certificates:
Telecommunications Technicians
Radio, TV, Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
MPT Radio Communications Certificate

Diploma Courses:
Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools 1/9/77

Dept. No. 7771, International House, LONDON
SW8 4UJ or telephone 622 9911

Subject of interest.....

Name .....

Address .....

.....

Tel# .....

SOUTHERN VALVE COMPANY

Upper Floor, 8 Potters Road, Barnet, Herts
Telephone: 01-440/8641 **MAIL ORDER ONLY**

ALL NEW & BOXED "QUALITY" BRANDED VALVES GUARANTEED 3 MONTHS.
BVA ETC. (TUNGSRAM FOR OUR PRICES.
6% ALLOWED IN LIEU OF GUARANTEE.
ALREADY DEDUCTED FROM OUR PRICES.
Note: Prices are only correct at time of going to press.
PLEASE VERIFY CURRENT PRICES.
Some leading makes available.
VAT invoices issued on request.

AZ 17	80p	EZ80	41p	PCL200	
DY86/7	49p	EZ81	38p		£1.40
DY802	60p			PD500	£3.25
EB91	18p	EY51/81	£1.10	PFL200	72p
ECC81	36p	GZ30	75p	PL36	70p
ECC82	36p	PC86	62p	PL81	60p
ECC83	36p	PC88	62p	PL81A	85p
ECC85	40p	PC97	50p	PL82	35p
ECC88	80p	PC900	50p	PL83	80p
ECH42	85p	PCC84	52p	PL84	48p
ECH81	44p	PCC85	44p		99p
ECH83	82p	PCC88	62p	PL500	90p
ECH84	85p	PCC89	59p	PL504	
ECL80	52p	PCF80	53p	PL508	£1.30
ECL82	48p	PCF82	41p	PL509	£2.30
ECL83	68p	PCF86	58p	PL519	£3.45
ECL86	49p	PCF800		PL802	£2.10
EF80	33p		£1.20	PY81	40p
EF83	90p	PCF801	39p	PY88	50p
EF85	33p	PCF802	35p	PY800	50p
EF86	52p			PY801	50p
EF183	48p	PCF805	£1.45	PY500	£1.30
EF184	45p	PCF806	75p	PY500A	
EH90	66p	PCF808	75p		£1.30
EL84	£1.10	PCF805		UBF89	40p
EL41	70p		£1.45	UCH81	44p
EL84	40p	PCH200	85p	UCH42	72p
EL86/41	47p	PCL81	52p	UCH81	49p
EL509	£2.75	PCL83	69p	UCL82	45p
EM84	80p	PCL84	48p	UCL83	69p
EY51	39p	PCL85	69p	UF41	70p
EY86/7	39p	PCL		UF89	45p
EY500A		805	62p	UL41	72p
	£1.60	PCL86	62p	UL84	49p

UY85	40p
U25	60p
U26	60p
U191	80p
6/30L2	75p
6BW7	68p
6P25	70p
6P28	70p
6V6 & GL	99p
10F1	99p
20L1	70p
20P4	95p
30C1	41p
30C15	78p
30C17	78p
30C18	£1.45
30F5	80p
30FL1	£1.00
30FL2	£1.00
30L1	85p
30L15	80p
30L17	72p
30P12	80p
30P19	80p
30PL1	£1.40
30PL13	
	£1.00
30PL14	
	£1.10
30PL15	85p
30P4MR	80p
	90p

One valve post 12p, each extra valve 6p. MAX 75p.
LISTS & ENQUIRIES. SAE PLEASE!
Large valves 14p each.
ALL PRICES INCLUDE VAT @ 12½%.

We offer return of post service.
CWO ONLY. No C.O.D.
Post free over £15. £5 to £15—75p (max.).
Items in stock at time of going to press but subject to market fluctuations without notice.
ENQUIRIES WELCOMED FROM TRADE & RETAIL (same prices).

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. Practical Wireless is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be offered or exposed for sale in a mutilated condition or in any unauthorised cover by way of Trade; and that no part of the publication or advertising, literary or pictorial matter whatsoever.

RADIO EXCHANGE LTD.

ALL PRICES INCLUDE VAT

NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit. Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio
- ★ Signal Tracer
- ★ Signal Injector
- ★ Transistor Tester NPN-PNP
- ★ 4 Transistor Push Pull Amplifier
- ★ 5 Transistor Push Pull Amplifier
- ★ 7 Transistor Loudspeaker Radio MW/LW
- ★ 5 Transistor Short Wave Radio
- ★ Electronic Metronome
- ★ Electronic Noise Generator
- ★ Batteryless Crystal Radio
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Regenerative Radio
- ★ Audible Continuity Tester
- ★ Sensitive Pre-Amplifier

Components include: 24 Resistors ★ 21 Capacitors ★ 10 Transistors ★ 5" × 3" Loudspeaker ★ Earpiece ★ Mica Baseboard ★ 3 12-way connectors ★ 2 Volume controls ★ 2 Slider Switches ★ 1 Tuning Condenser ★ 3 Knobs ★ Ready Wound MW/LW/SW Coils ★ Ferrite Rod ★ 64 yards of wire ★ 1 Yard of sleeving, etc. Complete kit of parts including construction plans.

Total Building Costs £9·00 P & P + Ins. £1·10

VHF AIR CONVERTER KIT

Build this Converter Kit and receive the Aircraft Band by placing it by the side of a radio tuned to Medium Wave or the Long Wave Band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome plated telescopic aerial, Gain Control, V.H.F. Tuning Capacitor, Transistor, etc.

All Parts including Case and Plans.

£3·95 P & P and Ins. 60p.

POCKET FIVE

NOW WITH 3" LOUDSPEAKER

5 Tuneable wavebands. M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½" × 14" × 3¼" approx. All Parts including Case and Plans.

Total Building Costs **£3·60** P&P + Ins.80p.

NEW ROAMER TEN MODEL R.K.3.

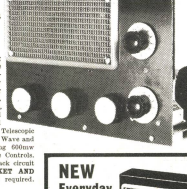

MULTIBAND V.H.F. AND A.M. RECEIVER
13 TRANSISTORS AND FIVE DIODES
QUALITY 6" × 3" LOUDSPEAKER

WITH Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Airspaced Slow Motion Drive Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W., Three Short Wave Bands, S.W.1, S.W.2, S.W.3, & Trawler Band. Built in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome Plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push Pull output using 600mw Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Negative Feedback circuit and **SPECIAL POWER BOOSTER SOCKET AND RESISTOR**, to virtually double gain if required. Powered by P.P.3 9 volt battery.

Complete kit of parts including carrying strap. Building Instructions and Operating Manuals.

£13·99 Including Post and Packing

Case Enclosure Kit (if required) £1·99 inc. P & P.

NEW Everyday Series

Build this exciting new series of designs.

E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" × 6½" × 2¾" approx. All parts including Case and Plans.

Total Building costs **£4·30** P & P + Ins. 80p.

E.V. 6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output.
All parts including Case and Plans.

Total Building costs **£4·95** P & P + Ins. 90p.

E.V. 7. Case and looks as above, 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker.
All parts including Case and Plans.

Total Building costs **£6·95** P & P + Ins. 90p.

ELECTRONIC CONSTRUCTION KITS

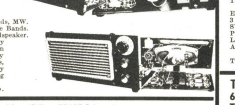

ECK2 Self Contained Multi-Band V.H.F. Receiver Kit. 8 Transistors and 3 Diodes. Push/Pull output. 3" Loudspeaker, Gain Control, 7 section chrome plated telescopic aerial, V.H.F. Tuning Capacitor, Resistors, Capacitors, Transistors, etc. Will receive T.V. Sound, Public Service Band, Aircraft, V.H.F. Local Stations, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit).
Complete kit of parts including construction plans.

£7·95 P & P and Ins. 90p.

ECK4 7 Transistors, 6 tunenble wavebands, MW, LW, Trawler Band, 3 Short Wave Bands. Receiver Kit. With 5" × 3" Loudspeaker. Push/Pull output stage, Gain Control, and Rotary Switch. 7 Transistors and 4 Diodes. 6 section chrome-plated telescopic aerial. 8" Sensitive Ready Wound Ferrite Rod Aerial. Tuning Capacitor, Resistors, Capacitors, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans.

£7·25 P & P and Ins. 90p.

EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- ★ Crystal Radio Medium Wave Coverage — No Battery necessary.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio
- ★ 2 Transistor Earpiece Radio Medium Wave Coverage.
- ★ 4 Transistor Medium Wave Loudspeaker Radio.
- ★ Electronic Noise Generator
- ★ Electronic Metronome.
- ★ 4 Transistor Push/Pull Amplifier.

All parts including Loudspeaker, Earpiece, MW Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans.

£6·55 P & P + Ins. 80p.

To RADIO EXCHANGE LTD
61A HIGH STREET, BEDFORD MK40 1SA
Tel: 0234 52367

ALL PRICES INCLUDE VAT Reg. No. 388372

★ Callers side entrance "Lavells" Shop.
★ Open 10-1, 2.30-4.30. Mon-Fri. 9-12 Sat.

I enclose £ .....

for .....

Name .....

Address .....

.....

PW.977

MAPLIN

ELECTRONIC ORGAN

The only organ you can build in stages and tailor to your requirements as you go along—and at each stage you'll have a fully working instrument! We haven't got the gimmicks (yet—they're coming soon), but we have got the most beautiful sounds—you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.

GRAPHIC EQUALISER

This high quality Graphic Equaliser will enhance even the most sophisticated system at a fraction of the cost of a ready-made equaliser of equal quality. You can get all the parts from us (except woodwork) including drilled and printed metalwork. Construction details in our leaflet: 15p.

TOOLS

We stock an excellent range of tools especially for the electronics enthusiast. From miniature wiring tools to multimeters including soldering irons and desoldering tools, screwdrivers, cutters, pliers, strippers, miniature electric drills for p.c.b.'s, transistor tester etc. Full details on catalogue pages 167 to 176.

PEDAL UNIT

A completely self-contained pedal unit. 13-note, 2-octave range, 4 organ stops. It can be added to any organ! A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue—post the coupon below now!

T.V. GAME

Play fascinating games NOW on your own T.V. in your own living room. The kids will think it's magic when the scores pop up on the screen. Lay your bets—anyone could win—with Maplin's prices everyone can win. Complete kit to play four games only **£24.95**. Add 25p for copy of construction details. See our June newsletter for details of rifle kit.

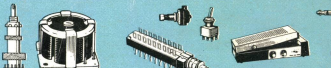

Our monthly newsletter keeps you up to date with latest new and prices – our latest special offers (they save you money) details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!

DON'T MISS OUT! SEND 60p NOW!

POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue by return of post. I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

NAME _____

ADDRESS _____

_____

PW8

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

284 London Road, Westcliff-on-Sea, Essex

Telephone: Southend (0702) 47379